

## I. Integrated circuits

### Introduction:-

The Integrated circuit (or) IC is a miniature, low cost electronic circuit consisting of active and passive elements and they are fabricated on a single silicon chip is called "Integrated circuits".

The main semiconductor material utilized is silicon; but for special applications, gallium arsenide and other semiconductor materials also be utilized.

### Advantages of IC's :-

1. Small size
2. Low cost
3. Less weight
4. Low supply voltages
5. Low power consumption
6. Fast speed
7. Highly reliable

### Types of IC's :- There are 2 types

1. Linear ICs

2. Digital ICs

## 1. Linear ICs (or) Analog ICs :-

The term linear used since output value is a linear function of input.

Ex:- Filters, modulators, Amplifiers like Inverting and Non Inverting.

→ These ICs mostly used in audio and radio frequency applications.

## 2. Digital ICs :-

These ICs concerned with 2 levels either 1 (or) 0.


Low level signal send to a Input, the output should be zero.

High level signal send to a Input, the output should be '1'.

Ex :- counters, Gates, mux etc...

→ These ICs mostly used in consumer electronics.

## Differential Amplifier :-

 

$V_1, V_2 \rightarrow$  Two Input signals

$V_o \rightarrow$  Output signal

In Ideal differential amplifier, output voltage  $V_o$  is proportional to the difference between 2 Input signals.

$$V_o \propto (V_1 - V_2)$$

$$\boxed{V_o = A_d(V_1 - V_2)}$$

differential gain ( $A_d$ ) :-

$$V_o = A_d (V_1 - V_2)$$

where  $A_d \rightarrow$  proportionality constant.  
 $A_d$  is the gain.

consider  $V_1 - V_2 = V_d$

$$\Rightarrow V_o = A_d V_d \Rightarrow A_d = \frac{V_o}{V_d}$$

common mode gain ( $A_c$ ) :-

If we apply 2 Input voltages are equal (common) i.e

$$V_1 = V_2 \text{ then } V_o = A_d (V_1 - V_2)$$

$$= A_d (V_1 - V_1) = 0 \Rightarrow V_o = 0$$

But the output voltage of the practical differential amplifier not only depends on the difference voltage but also depends on the average of 2 inputs.

such an average level of 2 input signals is called common mode signal ( $V_c$ ).

$$V_c = \frac{V_1 + V_2}{2}$$

practically, differential amplifier produces the output voltage proportional to common mode signals,

$$V_o = A_c V_c$$

Total output of any differential amplifier can be expressed as

$$V_o = A_d V_d + A_c V_c$$

## Common mode Rejection Ratio (CMRR) :-

The ability of a differential amplifier to reject a common mode signal is expressed by a ratio called common mode rejection ratio.

It is defined as the ratio of differential gain  $A_d$  to the common mode gain  $A_c$ .

$$\boxed{\text{CMRR} = \frac{|A_d|}{|A_c|}}$$

For,  $A_d \rightarrow \text{large value}$ ,  $A_c \rightarrow \text{small value}$   
 $\text{CMRR} \rightarrow \text{High value.}$

In terms of dB, CMRR in dB =  $20 \log \frac{|A_d|}{|A_c|}$  dB

Output voltage expressed in terms of CMRR as

$$V_o = A_d V_d + A_c V_c = A_d V_d \left[ 1 + \frac{A_c V_c}{A_d V_d} \right]$$

$$= A_d V_d \left[ 1 + \frac{1}{\left( \frac{A_d}{A_c} \right)} \cdot \frac{V_c}{V_d} \right]$$

$$\boxed{V_o = A_d V_d \left[ 1 + \frac{1}{\text{CMRR}} \cdot \frac{V_c}{V_d} \right]}$$

## Features of differential Amplifier :-


There are various features,

1. High differential voltage gain
2. Low common mode gain
3. High CMRR
4. High Input Impedance
5. Low output impedance
6. Low offset voltages and currents.

## operation of differential Amplifier :-
 
### circuit diagram:-

In this diagram,  
there are 2 inputs,  
2 outputs are used.




- Here, 2 separate transistors  $Q_1, Q_2$  are used and apply 2 inputs at base of both transistor.
- 2 separate transistors having similar characteristics ideally, common emitter resistor  $R_E$ , positive supply voltage  $V_{cc}$  and negative supply  $V_{ee}$ .

### working:-

case ① :- A signal is applied at base of transistor  $Q_1$ , and no signal is applied at base of transistor  $Q_2$ .

The Input signal sinusoidal applied at base of the transistor  $Q_1$ .

 First,  
x The positive half cycle  
is applied at base  
of  $Q_1$ , the transistor ON.



- If the transistor turns 'ON' there will be <sup>more</sup> voltage drop across  $R_C_1$ , resulting the collector of  $Q_1$  to be less positive. and current flows through the circuit.
- The -ve half cycle is applied at base of transistor  $Q_1$ , the transistor turned OFF, resulting in less voltage drop across  $R_C_1$ , no current flows through the circuit.
- In this way, an inverted output appears at collector of  $Q_1$ , by applying signal at Input of  $Q_1$ .
- At the time when  $Q_1$  gets ON by +ve half cycle of Input, the current through  $R_E$  will increase. so, Voltage drop at  $R_E$  will be more causing the emitters of both transistors go in +ve direction.
- No input is applied at base of transistor  $Q_2$  (zero Input) so transistor  $Q_2$  turned OFF. There is no voltage drop across  $R_C_1$  and no current flows through the circuit.
- In this way, we will have a non-inverting output at collector of  $Q_2$  for +ve Input at base of  $Q_1$ .

#### case ②:-

The signal is applied at base of transistor  $Q_2$  and no input is applied at transistor  $Q_1$  base terminal.

(4)

In this case, first the +ve half cycle is applied to base of transistor  $Q_{U_2}$ , transistor. ON there will be voltage drop across  $R_{C_2}$  and current flows through it.

second, The -ve half cycle is applied

at  $Q_{U_2}$ , transistor turned OFF. So, there is no voltage drop across  $R_{C_2}$  and no current flows through it.


So, there will be Inverted output at  $R_{C_2}$ .

→ No Input is applied at base of transistor  $Q_{U_1}$ , so the transistor turned OFF, no voltage drop across  $R_{C_1}$ . So the output across  $R_{C_1}$  will be Non-Inverted output.


### Differential Amplifier configurations :-

Depending upon Input and output terminals of differential Amplifier, there are 4 configurations.

 1. Dual Input Balanced output
2. Dual Input unbalanced output
3. Single Input balanced output
4. Single Input unbalanced output



 
## 1. Dual Input balanced output (DIBO) :-



In this configuration, two inputs are applied at base of transistor Q<sub>1</sub>, Q<sub>2</sub> and output is taken between 2 collector terminals so, this configuration called as "Dual Input balanced output" (or) Dual Input double ended output (or) floating output - (or) symmetrical differential amplifier.

 
## 2. Dual Input unbalanced output (DIUBO) :-



In this configuration, & Inputs applied at base of transistor  $\text{Q}_1, \text{Q}_2$  and output is taken between one collector terminal is called "dual Input unbalanced output" (or) "Dual Input single ended output."
 
### 3. single Input balanced output (SIBO):-


In this configuration, only one Input is applied at base of transistor  $\text{Q}_1$ , and output is taken between 2 collector terminals



is called "single Input balanced output" (or) "single Input double ended output".
 
### 4. single Input unbalanced output (SIUBO):-


In this configuration, only one Input is applied at base of transistor  $\text{Q}_1$  and output is taken at only one collector terminal is called "single Input unbalanced output" (or) "single Input single ended output".


 
## D.C Analysis of differential Amplifier :-

To determine the operating point values i.e  $I_{CQ}$  and  $V_{CEQ}$  for the differential Amplifier.

The DC equivalent circuit can be obtained by reducing the input A.C signals to zero.



→ Both transistors are matched transistors i.e symmetrical,

$$i) R_{C1} = R_{C2} = R_C$$

$$ii) R_E1 = R_E2 = R_E \quad (\because R_E = R_{E1} \parallel R_{E2})$$

$$iii) R_{in1} = R_{in2} = R_{in}$$

To find out operating points  $I_{CQ}$  and  $V_{CEQ}$ , for any one of the transistors. same is applicable for other transistor.

APPLY KVL TO Base-emitter loop

$$-R_{in}I_B - V_{BE} - R_E(2I_E) - (-V_{EE}) = 0$$

$$-R_{in}I_B - V_{BE} - 2I_E R_E + V_{EE} = 0 \quad \text{--- ①}$$

we know that,

$$\beta_{dc} = \frac{I_E}{I_B} \Rightarrow I_B = \frac{I_E}{\beta_{dc}} \quad \text{--- (2)}$$

substitute eq (2) in eq (1),

$$-R_{in} I_B - V_{BE} - 2R_E I_E + V_{EE} = 0$$

$$\Rightarrow V_{EE} - V_{BE} = R_{in} I_B + 2R_E I_E$$

$$\Rightarrow V_{EE} - V_{BE} = R_{in} \left( \frac{I_E}{\beta_{dc}} \right) + 2R_E I_E$$

$$= I_E \left( \frac{R_{in}}{\beta_{dc}} + 2R_E \right)$$

$$\Rightarrow I_E = \frac{V_{EE} - V_{BE}}{\left( \frac{R_{in}}{\beta_{dc}} \right) + 2R_E}$$

where,  $V_{BE} = 0.6$  to  $0.7$  for Si

$= 0.2$  for Ge.

consider  $\frac{R_{in}}{\beta_{dc}} \ll 2R_E$

$$\Rightarrow I_E = \frac{V_{EE} - V_{BE}}{2R_E} \quad \text{--- (3)}$$

w.k.t  $I_E \approx I_C$

$$\Rightarrow \boxed{I_{CQ} = \frac{V_{EE} - V_{BE}}{2R_E}} \quad \text{--- (4)}$$

determine  $V_{CEQ}$  :-

collector voltage of Q1, as

$$V_C = V_{CC} - I_C R_C \quad \text{--- (5)} \quad (\because V_{CC} = I_C R_C + V_C \\ \Rightarrow V_C = -I_C R_C + V_{CC})$$

collector-to-emitter voltage is

$$V_{CE} = V_C - V_E \quad \text{--- (6)}$$

substitute eq (5) in eq (6),

$$\Rightarrow V_{CE} = V_{CC} - I_C R_C - V_E \\ = V_{CC} - I_C R_C - (-V_{BE}) \quad (\because V_E = V_{BE})$$

$$V_{CE} = V_{CC} + V_{BE} - I_C R_C$$

(or)

$$V_{CEQ} = V_{CC} + V_{BE} - I_{CQ} R_C \quad \text{--- (7)}$$

Note :- The D.C Analysis expressions for  $I_{CQ}$  and  $V_{CEQ}$  remain same for all the four differential amplifier configurations.

A.C Analysis :-

To perform A.C Analysis to derive the expressions for voltage gain ( $A_v$ ), input resistance ( $R_i$ ) and output resistance ( $R_o$ ).

Assumptions:-

- i) set the D.C voltages  $+V_{CC}$  and  $-V_{EE} = 0$
- ii) substitute the small signal T equivalent models for the transistors.

7

## i. Dual Input balanced output differential Amplifier :-


 


Fig:- A.C equivalent circuit for Dual Input balanced output

 

### i) Voltage gain (A\_v)

KVL for Loop 1 and 2

$$v_{in1} - I_{b1} R_{in1} - \gamma_e i_{e1} - R_E (i_{e1} + i_{e2}) = 0 \quad \text{--- (1)}$$

$$v_{in2} - I_{b2} R_{in2} - \gamma_e i_{e2} - R_E (i_{e1} + i_{e2}) = 0 \quad \text{--- (2)}$$

$$\text{w.k.t} \quad \beta_{ac} = \frac{i_e}{i_b} \Rightarrow i_b = \frac{i_e}{\beta_{ac}}$$

$$\text{so} \quad i_{b1} = \frac{i_{e1}}{\beta_{ac}} \quad \text{--- (3)} \quad , \quad i_{b2} = \frac{i_{e2}}{\beta_{ac}} \quad \text{--- (4)}$$

Substitute eq (3), (4) in eq (1), (2)

$$\text{eq (1)} \Rightarrow v_{in1} - \left( \frac{i_{e1}}{\beta_{ac}} \right) R_{in1} - \gamma_e i_{e1} - R_E (i_{e1} + i_{e2}) = 0$$

$$\Rightarrow v_{in1} = \left( \frac{i_{e1}}{\beta_{ac}} \right) R_{in1} + \gamma_e i_{e1} + R_E (i_{e1} + i_{e2})$$

$$\Rightarrow V_{in1} = ie_1 \left( \frac{R_{in1}}{\beta_{ac}} \right) + r_e ie_1 + R_E ie_1 + R_E ie_2 \\ = ie_1 \left( \frac{R_{in1}}{\beta_{ac}} + r_e + R_E \right) + R_E ie_2 \quad \text{--- (5)}$$

eq(2)  $\Rightarrow$

$$V_{in2} - \left( \frac{ie_2}{\beta_{ac}} \right) R_{in2} - r_e ie_2 - R_E (ie_1 + ie_2)$$

$$\Rightarrow V_{in2} = ie_2 \left( \frac{R_{in2}}{\beta_{ac}} \right) + r_e ie_2 + R_E ie_1 + R_E ie_2 \\ = ie_2 \left( \frac{R_{in2}}{\beta_{ac}} + r_e + R_E \right) + R_E ie_1 \quad \text{--- (6)}$$

consider  $(r_e + R_E) \gg \frac{R_{in1}}{\beta_{ac}}$  and  $(r_e + R_E) \gg \frac{R_{in2}}{\beta_{ac}}$  then

eq(5), eq(6) changes to

$$V_{in1} = ie_1 (r_e + R_E) + R_E ie_2 \quad \text{--- (7)}$$

$$V_{in2} = ie_2 (r_e + R_E) + R_E ie_1 \quad \text{--- (8)}$$

eq(7), eq(8) can be written as

$$(r_e + R_E) ie_1 + (R_E) ie_2 = V_{in1}$$

$$(R_E) ie_1 + (r_e + R_E) ie_2 = V_{in2}$$

APPLY cramer's rule

$$ie_1 = \frac{\begin{vmatrix} V_{in1} & R_E \\ V_{in2} & r_e + R_E \end{vmatrix}}{\begin{vmatrix} r_e + R_E & R_E \\ r_e + R_E & r_e + R_E \end{vmatrix}} \quad \text{and} \quad ie_2 = \frac{\begin{vmatrix} r_e + R_E & V_{in1} \\ R_E & V_{in2} \end{vmatrix}}{\begin{vmatrix} r_e + R_E & R_E \\ R_E & r_e + R_E \end{vmatrix}}$$

$$i_{e_1} = \frac{(\gamma_e + R_E) V_{in1} - R_E V_{in2}}{(\gamma_e + R_E)^2 - R_E^2} \quad , \quad i_{e_2} = \frac{(\gamma_e + R_E) V_{in2} - R_E V_{in1}}{(\gamma_e + R_E)^2 - R_E^2} \quad \text{--- (9)} \quad \text{--- (10)}$$

The output voltage  $V_o = V_{c_2} - V_{c_1}$

$$= -R_C i_{c_2} - (-R_C i_{c_1})$$

$$= -R_C i_{c_2} + R_C i_{c_1}$$

$$\omega \cdot k \cdot T \quad I_c \approx I_E \quad , \quad V_o = -R_C i_{e_2} + R_C i_{e_1} \quad \text{--- (11)}$$

Substitute eq (9), (10) in eq (11)

$$\Rightarrow V_o = -R_C \left[ \frac{(\gamma_e + R_E) V_{in2} - R_E V_{in1}}{(\gamma_e + R_E)^2 - R_E^2} \right] + R_C \left[ \frac{(\gamma_e + R_E) V_{in1} - R_E V_{in2}}{(\gamma_e + R_E)^2 - R_E^2} \right]$$

$$= R_C \left[ \frac{(\gamma_e + R_E) V_{in1} - R_E V_{in2} - (\gamma_e + R_E) V_{in2} + R_E V_{in1}}{(\gamma_e + R_E)^2 - R_E^2} \right]$$

$$= R_C \left[ \frac{(\gamma_e + R_E)(V_{in1} - V_{in2}) + R_E(V_{in1} - V_{in2})}{\gamma_e^2 + R_E^2 + 2\gamma_e R_E - R_E^2} \right]$$

$$= R_C \left[ \frac{(\gamma_e + R_E + R_E)(V_{in1} - V_{in2})}{\gamma_e(\gamma_e + 2R_E)} \right]$$

$$V_o = R_C \left[ \frac{(\gamma_e + 2R_E)(V_{id})}{\gamma_e(\gamma_e + 2R_E)} \right] \quad (\because V_{in1} - V_{in2} = V_{id})$$

$$V_o = \frac{R_C}{\gamma_e} V_{id} \quad \Rightarrow \frac{V_o}{V_{id}} = \frac{R_C}{\gamma_e} \quad (\because \frac{V_o}{V_{id}} = A_D)$$

$$\Rightarrow A_D = \frac{R_C}{\gamma_e}$$

ii) Input resistance ( $R_{i1}$ ):-

$$R_{i1} = \frac{V_{in1}}{I_{b1}} \quad |_{V_{in2}=0} \quad -\textcircled{1}$$

$$\text{W.K.T} \quad i_{b1} = \frac{i_{e1}}{\beta_{ac}} \quad -\textcircled{2}$$

Substitute eqn  $\textcircled{2}$  in eqn  $\textcircled{1}$

$$R_{i1} = \frac{V_{in1}}{i_{e1}/\beta_{ac}} \quad |_{V_{in2}=0} \quad -\textcircled{3}$$

Substitute  $i_{e1}, i_{e2}$  values

$$R_{i1} = \frac{\frac{V_{in1} \beta_{ac}}{(r_e + R_E) V_{in1} - R_E V_{in2}}}{\frac{(r_e + R_E)^2 - (R_E)^2}{(r_e + R_E)^2 + 2r_e R_E - R_E^2}} \quad |_{V_{in2}=0}$$

$$= \frac{\frac{V_{in1} \beta_{ac}}{(r_e + R_E) V_{in1} - R_E(0)}}{\frac{r_e^2 + R_E^2 + 2r_e R_E - R_E^2}{r_e^2 + R_E^2 + 2r_e R_E - R_E^2}}$$

$$= \frac{\frac{V_{in1} \beta_{ac}}{(r_e + R_E) V_{in1}}}{r_e(r_e + 2R_E)}$$

$$= \frac{\beta_{ac} r_e (r_e + 2R_E)}{r_e + R_E}$$

$$R_{i2} = \frac{V_{in2}}{I_{b2}} \quad |_{V_{in1}=0} \quad -\textcircled{1}$$

$$i_{b2} = \frac{i_{e2}}{\beta_{ac}} \quad -\textcircled{2}$$

$$R_{i2} = \frac{\frac{V_{in2}}{i_{e2}/\beta_{ac}}}{\frac{(r_e + R_E)^2 - (R_E)^2}{(r_e + R_E)^2 + 2r_e R_E - R_E^2}} \quad |_{V_{in1}=0} \quad -\textcircled{3}$$

$$R_{i2} = \frac{\frac{V_{in2} \beta_{ac}}{(r_e + R_E) V_{in2} - R_E V_{in1}}}{\frac{(r_e + R_E)^2 - (R_E)^2}{(r_e + R_E)^2 + 2r_e R_E - R_E^2}} \quad |_{V_{in1}=0}$$

$$= \frac{\frac{V_{in2} \beta_{ac}}{(r_e + R_E) V_{in2} - R_E(0)}}{\frac{r_e^2 + R_E^2 + 2r_e R_E - R_E^2}{r_e^2 + R_E^2 + 2r_e R_E - R_E^2}}$$

$$= \frac{\frac{V_{in2} \beta_{ac}}{(r_e + R_E) V_{in2}}}{r_e(r_e + 2R_E)}$$

$$= \frac{\beta_{ac} r_e (r_e + 2R_E)}{r_e + R_E}$$

$$R_E \gg r_e$$

$$\Rightarrow R_{i1} = \frac{\beta_{ac} r_e (2R_E)}{R_E}$$

$$\Rightarrow R_{i1} = 2\beta_{ac} r_e$$

$$R_E \gg r_e$$

$$\Rightarrow R_{i2} = \frac{\beta_{ac} r_e (2R_E)}{R_E}$$



$$\Rightarrow R_{i2} = 2\beta_{ac} r_e$$

### iii) output resistance:-

In dual input balanced output configuration output is taken between 2 collector terminals i.e

$$R_{out1} = R_{out2} = R_C \quad (\text{or}) \quad R_{o1} = R_{o2} = R_C$$
  
### 2. Dual Input unbalanced output differential amplifier :-



i) Voltage gain ( $A_v$ ) :-

APPLY KVL TO LOOP ① & ②

$$V_{in1} - I_{b1}R_{in1} - \gamma_e i_{e1} - R_E(i_{e1} + i_{e2}) = 0 \quad \text{--- ①}$$

$$V_{in2} - I_{b2}R_{in2} - \gamma_e i_{e2} - R_E(i_{e1} + i_{e2}) = 0 \quad \text{--- ②}$$

$$\text{at } kT \quad I_{b1} = \frac{i_{e1}}{\beta_{ac}}, \quad I_{b2} = \frac{i_{e2}}{\beta_{ac}}$$

Substitute  $i_{b1}, i_{b2}$  values in eqn ①, ②

$$\text{from eqn ①, } V_{in1} = \frac{i_{e1}}{\beta_{ac}} R_{in1} + \gamma_e i_{e1} + R_E i_{e1} + R_E i_{e2}$$

$$= i_{e1} \left( \frac{R_{in1}}{\beta_{ac}} + \gamma_e + R_E \right) + R_E i_{e2} \quad \text{--- ③}$$

$$\text{eqn ②} \Rightarrow V_{in2} = i_{e2} \left( \frac{R_{in2}}{\beta_{ac}} + \gamma_e + R_E \right) + R_E i_{e1} \quad \text{--- ④}$$

consider  $(\gamma_e + R_E) \gg \frac{R_{in1}}{\beta_{ac}}$  and  $(\gamma_e + R_E) \gg \frac{R_{in2}}{\beta_{ac}}$  then

$$\text{eqn ③} \Rightarrow V_{in1} = i_{e1} (\gamma_e + R_E) + R_E i_{e2} \quad \text{--- ⑤}$$

$$\text{eqn ④} \Rightarrow V_{in2} = i_{e2} (\gamma_e + R_E) + R_E i_{e1} \quad \text{--- ⑥}$$

APPLY CRAMMERS RULE :-

$$i_{e1} = \frac{(\gamma_e + R_E) V_{in1} - R_E V_{in2}}{(\gamma_e + R_E)^2 - R_E^2} \quad \text{and}$$

$$i_{e2} = \frac{(\gamma_e + R_E) V_{in2} - R_E V_{in1}}{(\gamma_e + R_E)^2 - R_E^2}$$

The output voltage,  $V_o = V_{C2}$

$$= -i_{C2} R_{C2} = -i_{E2} R_{C2} \quad (\because i_C = i_E, R_{C2} = R_E)$$

$$V_o = -R_C i_{E2}$$

$$= -R_C \left[ \frac{(r_e + R_E) V_{in2} - R_E V_{in1}}{(r_e + R_E)^2 - R_E^2} \right]$$

$$= R_C \left[ \frac{R_E V_{in1} - (r_e + R_E) V_{in2}}{r_e^2 + R_E^2 + 2r_e R_E - R_E^2} \right]$$

$$= R_C \left[ \frac{R_E V_{in1} - (r_e + R_E) V_{in2}}{r_e(r_e + 2R_E)} \right]$$

$$= R_C \left[ \frac{R_E (V_{in1} - V_{in2})}{r_e (2R_E)} \right] \quad (\because R_E \gg r_e)$$

$$V_o = R_C \left[ \frac{V_{id}}{2r_e} \right] \quad (\because V_{in1} - V_{in2} = V_{id})$$

$$\Rightarrow \frac{V_o}{V_{id}} = \frac{R_C}{2r_e} \Rightarrow A_d = \boxed{\frac{R_C}{2r_e}}$$

The voltage gain is half the gain of dual input, balanced output differential amplifier.

ii) Input resistance :-


$$R_{i1} = R_{i2} = 2 \beta_{ac} r_e$$

( $\because$  Procedure is same as dual input balanced output - Input resistance)

iii) Output resistance :- In this configuration output is taken between one collector terminal  
i.e.  $R_{o2} = R_C$
 
### 3. single Input balanced output differential amplifier:-

In this configuration, Input is applied to base of transistor Q<sub>1</sub> and output is measured between 2 collector terminals.



i) Voltage gain ( $A_v$ ) :-

APPLY KVL to Loop ①, Loop ②

$$V_{in} - I_{b1}R_{in1} - r_e i_{e1} - R_C \frac{I_E}{\beta_{ac}} = 0 \quad \text{--- ①}$$

$$V_{in} - I_{b1}R_{in1} - r_e i_{e1} - r_e i_{e2} = 0 \quad \text{--- ②}$$

$$\text{W.K.T} \quad I_{b1} = \frac{i_{e1}}{\beta_{ac}}, \quad I_{b2} = \frac{i_{e2}}{\beta_{ac}}$$

Substitute  $I_{b1}, I_{b2}$  in eq ①, ②

from eq①,

$$v_{in} - \left( \frac{ie_1}{\beta_{ac}} \right) R_{in1} - r_e i e_1 - R_E (i e_1 - i e_2) = 0 \quad (\because I_E = i e_1 - i e_2)$$

$$\Rightarrow v_{in} = \frac{R_{in1}}{\beta_{ac}} i e_1 + r_e i e_1 + R_E i e_1 - R_E i e_2$$

$$= i e_1 \left( \frac{R_{in1}}{\beta_{ac}} + r_e + R_E \right) - R_E i e_2 \quad (\because (r_e + R_E) \gg \frac{R_{in1}}{\beta_{ac}})$$

$$v_{in} = i e_1 (r_e + R_E) - R_E (i e_2) \quad \text{--- } ③$$

from eq②,

$$v_{in} = \left( \frac{ie_1}{\beta_{ac}} \right) R_{in1} + r_e i e_1 + r_e i e_2$$

$$= i e_1 \left( \frac{R_{in1}}{\beta_{ac}} + r_e \right) + r_e i e_2$$

$$v_{in} = i e_1 (r_e) + r_e i e_2 \quad \text{--- } ④ \quad (\because r_e \gg \frac{R_{in1}}{\beta_{ac}})$$

APPLY CRAMMERS RULE

$$i e_1 = \frac{\begin{vmatrix} v_{in} & -R_E \\ v_{in} & r_e \end{vmatrix}}{\begin{vmatrix} r_e + R_E & -R_E \\ r_e & r_e \end{vmatrix}} = \frac{v_{in} r_e + R_E v_{in}}{(r_e + R_E) \frac{r_e}{R_E} + R_E r_e}$$

$$= \frac{(r_e + R_E) v_{in}}{r_e [r_e + R_E + R_E]}$$

$$= \frac{(r_e + R_E) v_{in}}{r_e (r_e + 2R_E)} \quad \text{--- } ⑤$$

and

$$i_{e_2} = \frac{\begin{vmatrix} \gamma_e + R_E & V_{in} \\ \gamma_e & V_{in} \end{vmatrix}}{\begin{vmatrix} \gamma_e + R_E & -R_E \\ \gamma_e & \gamma_e \end{vmatrix}} = \frac{(\gamma_e + R_E)V_{in} - V_{in}\gamma_e}{(\gamma_e + R_E)\gamma_e + R_E\gamma_e}$$
$$= \frac{\gamma_e V_{in} + R_E V_{in} - V_{in}\gamma_e}{\gamma_e[\gamma_e + R_E + R_E]}$$
$$= \frac{\gamma_e V_{in}}{\gamma_e(\gamma_e + 2R_E)} \quad \frac{R_E V_{in}}{\gamma_e(\gamma_e + 2R_E)}$$

$$\text{The output voltage } V_o = V_{C_2} - V_{C_1}$$

$$= R_C i_{C_2} - (-R_C i_{C_1})$$

$$= R_C i_{C_2} + R_C i_{C_1} \Rightarrow R_C (i_{C_1} + i_{C_2})$$

$$\Rightarrow R_C (i_{e_1} + i_{e_2}) \quad (\because i_C \approx i_e)$$

$$V_o = R_C \left[ \frac{(\gamma_e + R_E) V_{in}}{\gamma_e(\gamma_e + 2R_E)} + \frac{R_E V_{in}}{\gamma_e(\gamma_e + 2R_E)} \right]$$

$$= R_C \left[ \frac{(\gamma_e + R_E) V_{in} + R_E V_{in}}{\gamma_e(\gamma_e + 2R_E)} \right]$$

$$= R_C \left[ \frac{(\gamma_e + R_E + R_E) V_{in}}{\gamma_e(\gamma_e + 2R_E)} \right] \Rightarrow R_C \left[ \frac{(\gamma_e + 2R_E) V_{in}}{\gamma_e(\gamma_e + 2R_E)} \right]$$

$$V_o = \frac{R_C}{\gamma_e} \cdot V_{in}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{R_C}{\gamma_e} \Rightarrow A_d = \boxed{\frac{R_C}{\gamma_e}}$$

ii) Input resistance :-

$$R_i = \frac{V_{in}}{I_{b1}}$$

$$\text{W.K.T. } I_{b1} = \frac{i_{e1}}{\beta_{ac}}$$

$$\Rightarrow R_i = \frac{V_{in}}{i_{e1}/\beta_{ac}} \Rightarrow \frac{V_{in} \beta_{ac}}{i_{e1}}$$

$$\text{W.K.T. } i_{e1} = \frac{(r_e + R_E) V_{in}}{r_e (r_e + 2R_E)}$$

$$\Rightarrow R_i = \frac{\frac{V_{in} \beta_{ac}}{(r_e + R_E) V_{in}}}{\frac{r_e (r_e + 2R_E)}{r_e (r_e + 2R_E)}} = \frac{\beta_{ac} r_e (r_e + 2R_E)}{r_e + R_E}$$

consider  $R_E \gg r_e$

$$\Rightarrow R_i = \frac{\beta_{ac} r_e (2R_E)}{R_E}$$



$$\Rightarrow R_i = 2 \beta_{ac} r_e$$

iii) Output resistance :- In this configuration, the output is

taken between 2 collector terminals so,

\*  $R_{O1} = R_{O2} = R_C$  (or)  $R_{C1} = R_{C2} = R_C$
  
#### 4. single Input unbalanced output differential Amplifier :-



i) Voltage gain ( $A_d$ ) :-

$$\begin{aligned} \text{output voltage } V_o &= V_{c2} \\ &= R_C i_{c2} \\ &= R_C i_{e2} \quad (\because i_{c2} \approx i_{e2}) \end{aligned}$$

[∴ Procedure same as  
Single Input  
balanced output  
for calculating  $i_{e2}$   
Value]

$$V_o = R_C \left[ \frac{R_E V_{in}}{\gamma_e(\gamma_e + 2R_E)} \right]$$

$$= R_C \left[ \frac{R_E V_{in}}{\gamma_e(2R_E)} \right] \quad \left[ \because \gamma_e + 2R_E \approx 2R_E \right]$$

$$V_o = R_C \left[ \frac{V_{in}}{2\gamma_e} \right]$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{R_C}{2\gamma_e} \quad \Rightarrow A_d = \frac{R_C}{2\gamma_e}$$

The voltage gain is half the gain of single Input balanced output configuration.

ii) Input resistance :-

$$R_i = 2\beta_{ac} r_e$$

→ The Procedure is same as  
single input balanced output  
differential Amplifier I/p resistance

iii) output resistance ( $R_o$ ) :-

In this configuration output is taken between only one collector terminal so,

$$R_{o2} = R_c$$

comparisons of different configurations (using  $\gamma$ -parameters)


configuration	Differential gain ( $A_d$ )	Input resistance ( $R_i$ )	Output resistance ( $R_o$ )
Dual Input balanced output	$A_d = \frac{R_c}{2r_e}$	$R_{i1} = R_{i2} = 2\beta_{ac} r_e$	$R_{o1} = R_{o2} = R_c$
Dual Input unbalanced output	$A_d = \frac{R_c}{2r_e}$	$R_{i1} = R_{i2} = 2\beta_{ac} r_e$	$R_{o2} = R_c$
Single Input balanced output	$A_d = \frac{R_c}{r_e}$	$R_i = R_{i1} = 2\beta_{ac} r_e$	$R_{o1} = R_{o2} = R_c$
Single Input unbalanced output	$A_d = \frac{R_c}{2r_e}$	$R_i = R_{i1} = 2\beta_{ac} r_e$	$R_{o2} = R_c$

## A.C Analysis of differential Amplifier using h-parameters

In differential Amplifier, 2 transistors has similar characteristics i.e. Input voltage  $V_{in1} = V_{in2} = V_{in}$  and  $R_{E1} = R_{E2} = R_E$ .
 
### i) Differential Gain ( $A_d$ ):-

To calculate differential gain, consider only one transistor. This is called as Half circuit concept Analysis.



The equivalent circuit diagram for above circuit can be shown in fig. below, neglecting  $h_{oe}$ .

APPLY KVL to Input loop,

$$\frac{V_S}{2} = R_S i_b + h_{ie} i_b$$

$$= i_b (R_S + h_{ie})$$

 


Fig:- APPROXIMATE HYBRID MODEL

$$\Rightarrow i_b = \frac{V_S}{2(R_S + h_{ie})} \quad \text{--- (1)}$$

APPLY KVL to Output loop,

$$V_0 = -h_{fe} I_b R_C \quad \text{--- (2)}$$

Substitute eq (1) in eq (2)

$$\Rightarrow V_0 = -h_{fe} \left[ \frac{V_S}{2(R_S + h_{ie})} \right] R_C$$

$$\Rightarrow \frac{V_o}{V_s} = -\frac{h_{fe} R_c}{2(R_s + h_{ie})}$$

'-' sign indicates the phase difference between Input and output.

magnitude of differential gain  $A_d$  is

$$A_d = \frac{V_o}{V_s} = \frac{h_{fe} R_c}{2(R_s + h_{ie})}$$

→ FOR imbalanced output.  
—③


Note :- FOR Balanced output,  $A_d = 2 \times \frac{h_{fe} R_c}{2(R_s + h_{ie})}$

$$A_d = \frac{h_{fe} R_c}{R_s + h_{ie}}$$

 ii) common mode gain ( $A_c$ ) :-

$$\text{For common mode gain } V_c = \frac{V_1 + V_2}{2} = \frac{V_s + V_s}{2} = V_s$$

The equivalent circuit as shown in figure,



APPLY KVL to Input loop,

$$\begin{aligned} V_s &= I_b h_{ie} + 2R_E (I_b + h_{fe} I_b) + R_S I_b \\ &= I_b h_{ie} + 2R_E (1 + h_{fe}) I_b + R_S I_b \\ &= (h_{ie} + (1 + h_{fe}) 2R_E + R_S) I_b \quad —④ \end{aligned}$$

At output,  $V_o = -I_c R_c$

$$= -h_{fe} I_b R_c \quad —⑤$$

we know that,  $V_o = A_C \cdot V_S \Rightarrow A_C = \frac{V_o}{V_S} \quad \text{--- (6)}$

substitute eq (4), (5) in eq (6)

$$A_C = \frac{-h_{fe} I_b R_C}{(h_{ie} + (1+h_{fe}) 2R_E) I_b}$$

$$\Rightarrow A_C = \boxed{\frac{-h_{fe} R_C}{R_s h_{ie} + (1+h_{fe}) 2R_E}} \quad \text{--- (7)}$$

iii) CMRR :-  $CMRR = \left| \frac{A_d}{A_c} \right|$

$$= \frac{h_{fe} R_C}{2(R_s + h_{ie})} \times \frac{R_s + h_{ie} + (1+h_{fe}) 2R_E}{h_{fe} R_C}$$

$$CMRR = \boxed{\frac{R_s + h_{ie} + 2R_E (1+h_{fe})}{2(R_s + h_{ie})}} \quad \text{--- (8)}$$

iv) Input Impedance (or) Input resistance ( $R_i$ ) :-

$$R_i = \frac{V_S}{I_b} \quad \text{--- (9)}$$

$$\text{from eq (1), } I_b = \frac{V_S}{2(R_s + h_{ie})}$$

substitute  $I_b$  value in eq (9),


$$R_i = \frac{V_S}{\frac{V_S}{2(R_s + h_{ie})}} \Rightarrow R_i = 2(R_s + h_{ie})$$

v) Output resistance ( $R_o$ ) :- output taken between one of the output terminal.

i.e  $\boxed{R_o = R_C}$
 
### D.C coupling:-

The first stage output is connected to the next stage input is called coupling.



It is also called as cascading (or) multistaging (or) direct coupling.

### Cascaded differential Amplifier stages :- (or) Intermediate stage of an op-amp

The main purpose of the cascaded differential Amplifier is to provide high gain to the differential mode signal and cancel the common mode signal.

- In cascading of differential Amplifiers, output of one stage given to input of next stage.
- In this circuit, two differential Amplifiers are connected in series.

The series connection of differential Amplifiers is called cascading of differential Amplifiers, which is used to produce single ended output.

The circuit diagram for cascaded differential Amplifier is shown in fig. below

 


Fig:- cascaded differential Amplifier stages.

From figure,

$Q_1, Q_2$  are first stage transistors i.e dual Input balanced output configuration.  $Q_3, Q_4$  are second stage transistors i.e dual Input unbalanced output configuration.

→ The collector resistances of 1<sup>st</sup> stage are equal i.e  $R_{C1}$  while collector resistances of 2<sup>nd</sup> stage are equal  $R_{C2}$ .

→ First stage is a dual Input balanced output differential Amplifier . it uses emitter resistance  $R_{E1}$  which carries a current  $2I_{E1}$ , where  $I_{E1}$  is the emitter current of transistor  $Q_1$ , which is same as emitter current of transistor  $Q_2$  as the transistors are perfectly matched.

→ The second stage uses a pair of swamping resistances and emitter resistance  $R_{E2}$ . It carries a current of  $2I_B + 2I_{E3}$ .

### Swamping resistances :-

To achieve high input resistance, external resistances  $R'_E$  are connected in series with each emitter of transistor. Such resistances are called swamping resistors.


The various effects of swamping resistances used in differential amplifiers are,

- i) Increase Input resistance
- ii) minimization of changes in transistor parameters due to change in temperature
- iii) Increase in the linearity range of differential Amplifier
- iv) Reduction in <sup>common mode</sup> differential gain.

→ The main advantages of cascaded differential Amplifiers are

- i) Gain value Increases
- ii) Input Impedance is very high
- iii) CMRR Increases.
 
## Differential Amplifier with Swamping resistors (Extra syllabus)



### D.C Analysis

For calculating D.C Analysis, consider V<sub>in1</sub>, V<sub>in2</sub> values should be zero.

Apply KVL at Input loop,

$$-I_B R_{in1} - V_{BE} - I_E R'_E - 2I_E R_E + V_{EE} = 0 \quad \text{--- (1)}$$

$$\text{w.k.t } I_B = \frac{I_E}{\beta_{dc}} \quad \text{--- (2)}$$

Substitute eq(2) in (1)

$$-\frac{I_E}{\beta_{dc}} R_{in1} - I_E R'_E - 2I_E R_E = V_{BE} + V_{EE} = 0$$

$$V_{EE} - V_{BE} = I_E \left( -\frac{R_{in1}}{\beta_{dc}} + R'_E + 2R_E \right)$$

$$\Rightarrow I_E = \frac{V_{EE} - V_{BE}}{2R_E + R'_E} \quad \left( \because R'_E + 2R_E \gg \frac{R_{in}}{\beta_{dc}} \right)$$

Now

Apply KVL to output loop,

$$V_{CE} = V_{CC} + V_{BE} - I_C R_C$$

### A.C Analysis:-

For calculating A.C Analysis, D.C voltages i.e.  $V_{CC}$  and  $-V_{EE}$  should be zero.

$$\text{i) Differential gain } (A_d) = \frac{h_{fe} R_C}{R_S + h_{ie} + (1+h_{fe}) R'_E} \rightarrow \begin{matrix} \text{Dual Input} \\ \text{Balanced output} \end{matrix}$$

$$\text{and } A_d = \frac{h_{fe} R_C}{2[R_S + h_{ie} + (1+h_{fe}) R'_E]} \rightarrow \begin{matrix} \text{Dual Input} \\ \text{unbalanced output} \end{matrix}$$

ii) common mode gain for both transistors is

$$A_c = \frac{h_{fe} R_C}{R_S + h_{ie} + (1+h_{fe}) (R'_E + 2R_E)}$$

iii) Input Impedance,  $R_{in} = 2[R_S + h_{ie} + (1+h_{fe}) R'_E]$

iv) Output Impedance,  $R_o = R_C$

### Methods of Improving CMRR :-

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|$$

To Improve the CMRR, common mode gain  $A_c$  must be reduced.

→ In differential Amplifier circuit,  $R_E$  can be replaced by 2 methods

i) constant current bias method

ii) use of current mirror circuit

i) constant current bias method :-

In the differential Amplifier circuit, the resistance  $R_E$  can be replaced by constant current source method gives effect of a very high resistance without affecting Q-point values of differential amplifier.

APPLY KVL TO  $Q_3$

$$-IR_1 - IR_2 - (-V_{EE}) = 0$$

$$-I(R_1 + R_2) = -V_{EE}$$

$$\Rightarrow I = \frac{V_{EE}}{R_1 + R_2}$$

consider

$$V_B = -IR_1 \quad \text{--- (2)}$$

Substitute eq(1) in eq(2)

$$V_B = \left( -\frac{V_{EE}}{R_1 + R_2} \right) R_1 \quad \text{--- (3)}$$

 


Fig:- constant current source

$$\text{w.r.t } V_{BE} = V_B - V_E$$

$$\Rightarrow V_E = V_B - V_{BE} \quad \text{--- (4)}$$

Substitute eq(3) in (4)

$$V_E = \left( -\frac{V_{EE}}{R_1 + R_2} \right) R_1 - V_{BE} \quad \text{--- (5)}$$

From figure,

$$I_{E3} = \frac{V_E - (-V_{EE})}{R_3} = \frac{V_E + V_{EE}}{R_3} \quad \text{--- (6)}$$

Sub. eq(5) in eq(6)

$$\begin{aligned} I_{E3} &= \frac{V_B - V_{BE} + V_{EE}}{R_3} = \frac{-V_{EE} R_1}{R_1 + R_2} - V_{BE} + V_{EE} \\ &= \frac{-V_{EE} R_1 - V_{BE} (R_1 + R_2) + V_{EE} (R_1 + R_2)}{(R_1 + R_2) R_3} \\ &= \frac{-V_{EE} R_1 - V_{BE} R_1 - V_{BE} R_2 + V_{EE} R_1 + V_{EE} R_2}{(R_1 + R_2) R_3} \\ &= \frac{-V_{BE} (R_1 + R_2) + V_{EE} R_2}{(R_1 + R_2) R_3} \end{aligned}$$

$$I_{E3} = I_{C3} = \frac{V_{EE} \left( \frac{R_2}{R_1 + R_2} \right) - V_{BE}}{R_3} \quad \text{--- (7)} \quad (\because I_{E3} \approx I_{C3})$$

Thus,  $V_{EE}$ ,  $R_1$ ,  $R_2$ ,  $R_3$  are constants, current  $I_{C3}$  almost equal to  $I_{E3}$  also constant. So, transistor Q<sub>3</sub> acts as constant current source.

### ii) current mirror circuit:-

The circuit in which the output current is forced to equal the input current is called as "current mirror circuit".


- In a current mirror circuit, the output current is the mirror image of input current.

To the emitter of  $Q_1$  and  
 $Q_2$  of differential Amplifier



$$I_{\text{source}} = I_{\text{sink}}$$

a) Block diagram

 

b) circuit diagram

The circuit consists of two matched transistors  $Q_3, Q_4$ .

$$\text{i.e. } V_{BE3} = V_{BE4}$$

$$I_{B3} = I_{B4}$$

$$\text{and } I_{C3} = I_{C4}$$

APPLY KCL at node 'A'

$$I_2 = I_{C4} + I \quad \text{--- (8)}$$

APPLY KCL at node 'B'

$$I = I_{B3} + I_{B4}$$

$$= 2I_{B3} = 2I_{B4} \quad \text{--- (9)} \quad (\because I_{B3} = I_{B4})$$

$$\text{From eq (8), } I_2 = I + I_{C4}$$

$$= 2I_{B4} + I_{C4} \quad (\text{or}) \quad 2I_{B3} + I_{C3} \quad \text{--- (10)}$$

$$\text{w.k.t } I_B = \frac{I_C}{\beta}$$

$$\text{so eq (10) becomes, } I_2 = 2\left(\frac{I_{C4}}{\beta}\right) + I_{C4}$$

$$I_2 = 2\left(\frac{I_{C3}}{\beta}\right) + I_{C3}$$

consider  $\frac{I_{C3}}{\beta}$  is very small value,

$$\Rightarrow I_A = I_{C3}$$

It indicates output current is equal to mirror current of Input.

APPLY KVL at transistor Q<sub>3</sub>,

$$-I_2 R_2 - V_{BE3} - (-V_{EE}) = 0$$

$$V_{EE} - V_{BE3} = I_2 R_2$$

$$\Rightarrow I_2 = \frac{V_{EE} - V_{BE3}}{R_2}$$


Level Translator :- (or) Level shift stage in op-Amp :-

As the coupling capacitors are not used to couple the amplifiers in the cascaded stage, Dc biasing voltage level propagates through the Amplifier chain. This finally appears as a significant d.c component at the output along with a.c output.


In presence of d.c component at output, there are some effects

 - i) The output gets distorted.
- ii) It limits the maximum output voltage swing.

The main purpose of the level shifting is to shift the output d.c level towards the ground, with minimum change in a.c signal.



a) output with zero D.C level

 

b) distorted output due to additional D.C level


circuit 1 :- simplest level shifting network (Emitter follower)

APPLY KVL

$$V_o = V_{in} - V_{BE}$$

$$(\because V_{in} = V_{BE} + V_o)$$


$$\therefore V_o = V_{in} - V_{BE}$$

 

In the circuit,  
The amount of shift obtained is equal to  $V_{BE}$  which is  
almost 0.7V.

circuit 2 :- (common collector stage)

 In Previous circuit, shift is 0.7V  
is not sufficient. hence the  
circuit is modified with help of  
2 resistances  $R_1$  and  $R_2$ .



It is a common collector stage, which also act as buffer  
to Isolate high gain stages from output stage.

APPLY KVL to Base-emitter Loop

$$V_{in} - V_{BE} - IR_1 - IR_2 = 0 \Rightarrow V_{in} - V_{BE} = I(R_1 + R_2)$$

$$I = \frac{V_{in} - V_{BE}}{R_1 + R_2} \quad \text{--- (2)}$$

$$\text{and } V_o = IR_2 \Rightarrow V_o = \left( \frac{V_{in} - V_{BE}}{R_1 + R_2} \right) R_2$$


→ The main drawback of this circuit is that signal voltage also attenuated by the factor  $\frac{R_2}{R_1 + R_2}$ .

Circuit 3 :- (constant current source)

In the above circuit, resistor  $R_2$  can be replaced by constant current source.

From the circuit,

$$V_o = V_{in} - V_{BE} - I_1 R_1 \quad \text{--- (3)}$$

 


Circuit 4 :- (current mirror circuit)

In current mirror circuit,

$$I_1 = I$$

$$\text{and } I_1 = I = \frac{V_{EE} - V_{BE}}{R_2}$$
 
$$\text{and } V_o = V_{in} - V_{BE} - I_1 R_1 \quad \text{--- (4)}$$



By choosing proper values of  $I, R_1$ , the output  $V_o$  can be zero level.

### Circuit 5 (multiplier circuit)

It is another level shifting network with  $V_{BE}$  multiplier circuit.

From figure,

$$V_{AB} = I(R_1 + R_2) \quad \text{--- (5)}$$

Apply KVL to Base emitter loop of  $\text{Q}_2$ ,

$$V_{BE} = IR_2 \Rightarrow I = \frac{V_{BE}}{R_2} \quad \text{--- (6)}$$

Substitute eq(6) in eq(5)

$$V_{AB} = \frac{V_{BE}}{R_2} (R_1 + R_2)$$

$$V_{AB} = V_{BE} \left( \frac{R_1}{R_2} + 1 \right) \quad \text{--- (7)}$$


and

$$V_o = V_{in} - V_{AB} - V_{BE}$$

$$= V_{in} - V_{BE} - \left[ V_{BE} \left( \frac{R_1}{R_2} + 1 \right) \right]$$

$$= V_{in} - V_{BE} \left[ 1 + \frac{R_1}{R_2} + 1 \right]$$

 
$$V_o = V_{in} - V_{BE} \left[ 2 + \frac{R_1}{R_2} \right]$$



By selecting proper values of  $R_1, R_2$  to adjust  $V_o$  to zero.
 
### Circuit 6 (PNP and NPN transistor combination)

In this level shifting network can be used for PNP and NPN transistors.



The output voltage  $V_O$  is given by

$$\boxed{V_O = \frac{R_2}{R_1} (V_{CC} - V_{BE} - V_{IN})}$$

## 2. Operational Amplifiers

An operational Amplifier is a direct coupled high-gain amplifier usually consisting of one (or) more differential amplifiers and usually followed by a level translator and output stage.

→ operational Amplifiers mainly 2 types

- i) open loop OP-AMPS
- ii) closed loop OP-AMPS

### i) open loop OP-AMPS :-

There is no feed back present, gain of the amplifier is high.


There are 3 open loop configurations

- i) differential Amplifier
- ii) Inverting Amplifier
- iii) Non-Inverting Amplifier

### i) differential Amplifier :-

'+' → Non-Inverting terminal

'-' → Inverting terminal

 

From the figure,


Input voltage  $V_1$  is applied to Non-Inverting terminal through the resistor  $R_1$ .

$V_2$  is connected to Inverting terminal through the resistor  $R_2$   
 differential voltage gain  $V_d = V_1 - V_2$

$$\text{output voltage, } V_o = A_d (V_1 - V_2)$$

 ii) Inverting Amplifier:-

In this configuration, Input  
 is applied to Inverting terminal  
 & Non Inverting terminal is connected  
 to ground i.e.  $V_1 = 0$




$$\text{w.k.t } V_o = A_d (V_1 - V_2)$$

$$= A_d (0 - V_2) \Rightarrow V_o = -A_d V_2$$

 iii) Non-Inverting amplifier :-

In this configuration,  
 Input is applied to Non-Inverting  
 terminal & Inverting terminal is  
 connected to ground i.e.  $V_2 = 0$



$$\text{w.k.t } V_o = A_d (V_1 - V_2)$$


$$= A_d (V_1 - 0)$$

$$V_o = A_d V_1$$

## 2. closed LOOP OP-AMP :-

In closed loop operation, the output is connected to Input is called feed back.

Generally -ve feed back is used.

 

In this fig,

some part of the output is given to Input, through the resistor is called feed back resistor.

### Advantages

- It stabilizes the gain
- Band width Increases
- Input and output resistances are changed
- Decreases Non-linear distortion.

## characteristics of operational Amplifiers :-

operational Amplifiers mainly 2 types

1. Ideal op-Amp
2. Practical op-Amp

### 1. Ideal op-Amp characteristics :-

1. infinite Input resistance
2. zero Output resistance
3. infinite Voltage gain

4. zero offset voltage
5. Infinite Band width
6. Infinite CMRR
7. Infinite slew rate
8. No effect to temperature

1. Infinite Input resistance ( $R_i = \infty$ ) :-

The input resistance is measured at either Inverting (or) Non-Inverting terminal with other terminal is grounded. In ideal OP-Amp the current at Inverting and Non-Inverting terminal is zero. There is no loading on preceding stage.

2. zero output resistance ( $R_o = 0$ ) :-

The output resistance is measured between output terminal and ground. Since  $R_o = 0$ , output of OP-Amp does not depend on current flows through it. Therefore, output can drive other devices.

3. Infinite voltage gain ( $A_{OL} = \infty$ ) :-

It is defined as the ratio of output voltage to the difference Input voltage. For, ideal OP-Amp the voltage gain is infinity.

#### 4. zero offset voltage ( $V_{ios} = 0$ ) :-

For an ideal OP-Amp, Input is zero ( $V_1 = V_2 = 0$ ), The output voltage also zero.

The presence of small output voltage through  $V_1 = V_2 = 0$  is called "offset".

#### 5. Infinite Band width ( $BW = \infty$ ) :-

Band width is nothing but difference between upper cut-off frequency and lower cut-off frequency.

The operating frequency range from 0 to  $\infty$ , so  $BW = \infty$ .

#### 6. Infinite CMRR ( $CMRR = \infty$ ) :-

CMRR is defined as the ratio of differential gain ( $A_d$ ) to common mode gain ( $A_c$ ).

$$CMRR = \frac{A_d}{A_c}$$

For Ideal OP-Amp,  $A_c = 0$   $\Rightarrow CMRR = \frac{A_d}{0} \Rightarrow CMRR = \infty$

#### 7. Infinite slew rate ( $s = \infty$ ) :-

Slew rate is defined as the "maximum rate of change of output voltage for each unit time".

$$S = \left. \frac{dV_o}{dt} \right|_{\max}$$


$\rightarrow$  Slew rate expressed in v/μs

$\rightarrow$  For Ideal OP-Amp, slew rate is infinite
 
## 8. No Effect to temperature :-

The characteristics of OP-Amp do not change with temperature.

The equivalent circuit of Ideal OP-Amp is shown in fig.



## Ideal voltage transfer curve :-

We know that, the output voltage is  $V_o = A_d V_d$


$$= A_d (V_1 - V_2)$$

The graph is drawn between output voltage  $V_o$ , Input voltage  $V_i$

keeping  $A_d$  is constant.

From the graph,

 output voltage cannot exceed the +ve and -ve saturation voltages.




because, the output voltage is directly proportional to difference of input voltages. So, output voltage reaches to saturation voltages, the output voltage remains constant.

The curve is called Ideal voltage transfer curve.

## 2. Practical OP-Amp :-

The equivalent circuit is shown in fig.

 

$$\text{The output voltage } V_o = A_d \cdot [V_1 - V_2]$$

Practical, OP-Amp characteristics

- i) Input resistance ( $R_i$ ) is  $2\text{M}\Omega$
- ii) Output resistance ( $R_o$ ) is  $75\Omega$
- iii) Open loop voltage gain ( $A_{OL}$ ) is  $2 \times 10^5$
- iv) Bandwidth is 1MHz
- v) CMRR is 90dB
- vi) Slew rate is  $0.5\text{ V}/\mu\text{sec}$

## Types of Integrated circuits :-

There are 2 types

- 1. Analog Integrated circuits
- 2. Digital Integrated circuits

### 1. Analog Integrated circuits :-

Integrated circuits that operate over an entire range of continuous values of signal Amplitude are called Analog Integrated circuits.

These are further classified into 2 types

1. Linear Integrated circuits

2. Radio frequency integrated circuits

i) Linear Integrated circuits:-

An Analog IC is said to be linear, if there exists a linear relation between its voltage and current.

Ex:- IC 741, 8-Pin Dual-In-Line package (DIP).

ii) Radio frequency Integrated circuits :-

An analog IC is said to be non linear, if there exists a non-linear relation between voltage and current.

2. Digital Integrated circuits:-


If the integrated circuits operates only at a few pre-defined levels instead of operating for an entire range of continuous values of signal amplitude, then these are called Digital Integrated circuits.

Ex:- logic gates, multiplexers, shift registers etc..

Classifications of Operational Amplifiers :-

## classifications of IC's :-

### i) Based on fabrication:-

 

### i) monolithic IC's:-

All the circuit components, both Active and passive elements are connected in a single chip of silicon.

→ The word 'monolithic' is originated from Greek word means 'single stone' (or) 'one stone'.

→ mainly used monolithic IC's because i) lower cost

ii) High reliability

→ Based on active devices used, monolithic IC's again classified into Bipolar and unipolar ICs.

Bipolar IC's uses BJT's and unipolar IC's use FET.

→ Depending upon Isolation technique, Bipolar IC's divided

into p-n junction Isolation ICs and dielectric Isolation ICs.

Q. Based on chip size and levels of Integration :-

chip development	chip size	Invented year	uses
1. Small scale Integration (SSI)	<100 active devices	1960	Integrated resistors, diodes, BJT's.
2. medium scale Integration (MSI)	100 - 1000 active devices	1965 - 1970	BJT's and Enhanced mosFETs
3. Large scale Integration (LSI)	1000 - 10,000 active devices	1970 - 1975	MOSFETs
4. Very Large scale Integration (VLSI)	>100000 active devices	1975	8-bit, 16-bit micro processors
5. ultra Large scale Integration (ULSI)	over 1 million active devices	-	Pentium microprocessors

3. Based on signal Processed :-

It can be 4 types

1. Digital Integrated circuits
2. Analog Integrated circuits
3. mixed- signal Integrated circuits
4. memory- Integrated circuits

1. Digital Integrated circuits :-

They perform mathematical calculations, flow of data and make decisions based on Boolean logic Principles (either logic '0' or logic '1')

Q. Based on chip size and levels of Integration :-

chip development	chip size	invented year	uses
1. Small Scale Integration (SSI)	<100 active devices	1960	Integrated resistors, diodes, BJTs.
2. medium Scale Integration (MSI)	100 - 1000 active devices	1965 - 1970	BJT's and Enhanced MOSFETs
3. Large Scale Integration (LSI)	1000 - 10,000 active devices	1970 - 1975	MOSFETs
4. Very Large scale Integration (VLSI)	>10000 active devices	1975	8-bit, 16-bit micro processors
5. Ultra Large Scale Integration (ULSI)	over 1 million active devices	-	Pentium microprocessors

3. Based on signal Processed :-

It can be 4 types

1. Digital Integrated Circuits
2. Analog Integrated Circuits
3. mixed-signal Integrated Circuits
4. memory- Integrated Circuits

1. Digital Integrated Circuits :-

They perform mathematical calculations, flow of data

and make decisions based on Boolean logic principles (either logic '0' or logic '1')

→ digital Integrated circuits mainly used in computers, cell phones, televisions.

→ It includes microprocessors, micro controllers, logic circuits.

## 2. Analog Integrated circuits:-

Analog Integrated circuits amplify, filter and modify electrical signals.

for ex, in cellular phones, they amplify and filter the incoming signal from the phone's antenna. The sound encoded into that signal has a low amplitude level; after the circuit filters the sound signal from incoming signal, the circuit amplifies sound signal and sends it to speaker in your cell phone, allowing you hear the voice on other end.

## 3. mixed signal circuits:-

In this type, to convert Analog signals to digital signals.

→ They convert analog voltage levels to digital number representation of voltage levels.

## 4. memory Integrated circuits:-


memory circuits perform calculations and to save the data (or) information.

→ Data it access → pictures, sound, text....

→ computer system may include 20 to 40 memory chips.

## IC Package types :-

### IC package types

 

#### i) metal can package :-

- The metal sealing plate is at the bottom over which the chip is bonded.
- The plane is effective for heat dissipation, hence this type used for power amplifiers.
- It also permits the External heat sink.
- It also called as "Transistor Pack"
- The available pins are 3, 5, 8, 10, 12 pins.

 


Fig :- TO-5 style package (6, 8, 10, 12 Lead)

#### ii) Dual-In-Line Package (DIP) :-

In this type, the chip is mounted Inside a plastic (or) ceramic case.

- It is easy to handle and most widely used.
- The 8-pin DIP is called mini DIP.

→ Available Pins are 12, 14, 16, 20.

 


Fig:- 14, 16, Lead version of DIP.

iii) Flat Pack:-

In this type the chip is enclosed in a rectangular ceramic case.

→ The terminals are taken out through the sides and ends.

→ The available Pins are 8, 10, 14, 16 leads.

 


Fig:- 10-Lead Version of Flat Package

### Selection of IC package :-

Type	Criteria
1. metal can package	i) Heat dissipation is important ii) Applications x) FOR High Power Amplifiers, Voltage regulators etc..
2. Dual InLine package (DIP)	i) For Experimental (or) bread boarding purposes ii) If bending (or) soldering of the leads is not required. iii) suitable for printed circuit boards.
3. Flat pack	i) more reliability is required ii) light in weight iii) suitable for airborne applications.

### Power supply :-


The op-Amp works on a dual supply. A dual supply consists of 2 supply voltages, they are +ve supply  $+V_{CC}$  and -ve supply  $-V_{EE}$ .

There are 2 types of dual supply

 - i) Balanced dual supply
- ii) unbalanced dual supply


→ In balanced dual supply,

Both power supply voltages are same in magnitude i.e  $+V_{CC} = +15V$ ,  $-V_{EE} = -15V$ .



Balanced dual Supply

 - In unbalanced dual supply, both supply voltages magnitudes are not equal.



- Practically in most of the op-amp circuits balanced power supply is used. and power supply ranges are  $\pm 9V$ ,  $\pm 12V$ ,  $\pm 22V$  etc..
- To avoid the use of 2 separate power supplies, a single power supply is used.
- There are various methods of obtaining dual supply from single supply.

i) From fig,

- Each positive and negative supply has equal magnitude i.e equal to half of the single supply voltage used ( $\frac{V_{in}}{2}$ ).

 


Fig:- obtaining dual supply from Single supply

- capacitors used to supply bypassing i.e decoupling of power supply.
- Resistors should not draw high current from supply hence the values more than  $10k\Omega$ .

→ If the voltages required are other than  $\frac{V_{in}}{2}$  then zener diodes are used for appropriate voltage rating.

 


Fig :- use of zener diodes

→ many times practically due to mismatch in the devices, equal +ve and -ve voltages are not available. To adjust them we are using Potentiometer.

→ To avoid damage due to reversal of polarities connected to IC, diodes D<sub>1</sub>, D<sub>2</sub> used.

 


Fig :- use of Potentiometer


### Temperature ranges :-

There are 3 different temperature ranges

 - i) military temperature range → -55°C to +125°C (-55°C to +85°C)
- ii) Industrial temperature range → -20°C to +85°C (-40°C to +85°C)
- iii) commercial temperature range → 0°C to 70°C (0°F to +75°F)

Block diagram representation of OP-Amp :-

OP-AMPS usually consists of 4 cascaded blocks.



### I. Input stage:-

- In this stage using dual input balanced output differential amplifier circuit. i.e we are giving 2 Inputs and produces 2 outputs.
- The function of differential Amplifier is used to Amplify the difference between 2 Input signals.
- High Input Impedance (or) high Input resistance is required and low output resistance is required.
- In this stage 2 Inputs are required they are Inverting & Non-Inverting terminals.
  - In the Inverting terminal (-) It requires  $180^\circ$  phase shift between Input and output.
  - In the Non-Inverting terminal (+), no phase shift is required between Input and output.

## 2. Intermediate stage :-

The output of the Input stages drives the next stage which is an intermediate stage.

- This stage is similar to dual input, unbalanced output i.e we are giving 2 inputs and produce single output.
- The main function of this stage is used to Increases the gain value.
- Practically, the intermediate stage is not a single amplifier it contains cascaded Amplifiers called multi stage Amplifiers.

### Note :-

The concept of Intermediate stage is similar to the operation of cascaded differential amplifier stages in unit-1.

## 3. Level shifting stage:-

All the stages are directly coupled to each other.

The coupling capacitors are not used to cascade the stages.

Hence the d.c. avuiесcent voltage level of previous stage gets applied to input to next stage. Hence stage by stage d.c. level increases. As the d.c. level increases, it causes distortion in the output due to clipping. This may limit the maximum A.c. output voltage swing without any distortion.

- The Level shifter stage brings the d.c level down to ground potential, when no signal is applied at the input.
- The buffer is usually an Emitter follower whose Input Impedance is very high.

Note:-

level shifting stage operation is similar to D.c translator operation in unit-1.

#### 4. output stage:-

- The basic requirement of output stage is low output resistance
- The Push-pull complementary Amplifier used an output stage.
- This stage Increases the output voltage swing and keeps the voltage swing symmetrical with respect to ground.
- The requirements of good output stage are
  - i) Large output voltage, current swing capability
  - ii) Low output Impedance
  - iii) Low Quiescent power dissipation
  - iv) short circuit protection

consider Push-Pull Amplifier in class B, which is basically Emitter-follower with complementary transistors.

 
 


Fig:- output stage of an OP-Amp

- when  $V_{in}$  is +ve, transistor  $Q_1$  ON,  $Q_2$  OFF.  
 $Q_1$  supplies the load.
- when  $V_{in}$  is -ve,  $Q_1$  OFF,  $Q_2$  ON.  $Q_2$  act as sink to remove the current from the load.
- major limitation of the circuit is output voltage remains zero as  $V_{in}$  is less than  $V_{BE}$ . This introduces the cross-over distortion in the output.

 


Fig:- cross over distortion in the output

## characteristics and performance specifications of OP-AMP :-


### i) Input offset voltage :-

when ever both input terminals of the OP-amp are grounded, ideally the output voltage is zero but practically it has non-zero output voltage. This is due to mismatching present in the Internal circuit of OP-amp.


Def:-

The differential voltage that must be applied between 2 input terminals of the OP-AMP, to make the output voltage zero is called "Input offset voltage".

 - It is denoted as  $V_{ios}$
- practically for OP-amp 741C, the Input offset voltage is 6mV.
- Ideally,  $V_{ios}$  is zero



### ii) Input offset current :-

 

def :- The algebraic difference between the currents flowing into the two Input terminals of the op-amp is called "Input offset current".

→ It is denoted by  $I_{ios}$

→ mathematically,

$$I_{ios} = |I_{b1} - I_{b2}|$$

where,  $I_{b1}$  → current entering into Non Inverting Input terminal

$I_{b2}$  → current entering into Inverting Input terminal

→ Practically,  $I_{ios}$  value is 200 nA.

→ Ideally,  $I_{ios}$  is zero.

3. Input bias current :-

It is defined as the,

The Average value of two currents

flowing into the op-amp input terminals is called "Input bias current".


→ It is denoted as  $I_b$ .

mathematically,

$$I_b = \frac{I_{b1} + I_{b2}}{2}$$

→ Ideally it should be zero, practically for op-amp 741C, is

500 nA.

 

#### 4. Differential Input resistance :- (or) Input resistance :- ( $R_i$ )

It is the equivalent resistance measured at either the Inverting (or) Non-Inverting terminal with other input terminal <sup>Input</sup> <sub>x</sub> grounded.

- It is denoted as  $R_i$ ;
- Ideally, it should be Infinite value
- Practically, opamp 741C is order of  $2\text{M}\Omega$ .

#### 5. Input capacitance :- ( $C_i$ )

It is the equivalent capacitance measured at either the Inverting (or) Non-Inverting terminal with other input terminal <sup>Input</sup> <sub>x</sub> grounded.

- It is denoted as  $C_i$ ;
- Practically, for op-amp 741C, it is  $1-4\text{PF}$ .

#### 6. Open Loop Voltage Gain :- (or) Large signal voltage gain ( $A_{OL}$ ) :-

It is defined as the ratio of output voltage to the differential input voltage, when op-amp is in open loop configuration without any feed back.

$$A_{OL} = \frac{V_o}{V_d}$$

- For opamp 741C, it is typically  $2,00,000$ .


### 7. CMRR :-

It is the ratio of differential voltage gain ( $A_d$ ) to the common mode voltage gain ( $A_c$ ).

$$\boxed{\text{CMRR} = \frac{A_d}{A_c}}$$

$A_d$  is nothing but open loop voltage gain  $A_{OL}$  &  $A_c$  is measured by using the circuit as shown in fig.

 From fig,  
common mode input  $V_c$  is applied to both Input terminals,  
output  $V_{oc}$  is measured.



Then, common mode gain  $\boxed{A_c = \frac{V_{oc}}{V_c}}$

- It is expressed in dB
- For op-amp 741C it is 90dB.

### 8. Output voltage swing :-

The op-amp output voltage gets saturated at  $+V_{cc}$  and  $-V_{ee}$  and it can not produce output voltage more than  $+V_{cc}$  and  $-V_{ee}$ .

- Practically, saturation voltages  $+V_{sat}$  and  $-V_{sat}$  are less than  $+V_{cc}$  and  $-V_{ee}$ .
- For op-amp 741C, the saturation voltages are  $\pm 13V$  for supply voltages  $\pm 15V$ .

### 9. Output resistance :-

It is the equivalent resistance measured between the output terminal of the op-amp and the ground.

→ It is denoted as  $R_o$


→ For op-amp 741C it is  $75\Omega$

### 10. Offset voltage adjustment range :-

→ The pins 1 and 5 are offset null pins for op-amp 741.

→ A  $10k\Omega$  Potentiometer can be connected to pin 1 and pin 5.

 → The variable end of Potentiometer is connected to  $-V_{EE}$ . By varying Potentiometer, the output can be adjusted to zero.



def :- "The range for which input offset voltage can be adjusted using the potentiometer to reduce output to zero", is called offset voltage adjustment range.

→ For op-amp 741C, it is  $\pm 15mV$ .

### 11. Input voltage range :-


It is the range of common mode voltages which can be applied for which op-amp functions properly.

→ This range also dependent on supply voltages.

→ For op-amp 741C,  $\pm 15V$  supply voltages, Input voltage range is  $\pm 13V$ .
 
### 12. Power Supply Rejection Ratio (PSRR) :-

It is defined as the "Ratio of change in input offset voltage due to change in supply voltage producing it, keeping other power supply voltage constant."



→ It is also called as power supply sensitivity (PSV)

i) If V<sub>EE</sub> is constant, V<sub>cc</sub> is fixed then

$$\boxed{PSRR = \frac{\Delta V_{ios}}{\Delta V_{cc}} \Big|_{V_{EE}=\text{constant}}}$$

ii) If V<sub>cc</sub> is constant, V<sub>EE</sub> is fixed then

$$\boxed{PSRR = \frac{\Delta V_{ios}}{\Delta V_{EE}} \Big|_{V_{cc}=\text{constant}}}$$

→ PSRR is expressed in mV/V (or)  $\mu\text{V}/\text{V}$

→ For IC 741 op-amp, PSRR is  $30\mu\text{V}/\text{V}$ .

→ It is also called as supply voltage rejection ratio (SVRR).

### 13. Power consumption :- (P<sub>c</sub>)

It is the amount of quiescent power to be consumed by op-amp with zero input voltage.

→ For op-amp 741C, it is  $85\text{mW}$ .

#### 14. Slew rate :-

It is defined as the maximum rate of change of output voltage with time.

$$\text{slew rate } (S) = \left. \frac{dV_o}{dt} \right|_{\text{max}} \quad \text{--- (1)}$$

→ slew rate is specified in  $V/\mu\text{sec}$

→ It is specified by the op-amp in unity gain condition.

→ The slew rate is caused due to limited charging rate of the compensation capacitor and current limiting and saturation of the internal stages of op-amp, when a high frequency large amplitude signal is applied.

The internal capacitor voltage can not change instantaneously

It is given by  $\frac{dV_o}{dt} = \frac{I}{C} \quad \text{--- (2)}$

$$\left[ \because V_o = \frac{1}{C} \int i dt \right]$$

$$\frac{dV_o}{dt} = \frac{i}{C}$$

From eq (2), small value of 'C', current value large.

$$\therefore S = \frac{I_{\text{max}}}{C}$$

For IC741,

The charging current is 15mA and the internal capacitor is 30PF.  $S = 0.5 V/\mu\text{sec}$

### Slew rate equation :-

$$\text{consider } V_S = V_m \sin \omega t$$

$$V_O = V_m \sin \omega t$$

$$\frac{dV_O}{dt} = V_m \omega \cos \omega t$$

$$\text{slew rate (s)} = \left. \frac{dV_O}{dt} \right|_{\text{max}}$$

$$S = V_m \omega \quad [\because \text{for max, } \cos \omega t = 1]$$

$$S = 2\pi f V_m \text{ V/sec} \quad \text{---(3)}$$

For distortion free output, the max. allowable input frequency  $f_m$ ,

from eq (3), 
$$f_m = \frac{S}{2\pi V_m}$$

### 15. Gain-Band width product :-


It is the band width of op-amp when voltage gain is unity.

It is denoted as GB.

→ Gain is Expressed in dB, so unity gain has dB value  $20 \log 1 = 0 \text{dB}$

→ It also called unity gain bandwidth (UGB) (or) closed loop

bandwidth.

 

From the graph, gain reduces, frequency Increases.

#### 16. Equivalent Input noise voltage and current :-

The Noise is random in nature, hence it expressed as a power density.

→ The equivalent Noise voltage is expressed as  $V^2/Hz$ , equivalent noise current is expressed as  $A^2/Hz$ .

#### 17. Average temperature coefficient of offset Parameters :-

→ The Average rate of change of Input offset voltage per unit change in temperature is called Average temperature coefficient of input offset voltage (or) Input offset voltage drift.

→ It is measured in  $mV/^\circ C$ . For 741C it is  $0.5 mV/^\circ C$

→ The average rate of change of Input offset current per unit change in temperature is called Average temperature coefficient of Input offset current (or) Input offset current drift.

→ It is measured in  $nA/^\circ C$  (or)  $PA/^\circ C$ . For 741C it is  $12 PA/^\circ C$

#### 18. Output offset voltage ( $V_{OOS}$ ) :-

The output offset Voltage is the dc voltage present at the output terminals when both the Input terminals are grounded.

→ It is denoted as  $V_{OOS}$ .

#### 19. Supply current:-

It is the current drawn by the OP-amp from the power supply.

→ For OP-amp 741C it is 2.8 mA

#### Transient response Rise time :-

When the output of the OP-amp is suddenly changing like pulse type, then rise time of the response depends on the cut-off frequency  $f_H$  of the OP-amp. Such rise time is called cut-off frequency limited risetime (or) transient response rise time.

$$t_R = \frac{0.35}{f_H}$$

#### D.c characteristics of OP-Amp :-

The Important d.c characteristics are

- i) Input bias current ( $I_b$ )
- ii) Input offset current ( $I_{ios}$ )
- iii) Input offset voltage ( $V_{ios}$ )
- iv) Thermal drift

#### 4. Thermal drift:-

The OP-amp parameters input offset current, Input offset voltage, Input bias current are not constant but vary with the factors : i) Temperature ii) change in supply

Voltage    iii) Time

The effect of change in temperature on the parameters is most severe.

### ii) Effect on Input offset voltage :-

It is defined as the average rate of change of input offset voltage per unit change in temperature.

→ It is also called as Input offset voltage drift.

$$\text{Input offset voltage drift} = \frac{\Delta V_{ios}}{\Delta T}$$

where,


$\Delta V_{ios}$  → change in Input offset voltage

$\Delta T$  → change in temperature

→ It is expressed in  $\mu\text{V}/^\circ\text{C}$ .

→ The drift is not constant and it is not uniform over specified operating temperature range.

 → The value of Input offset voltage may increase (or) decrease with increasing temperature.



### ii) Effect on Input bias current drift :-

It is defined as the average rate of change of Input bias current per unit change in temperature.


$$\text{Thermal drift in Input bias current} = \frac{\Delta I_b}{\Delta T}$$

→ It is measured in nA/°C (or) pA/°C

→ These parameters vary randomly with temperature i.e. they

may be +ve in one temperature

range and -ve in other temperature range

 

### iii) Effect on Input offset current drift :-


It is defined as the average rate of change of Input offset current per unit change in temperature.

$$\text{Thermal drift in Input offset current} = \frac{\Delta I_{ios}}{\Delta T}$$

→ It is measured in nA/°C  
(or) pA/°C

→ These parameters vary randomly with temperature i.e. they may be +ve in

one temperature range and -ve in other.

 

## A.C characteristics :-

mainly there are

1. Frequency response
2. Slew rate
3. Stability of an op-amp


### 1. Frequency response :-

Ideally, an op-amp should have infinite bandwidth but practically, op-amp gain decreases with increase in temperature such a gain reduction with respect to frequency is called roll off.

- The plot showing the variations in magnitude and phase angle of the gain due to change in frequency is called frequency response of op-amp.
- when the gain in decibels (dB), phase angle in degrees are plotted against logarithmic scale of frequency, the plot is called "Bode plot".
- Gain of the op-amp changes with variation in frequency is called "magnitude plot".
- Phase shift changes with change in frequency is called "phase angle plot".

obtaining frequency response :-

 To obtain frequency response, consider the high frequency model of op-amp with capacitor 'c' at the output.



Let  $-jx_c$  be the capacitive reactance.

using voltage divider rule,

$$V_0 = \frac{-jx_c}{R_o - jx_c} \cdot A_{OL} V_d$$

$$\text{Let } -j = \frac{1}{j}, \quad x_c = \frac{1}{2\pi f c}$$

$$\Rightarrow V_0 = \frac{\frac{1}{j2\pi f c}}{R_o + \frac{1}{j2\pi f c}} \cdot A_{OL} V_d$$

$$\Rightarrow V_0 = \frac{1}{R_o(j2\pi f c) + 1} \cdot A_{OL} V_d$$

$$\Rightarrow \frac{V_0}{V_d} = \frac{A_{OL}}{1 + j2\pi f R_o c}$$

$$\Rightarrow \boxed{A_{OL}(f) = \frac{A_{OL}}{1 + j2\pi f R_o c}} \quad -①$$

$$\text{consider } f_o = \frac{1}{2\pi R_o c}$$

$$\Rightarrow \boxed{A_{OL}(f) = \frac{A_{OL}}{1 + j(f/f_o)}} \quad -②$$

#### 19. Supply current:-

It is the current drawn by the OP-amp from the power supply.

→ For OP-amp 741C it is 2.8 mA

#### Transient response Rise time :-

When the output of the OP-amp is suddenly changing like pulse type, then rise time of the response depends on the cut-off frequency  $f_H$  of the OP-amp. Such rise time is called cut-off frequency limited risetime (or) transient response rise time.

$$t_R = \frac{0.35}{f_H}$$

#### D.c characteristics of OP-Amp :-

The Important d.c characteristics are

- i) Input bias current ( $I_b$ )
- ii) Input offset current ( $I_{ios}$ )
- iii) Input offset voltage ( $V_{ios}$ )
- iv) Thermal drift

#### 4. Thermal drift:-

The OP-amp parameters input offset current, Input offset voltage, Input bias current are not constant but vary with the factors : i) Temperature ii) change in supply

Voltage    iii) Time

The effect of change in temperature on the parameters is most severe.

### ii) Effect on Input offset voltage :-

It is defined as the average rate of change of input offset voltage per unit change in temperature.

→ It is also called as Input offset voltage drift.

$$\text{Input offset voltage drift} = \frac{\Delta V_{ios}}{\Delta T}$$

where,


$\Delta V_{ios}$  → change in Input offset voltage

$\Delta T$  → change in temperature

→ It is expressed in  $\mu\text{V}/^\circ\text{C}$ .

→ The drift is not constant and it is not uniform over specified operating temperature range.

 → The value of Input offset voltage may increase (or) decrease with increasing temperature.



### ii) Effect on Input bias current drift :-

It is defined as the average rate of change of Input bias current per unit change in temperature.


$$\text{Thermal drift in Input bias current} = \frac{\Delta I_b}{\Delta T}$$

→ It is measured in nA/°C (or) pA/°C

→ These parameters vary randomly with temperature i.e. they

may be +ve in one temperature

range and -ve in other temperature range

 

### iii) Effect on Input offset current drift :-


It is defined as the average rate of change of Input offset current per unit change in temperature.

$$\text{Thermal drift in Input offset current} = \frac{\Delta I_{ios}}{\Delta T}$$

→ It is measured in nA/°C  
(or) pA/°C

→ These parameters vary randomly with temperature i.e. they may be +ve in

one temperature range and -ve in other.

 

## A.C characteristics :-

mainly there are

1. Frequency response
2. slew rate
3. stability of an op-amp


### 1. Frequency response :-

Ideally, an op-amp should have infinite bandwidth but practically, op-amp gain decreases with increase in temperature such a gain reduction with respect to frequency is called roll off.

- The plot showing the variations in magnitude and phase angle of the gain due to change in frequency is called frequency response of op-amp.
- when the gain in decibels (dB), phase angle in degrees are plotted against logarithmic scale of frequency, the plot is called "Bode plot".
- Gain of the op-amp changes with variation in frequency is called "magnitude plot".
- Phase shift changes with change in frequency is called "phase angle plot".

obtaining frequency response :-

 To obtain frequency response, consider the high frequency model of op-amp with capacitor 'c' at the output.



Let  $-jx_c$  be the capacitive reactance.

using voltage divider rule,

$$V_0 = \frac{-jx_c}{R_o - jx_c} \cdot A_{OL} V_d$$

$$\text{Let } -j = \frac{1}{j}, \quad x_c = \frac{1}{2\pi f c}$$

$$\Rightarrow V_0 = \frac{\frac{1}{j2\pi f c}}{R_o + \frac{1}{j2\pi f c}} \cdot A_{OL} V_d$$

$$\Rightarrow V_0 = \frac{1}{R_o(j2\pi f c) + 1} \cdot A_{OL} V_d$$

$$\Rightarrow \frac{V_0}{V_d} = \frac{A_{OL}}{1 + j2\pi f R_o c}$$

$$\Rightarrow \boxed{A_{OL}(f) = \frac{A_{OL}}{1 + j2\pi f R_o c}} \quad -①$$

$$\text{consider } f_o = \frac{1}{2\pi R_o c}$$

$$\Rightarrow \boxed{A_{OL}(f) = \frac{A_{OL}}{1 + j(f/f_o)}} \quad -②$$

where,

$A_{OL}(f)$  = open loop voltage gain as a function of frequency

$A_{OL}$  = Gain of the OP-Amp

$f$  = operating frequency

$f_0$  = Break frequency (or) cut-off frequency

eq② can be written in magnitude and Polar form,

$$\text{i.e. magnitude} \rightarrow |A_{OL}(f)| = \frac{A_{OL}}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}}$$

$$\text{phase angle} \rightarrow \angle A_{OL}(f) = \phi(f) = -\tan^{-1}\left(\frac{f}{f_0}\right)$$


FOR IC741 OP-Amp,

$f_0 = 5\text{Hz}$ , open loop gain 2,00,000 calculate magnitude


and phase shifts at various frequencies as show in table

below.

frequency in Hz	$ A_{OL}(f)  = 20 \log \frac{A_{OL}}{\sqrt{1 + (f/f_0)^2}}$ in decibels (dB)	$\phi(f) = -\tan^{-1}\left(\frac{f}{f_0}\right)$ in degrees
0	106.02 dB	$0^\circ$
5	103.01 dB	$-45^\circ$
10	99.03 dB	$-63.43^\circ$
100	79.98 dB	$-87.13^\circ$
1000	60.00 dB	$-89.71^\circ$
$100 \times 10^3$	20 dB	$-89.99^\circ$
$1 \times 10^6$	0 dB	$-89.999^\circ$

 

a) magnitude characteristics

 

b) phase characteristics

From the graph


- i) open loop gain  $A_{OL}$  is constant from 0Hz to break freq.  $f_0$
- ii) At  $f=f_0$ , gain is 3dB down from its value at 0Hz.  
Hence  $f_0$  is also called -3dB frequency (or) corner frequency
- iii) After  $f=f_0$ , gain decreases, slope of the magnitude plot is  $-20\text{dB/decade}$  (or)  $-6\text{dB/octave}$ , after  $f=f_0$ .
- iv) At certain frequency, gain reduces to 0dB. i.e  $20 \log |A_{OL}|$  is 0dB i.e  $|A_{OL}|=1$ . Such frequency is called gain cross-over frequency (or) unity gain bandwidth (UGB) (or) closed loop bandwidth.

## 2. slew rate :-

\*Note :- Previously discussed to refer that.
 
### 3. Stability of an OP-amp :-

consider non Inverting amplifier with resistive feed back as shown in fig.



a) Non Inverting Amplifier

→ The block between Input and output is called forward block.

→ The block between output signal and feed back is called feed back block.

 


Fig:- Block diagram of Non-Inverting Amplifier

$$\text{From fig, } X = V_{in} - \beta V_o \quad \text{--- ①}$$

$$\text{and } V_o = X [A_{OL}(f)]$$

$$\Rightarrow X = \frac{V_o}{A_{OL}(f)} \quad \text{--- ②}$$

Sub. eq ② in ①

$$\Rightarrow \frac{V_o}{A_{OL}(f)} = V_{in} - \beta V_o$$

$$\Rightarrow \frac{V_o}{A_{OL}(f)} + \beta V_o = V_{in} \Rightarrow V_o \left[ \frac{1}{A_{OL}(f)} + \beta \right] = V_{in}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{A_{OL}(f)}{1 + A_{OL}(f)\beta} \quad \text{--- (3)}$$

or (3) called closed loop gain.

$$\left\{ \begin{array}{l} \because \frac{V_o}{V_{in}} = \frac{1}{A_{OL}(f)} + \beta \\ = \frac{1 + \beta A_{OL}(f)}{A_{OL}(f)} \end{array} \right.$$

The characteristic equation of system is given by

$$1 + A_{OL}(f)\beta = 0$$

$$\Rightarrow A_{OL}(f)\beta = -1 \quad \text{--- (4)}$$

or (4) expressed in complex form as

$$A_{OL}(f)\beta = -1 + j \cdot 0 \quad \text{--- (5)}$$

The magnitude and phase angles given by

$$|A_{OL}(f)\beta| = \sqrt{1^2 + 0^2}$$

$$\Rightarrow |A_{OL}(f)\beta| = 1 \quad \text{--- (6)}$$

$$\text{and } \angle A_{OL}(f)\beta = \tan^{-1}\left(\frac{0}{1}\right)$$

$$= 0^\circ \text{ (or) } 0\pi \text{ radians.} \quad \text{--- (7)}$$

or (6), (7) are called Barkhausen criterion for the sustained oscillations.

Stability specifications :-

i) Gain cross over frequency ( $\omega_{gc}$ ) :-

The frequency at which the loop gain magnitude  $|A_{OL}(f)\beta| = 1$  i.e.  $20 \log |A_{OL}(f)\beta| = 0 \text{ dB}$  is called gain cross over frequency.

ii) Phase cross over frequency ( $\omega_{pc}$ ):-

The frequency at which the phase shift introduced by the loop gain is  $-180^\circ$  (or)  $n\pi$  radians is called phase cross over frequency.

iii) Gain margin (G.m):-

The gain measured at the frequency  $\omega = \omega_{pc}$  is called gain margin. So, loop gain  $|A_{OL}(f)\beta|$  measured at  $\omega = \omega_{pc}$  mathematically,

$$G.m = -20 \log |A_{OL}(f)\beta|_{\omega=\omega_{pc}} \text{ dB}$$

iv) Phase margin (P.m):-

The amount by which angle of loop gain  $L A_{OL}(f)\beta$  differ from the  $-180^\circ$  phase shift, at  $\omega = \omega_{gc}$  is called phase margin. mathematically

$$P.m = 180^\circ + L A_{OL}(f)\beta|_{\omega=\omega_{gc}}$$

 


Fig:- freq. response of stable op-amp

## Measurement techniques of op-amp parameters

### 1. measurement of open loop voltage gain ( $A_{OL}$ ) :-

It is defined as the ratio of output voltage to the input differential voltage.

→ It is normally specified at a.c with an output voltage swing of  $\pm 10V$  across the load, with the amplifier working at  $\pm 15V$  Power supply.

 


Fig:- measurement of open loop voltage gain

→ The source signal is attenuated by 40dB i.e reduced by  $\frac{1}{100}$  before applying  $V_S$ , the output offset voltage is compensated using resistive network connected to non Inverting input terminal.

From fig,

$$A_{OL} = \frac{V_o}{V_{in}}$$

## 2. measurement of Input bias current :-

It is defined as the Average of currents that flow into Inverting and Non Inverting terminals of the OP-amp.

$$I_b = \frac{I_{b1} + I_{b2}}{2}$$

- The OP-amp is used in the closed loop configuration
- The 2-Input currents  $I_{b1}$  and  $I_{b2}$  flowing through resistances like  $7.2\text{ m}\Omega$ .
- The capacitors used to eliminates noise.

The steps used for the measurements are

### 1. short A and B :-

due to this, A gets grounded.

Now  $I_{b1}$  flows through resistance R, output voltage is  $V_{o1}$ .

$$\Rightarrow V_{o1} = I_{b1} R$$

$$I_{b1} = \frac{V_{o1}}{R}$$

### 2. short C and D :-

In this case  $I_{b2}$  flows through resistor R, output voltage is  $V_{o2}$ .

$$\Rightarrow V_{o2} = I_{b2} R \Rightarrow I_{b2} = \frac{V_{o2}}{R}$$

 


Fig:- measurement of Input bias current

### 3. measurement of Input offset current :-

It is defined as the difference between 2 currents flows through it.

$$I_{ios} = |I_{b1} - I_{b2}|$$

Note:- The circuit and measurement is similar to Input bias current.

### 4. measurement of Input offset voltage and PSRR :-

It is defined as the voltage applied between Input terminals to get zero output voltage.

 


Fig:- measurement of  $V_{ios}$  and PSRR

The OP-amp is dual supply is adjusted to exact  $\pm 10V$ .

The Potentio meter is used to adjust output voltage to zero.

From fig,  $I = \frac{V_E}{1k\Omega + 1\Omega} \approx \frac{V_E}{1000}$

and  $V_A = I \times 1\Omega = \frac{V_E}{1000}$

Input offset voltage applied to Non-Inverting terminal to get zero output.

$$\therefore V_{ios} = V_A = \frac{V_E}{1000}$$

→ same circuit is used to measure PSRR. (Power supply rejection ratio)

It is defined as the ratio of change in input offset voltage to change in supply voltage by keeping other supply as constant.

$$\text{i.e. } PSRR = \left| \frac{\Delta V_{ios}}{\Delta V_{cc}} \right| \quad | V_{EE} = \text{const.}$$

(or)

$$PSRR = \left| \frac{\Delta V_{ios}}{\Delta V_{EE}} \right| \quad | V_{cc} = \text{constant}$$

→ From fig, supply is  $\pm 10V$

i)  $-10V$  is constant ( $V_{EE}$ ):

In this case  $+V_{cc}$  changed to  $+9V$  from  $+10V$ . again  $V_E$  adjusted to get output voltage as zero, corresponding  $V_A$  measured which is considered as  $V_{ios1}$ . Then  $+V_{cc}$  changed to  $+11V$  again  $V_E$  adjusted to get output voltage to zero. corresponding  $V_A$  is  $V_{ios2}$ .

Then PSRR,

$$PSRR = \frac{\Delta V_{ios}}{\Delta V_{cc}} = \frac{V_{ios2} - V_{ios1}}{11 - 9} = \frac{V_{ios2} - V_{ios1}}{2}$$

ii)  $+10V$  is constant ( $V_{cc}$ ): change  $V_{EE}$  from  $-9$  to  $-11V$  and measure  $V_A$ .

PSRR corresponding to -ve supply can be measured.

### 5. measurement of CMRR :-

It is defined as the ratio of differential gain to common mode gain.

→ The common mode signal  $V_S$  is applied to both Inputs.

$$\text{i.e } A_C = \frac{V_o}{V_S}$$

$$\text{and } V_d = V_B - V_A \quad \text{--- (1)}$$

 


Fig :- measurement of CMRR

Now

$$V_B = \frac{V_S \cdot R_1}{R_1 + R_f} \quad \text{--- (2)}$$

To calculate  $V_A$ , use superposition principle, as  $V_A$  due to 2 voltages  $V_S$  and  $V_o$ .

$$\underline{V_o \text{ grounding}} \rightarrow V_{A1} = \frac{R_f}{R_1 + R_f} \cdot V_S$$

$$\underline{R_1 \text{ as grounding}} \rightarrow V_{A2} = \frac{R_1}{R_1 + R_f} \cdot V_o$$

$$\Rightarrow V_A = V_{A1} + V_{A2}$$

$$= \frac{R_f V_S}{R_1 + R_f} + \frac{R_1 V_o}{R_1 + R_f} \quad \text{--- (3)}$$

substitute eq (2), (3) in (1)

$$\Rightarrow V_d = \frac{V_S R_1}{R_1 + R_f} - \frac{R_f V_S}{R_1 + R_f} - \frac{R_1 V_o}{R_1 + R_f}$$

$$\Rightarrow V_d = \frac{V_s R_f - V_s R_f - V_o R_1}{R_1 + R_f}$$

$$\Rightarrow V_d = -\frac{V_o R_1}{R_1 + R_f} \Rightarrow \frac{V_d}{V_o} = -\frac{R_1}{R_1 + R_f}$$

$$\Rightarrow \frac{V_o}{V_d} = -\frac{R_1 + R_f}{R_1}$$

$$\Rightarrow A_d = -\left[1 + \frac{R_f}{R_1}\right]$$


By knowing values of  $R_1, R_f$ , magnitude of  $A_d$  can be obtained.

Hence, CMRR can be measured as

$$\boxed{\text{CMRR} = \frac{|A_d|}{|A_c|}}$$
 
#### 6. measurement of output offset voltage :-

It is defined as the difference between d.c voltage present at the output terminals when both input terminals are grounded.



From fig,

output voltage due to

$I_{b2}$  is,

$$V_{o1} = I_{b2} R_1 \left( -\frac{R_f}{R_1} \right) \quad \text{--- (1)}$$

output voltage due to  $I_{b1}$  is,

$$V_{o2} = I_{b1} R_C \left( 1 + \frac{R_f}{R_1} \right)$$

Fig i - measurement of output offset voltage

Practically,  $R_c$  is selected equal to  $R_i$

$$\Rightarrow V_{o2} = I_{b1}(R_i + R_f) \quad \text{--- (2)}$$

From eq (1), (2)

$$V_{o1} + V_{o2} = -I_{b2}R_f + I_{b1}R_i + I_{b1}R_f$$

consider  $R_i \ll R_f$ , neglect  $I_{b1}R_i$  term

$$= -I_{b2}R_f + I_{b1}R_f$$

$$= R_f(I_{b1} - I_{b2}) = R_f \cdot I_{ios}$$

where  $I_{ios}$  is the magnitude of difference between 2 I/P currents.

while output voltage due to Input offset voltage is given by

$$V_{ios} \left(1 + \frac{R_f}{R_i}\right).$$

Total output offset voltage is given by

$$V_{oos} = V_{ios} \left(1 + \frac{R_f}{R_i}\right) + I_{ios} R_f$$

The voltage may be +ve (or) -ve

### Frequency compensation techniques :-

The OP-amp circuit with single break (or) corner frequency is inherently stable.


consider the system with three break (or) corner frequencies. This is possible in practice due to capacitive

component produced by no. of stages.

The open-loop transfer function is given by

$$A_{OL}(f) = \frac{A_{OL}}{\left[1+j\left(\frac{f}{f_1}\right)\right]\left[1+j\left(\frac{f}{f_2}\right)\right]\left[1+j\left(\frac{f}{f_3}\right)\right]} ; 0 < f_1 < f_2 < f_3$$

Frequency compensation techniques

 


### 1. External compensation :-

The compensating network is connected to the system externally.
 
### ii) Dominant pole compensation :-

The compensated

transfer function  $A' = \frac{V_o}{V_i}$



$$= \frac{-jX_C}{R-jX_C} \cdot A$$

$$= \frac{\frac{1}{j2\pi f_C}}{R + \frac{1}{j2\pi f_C}} \cdot A$$

$$\left[ \begin{array}{l} \therefore -j = \frac{1}{j} \\ X_C = \frac{1}{2\pi f_C} \end{array} \right]$$

$$A' = \frac{\frac{1}{j2\pi f_c}}{\frac{R(j2\pi f_c) + 1}{j2\pi f_c}} \cdot A$$

$$= \frac{1}{1 + j2\pi f_c R C} \cdot A$$


$$\Rightarrow \boxed{A' = \frac{A}{1 + j\left(\frac{f}{f_d}\right)}} \quad (\because \text{consider } f_d = \frac{1}{2\pi R C})$$

$f_d \rightarrow$  break frequency (or) corner frequency

$$\Rightarrow A' = \frac{A_{OL}}{\left[1 + j\left(\frac{f}{f_d}\right)\right] \left[1 + j\left(\frac{f}{f_1}\right)\right] \left[1 + j\left(\frac{f}{f_2}\right)\right] \left[1 + j\left(\frac{f}{f_3}\right)\right]}$$

where  $f_d < f_1 < f_2 < f_3$

 The values of R and c are selected in such a way that loop gain drops to 0 dB with slope of -20dB/decade and at a frequency where the poles of uncompensated system contributes very small phase shift.



Advantage :-

To adjust  $f_d$  value, adequate phase margin and stability of system is assured.

## disadvantage

→ Band width reduces.

## ii) Pole-zero compensation :-

In this method, transfer function 'A' is modified by adding a pole and a zero with help of compensating network.

→ The zero added at higher frequency

→ pole added at lower frequency.

 


Fig :- Pole-zero compensation

Apply voltage divider rule,

$$V_o = \frac{z_2}{z_1 + z_2} \cdot V_o'$$

where,  $z_2 = R_2 - jX_{C_2}$

$$z_1 = R_1$$

$$\Rightarrow V_o = \frac{R_2 - jX_{C_2}}{R_1 + R_2 - jX_{C_2}} \cdot V_o'$$

$$\Rightarrow \frac{V_o}{V_o'} = \frac{R_2 - jX_{C_2}}{R_1 + R_2 - jX_{C_2}}$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{R_2 + \frac{1}{j2\pi f c_2}}{R_1 + R_2 + \frac{1}{j2\pi f c_2}}$$

$\left[ \begin{array}{l} \therefore -j = \frac{1}{j} \\ x_{c2} = \frac{1}{2\pi f c_2} \end{array} \right]$

$$A' = \frac{R_2(j2\pi f c_2) + 1}{(R_1 + R_2) j2\pi f c_2 + 1} \quad \text{--- } ①$$

consider  $f_1 = \frac{1}{2\pi R_2 c_2}$  and

$$f_0 = \frac{1}{2\pi(R_1 + R_2)c_2}$$

Then eq ①, becomes

$$\boxed{A' = \frac{1 + j \left( \frac{f}{f_1} \right)}{1 + j \left( \frac{f}{f_0} \right)}} \quad \text{--- } ②$$

The values of  $R_1, R_2, c_2$  are selected that break frequency for the zero matches with 1<sup>st</sup> corner frequency  $f_1$  of the uncompensated system. while pole of the compensating network  $f_0$  is selected in a such a way that compensated transfer function  $A'$  passes through 0 dB at 2<sup>nd</sup> corner frequency  $f_2$  of the uncompensated system.

Loop gain becomes  $A' = A A_1$

consider  $A' = \frac{V_o}{V_i}$

$$= \frac{V_o}{V'_o} \cdot \frac{V'_o}{V_i} \quad \text{--- } ③$$

Substitute ev② in ev③

$$A' = \left[ \frac{1+j\left(\frac{f}{f_1}\right)}{1+j\left(\frac{f}{f_0}\right)} \right] \cdot A$$


But  $A = \frac{A_{OL}}{\left[1+j\left(\frac{f}{f_1}\right)\right] \left[1+j\left(\frac{f}{f_2}\right)\right] \left[1+j\left(\frac{f}{f_3}\right)\right]}$

$$\Rightarrow A' = \left[ \frac{1+j\left(\frac{f}{f_1}\right)}{1+j\left(\frac{f}{f_0}\right)} \right] \cdot \frac{A_{OL}}{\left[1+j\left(\frac{f}{f_1}\right)\right] \left[1+j\left(\frac{f}{f_2}\right)\right] \left[1+j\left(\frac{f}{f_3}\right)\right]}$$

$$\Rightarrow A' = \boxed{\frac{A_{OL}}{\left[1+j\left(\frac{f}{f_0}\right)\right] \left[1+j\left(\frac{f}{f_2}\right)\right] \left[1+j\left(\frac{f}{f_3}\right)\right]}} ; 0 < f_0 < f_1 < f_2 < f_3$$

The 1<sup>st</sup> corner frequency is  $f_0$  and gain starts rolling off at -20 dB/decade at  $f_0$ .

 → At  $f=f_1$ , there is Pole-zero cancellation and rolling rate continues at -20 dB/decade.



Advantage

→ Band width is more as compared to Dominant Pole compensation.

## Internal compensation technique:-

In OP-amps IC 741, compensation is provided internally, which is generally built in lag compensation.

→ A capacitor ranging from 10 to 30PF is fabricated between Input and output stage to achieve compensation. This type of compensation is called "miller effect compensation" such OP-amps are called compensated OP-amps.

## miller effect compensation :-


The main drawback in dominant pole compensation is the reduction in bandwidth. In dominant pole compensation, capacitor is connected to ground from output terminal.

In miller effect compensation capacitor is connected in feed back path.

The Gain of the darlington stage is given by

$$\omega_2 = -G_{mc} R_o$$

 $G_{mc}$  → Transconductance of the stage



$$Z_{cm} = \frac{Z_{cc}}{1 + \omega_2}$$

$$\text{where, } z_{cm} = \frac{1}{j\omega c_m}, z_{cc} = \frac{1}{j\omega c_c}$$

$$\Rightarrow \frac{1}{j\omega c_m} = \frac{\frac{1}{j\omega c_c}}{1 + \alpha_2}$$


$$\Rightarrow \frac{(1 + \alpha_2)}{j\omega c_c} = \frac{1}{j\omega c_m} \Rightarrow \frac{1}{j\omega c_m} = \frac{1}{(1 + \alpha_2)j\omega c_c}$$

$$\Rightarrow C_m = (1 + \alpha_2) C_c$$

The Miller equivalent capacitance  $C_m$  forms a low pass RC section with input  $R_i$ , whose corner frequency is given by

$$f_d = \frac{1}{2\pi C_m R_i}$$

 The uncompensated and compensated magnitude plots are shown in fig.



Advantage:-

→ It increases the band width.

### 3. Linear and Non-linear Applications of opamp

#### Introduction:-

1. Linear circuit :- The output voltage varies linearly with respect to input voltage. \* feed back is used from output to Inverting terminal  
→ Applications are Adder, Subtractor, Integrator, Differentiator, buffer etc..

#### 2. Non-linear circuit :-

- Feed back is used from output to the noninverting input terminal.
- The feed back may be provided to Inverting input terminal using nonlinear elements like diodes, transistors etc..
- Applications are comparators, Schmitt trigger, log amplifier, Antilog Amplifier, Precision rectifier.

#### Virtual ground :-

This means the differential Input voltage  $V_d$  between the Inverting and Non Inverting Input terminals is zero

$$\text{i.e } V_d = V_A - V_B$$

$$0 = V_A - V_B \Rightarrow V_A = V_B$$

 


Fig:- Concept of Virtual ground



REDMI NOTE 5 PRO  
MI DUAL CAMERA


FOR EX,

If the Non-Inverting terminal is grounded, according to the concept of virtual short, Inverting terminal is also at ground potential, there is no physical connection between inverting terminal and ground. This is the principle of virtual ground.

Ideal Inverting Amplifier :-

An Amplifier which provides a phase shift of  $180^\circ$  between input and output is called Inverting Amplifier.

From fig,

 

$$V_B = 0$$

concept of virtual ground,  $V_A = 0$

$$\text{Input side, } I = \frac{V_{in} - V_A}{R_i}$$

$$= \frac{V_{in} - 0}{R_i} = \frac{V_{in}}{R_i} \quad \text{--- (1)}$$

$$\text{Output side, } I = \frac{V_A - V_o}{R_f} = \frac{0 - V_o}{R_f}$$

$$= -\frac{V_o}{R_f} \quad \text{--- (2)}$$

Evaluating eq (1), (2)

REDMI NOTE 5 PRO MI DUAL CAMERA

$$\frac{V_{in}}{R_i} = -\frac{V_o}{R_f} \Rightarrow V_o = -\frac{R_f}{R_i} V_{in}$$

(2)

$$\Rightarrow \frac{V_o}{V_{in}} = -\frac{R_f}{R_i}$$

$$\Rightarrow A_{VF} = -\frac{R_f}{R_i}$$

where  $A_{VF} \rightarrow$  Gain with feed back

'-' sign indicates that polarity of output is opposite to input.


 


Fig:- Input and output waveforms
 
### Ideal Non-Inverting Amplifier :-

An amplifier which amplifies the input without producing any phase shift between input and output is called Non-Inverting Amplifier.



From fig,

$$V_B = V_{in}$$

concept of virtual ground,  $V_A = V_{in}$

output side  $I = V_o - V_A = V_o - V_{in}$  — ①

REDMI NOTE 5 PRO  
MI DUAL CAMERA

At Inverting terminal,

$$I = \frac{V_{A-O}}{R_1} = \frac{V_A}{R_1} = \frac{V_{in}}{R_1} \quad \text{--- (2)}$$

Evaluating eq(1), (2)

$$\Rightarrow \frac{V_o - V_{in}}{R_f} = \frac{V_{in}}{R_1}$$

$$\Rightarrow \frac{V_o}{R_f} - \frac{V_{in}}{R_f} = \frac{V_{in}}{R_1}$$

$$\Rightarrow \frac{V_o}{R_f} = \frac{V_{in}}{R_1} + \frac{V_{in}}{R_f}$$

$$= V_{in} \left[ \frac{1}{R_1} + \frac{1}{R_f} \right] \Rightarrow V_{in} \left[ \frac{R_f + R_1}{R_1 R_f} \right]$$


$$\Rightarrow \frac{V_o}{R_f} = V_{in} \left[ \frac{R_f + R_1}{R_1 R_f} \right]$$

$$\Rightarrow V_o = V_{in} \cdot R_f \left[ \frac{R_f + R_1}{R_1 R_f} \right]$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{R_f + R_1}{R_1}$$

$$\Rightarrow A_{VF} = 1 + \frac{R_f}{R_1}$$

 The '+' sign indicates there is no phase shift between input and output.




REDMI NOTE 5 PRO  
MI DUAL CAMERA

Qia: - Input and output waveforms

### practical Inverting Amplifier :-

The practical Inverting op-amp has major differences as compared to ideal, they are

 - i) input resistance  $R_i$  is less than  $\infty$ , hence Input current is finite
- ii)  $A_{OL}$  is less than  $\infty$
- iii)  $R_o$  is not zero.



APPLY KCL, at node 'A'

$$I = I_{b2} + I_f$$

$I_{b2}$  can be neglected, since it flows to inverting terminal

$$\Rightarrow I \approx I_f \quad \text{--- (1)}$$

$$\Rightarrow \frac{V_{in} - V_A}{R_1} = \frac{V_A - V_o}{R_f} \quad \text{--- (2)}$$

$$\text{w.k.t } V_o = A_{OL} V_d$$

$$= A_{OL} (V_1 - V_2) = A_{OL} (V_B - V_A)$$

from fig, input is inverting (-) so non inverting input

$$V_B = 0$$

$$\Rightarrow V_o = A_{OL} (0 - V_A) \Rightarrow V_o = -V_A \cdot A_{OL}$$

$$\Rightarrow V_A = -\frac{V_o}{A_{OL}} \quad \text{--- (3)}$$

sub. eq (3) in (2)

**REDMI NOTE 5 PRO  
MI DUAL CAMERA**

$$\frac{V_{in} + \frac{V_o}{A_{OL}}}{R_1} = \frac{-\frac{V_o}{A_{OL}} - V_o}{R_f}$$

$$\Rightarrow \left( V_{in} + \frac{V_o}{A_{OL}} \right) R_f = \left( -\frac{V_o}{A_{OL}} - V_o \right) R_i$$

$$\Rightarrow V_{in} R_f + \frac{V_o}{A_{OL}} R_f = -\frac{V_o}{A_{OL}} R_i - V_o R_i$$

$$\Rightarrow V_{in} R_f = -\frac{V_o}{A_{OL}} R_f - \frac{V_o}{A_{OL}} R_i - V_o R_i$$

$$= -V_o \left[ \frac{R_f}{A_{OL}} + \frac{R_i}{A_{OL}} + R_i \right]$$

$$= -V_o \left[ \frac{R_f + R_i + A_{OL} R_i}{A_{OL}} \right]$$

$$\Rightarrow V_o = -\frac{V_{in} R_f}{R_f + R_i + A_{OL} R_i} \cdot A_{OL}$$

$$A_{CL} \Rightarrow \frac{V_o}{V_{in}} = -\frac{A_{OL} R_f}{R_i + R_f + A_{OL} R_i}$$

— (4)

Ideally,  $A_{OL}$  is very large,  $A_{OL} R_i \gg R_i + R_f$  hence  $R_i + R_f$  is neglected.


$$\Rightarrow A_{CL} = -\frac{A_{OL} R_f}{A_{OL} R_i} \Rightarrow A_{CL} = -\frac{R_f}{R_i} \text{ (ideal)}$$

Block diagram of Practical Inverting Amplifier :-

From fig,

$$V_d = -V_{in} K - V_f \quad \text{--- (1)}$$

$$V_o = V_d A \quad \text{--- (2)}$$

 

REDMI NOTE 5 PRO  
MI DUAL CAMERA

(4)

Sub. eq(1) in (2)

$$v_o = (-v_{in}k - v_f)A \quad \text{--- (4)}$$

Sub. eq(3) in (4)

$$v_o = (-v_{in}k - Bv_o)A \quad \text{--- (5)}$$

$$v_o = -v_{in}kA - Bv_o A$$

$$\Rightarrow v_o + Bv_o A = -v_{in}kA$$

$$\Rightarrow v_o(1+BA) = -v_{in}kA$$

$$\Rightarrow \frac{v_o}{v_{in}} = \frac{-kA}{1+BA} \quad \text{--- (6)}$$

From eq(4),  $A_{CL} = -\frac{A_{OL}R_f}{R_i + R_f + A_{OL}R_i}$  --- (7)  
in previous topic

Divide  $(R_i + R_f)$  Numerator & denominator term

$$A_{CL} = \frac{-\frac{A_{OL}R_f}{R_i + R_f}}{\frac{R_i + R_f + A_{OL}R_i}{R_i + R_f}} = \frac{-\frac{A_{OL}R_f}{R_i + R_f}}{1 + \frac{A_{OL}R_i}{R_i + R_f}} \quad \text{--- (8)}$$

Compare eq(6), (8) we get,

$$A = A_{OL}, K = \frac{R_f}{R_i + R_f}, B = \frac{R_i}{R_i + R_f}$$

$$\Rightarrow A_{CL} = -\frac{AK}{1+BA} \quad \text{--- (9)}$$

Ideally,  $BA \gg 1 \approx 1+BA = BA$ 

$$\Rightarrow A_{CL} = -\frac{AK}{BA} = -\frac{K}{B}$$

REDMI NOTE 5 PRO  
MI DUAL CAMERA

$$= -\frac{R_f}{R_i + R_f} \times \frac{R_i + R_f}{R_i}$$

$$\Rightarrow A_{CL} = -\frac{R_f}{R_i}$$

### Practical Non-Inverting Amplifier :-


$R_f$  → feed back resistor

From fig.

$$V_f = (V_1 - V_2) A_{OL}$$

$$V_o = (V_{in} - V_f) A_{OL} \quad \text{--- (1)}$$

 $\{ V_1 = V_{in} \}$      $\{ V_2 = V_f \}$



Apply voltage divider rule,

$$V_f = \frac{R_1}{R_1 + R_f} \cdot V_o \quad \text{--- (2)}$$

sub. eqn (2) in eqn (1)

$$V_o = \left( V_{in} - \frac{R_1 V_o}{R_1 + R_f} \right) A_{OL}$$

$$\Rightarrow V_o = A_{OL} V_{in} - A_{OL} \frac{V_o R_1}{R_1 + R_f}$$

$$\Rightarrow V_o + A_{OL} \frac{V_o R_1}{R_1 + R_f} = A_{OL} V_{in}$$

$$\Rightarrow V_o \left[ 1 + A_{OL} \frac{R_1}{R_1 + R_f} \right] = A_{OL} V_{in}$$

$$\Rightarrow V_o = \frac{A_{OL}}{1 + A_{OL} \frac{R_1}{R_1 + R_f}} \cdot V_{in}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{A_{OL}}{\frac{R_1 + R_f + A_{OL} R_1}{R_1 + R_f}}$$

$$\Rightarrow A_{CL} = \frac{A_{OL} (R_1 + R_f)}{R_1 + R_f + A_{OL} R_1} \quad \text{--- (3)}$$

REDMI NOTE 5 PRO  
MI DUAL CAMERA

(5)

consider,

$$A_{OL} R_1 > (R_1 + R_f)$$

then eq (3) changes to ,  $A_{OL} = \frac{A_{OL} (R_1 + R_f)}{A_{OL} R_1}$


$$\Rightarrow A_{OL} = \frac{R_1 + R_f}{R_1}$$

$$\Rightarrow A_{OL} = 1 + \frac{R_f}{R_1} \text{ (ideal)}$$

Block diagram of practical Non-Inverting Amplifier :-

Forward Path gain 'A' and  
feed back path gain 'B'.

From fig.

 

$$V_d = V_{in} - V_f \quad \text{--- (1)}$$

$$V_o = A V_d \quad \text{--- (2)}$$

$$V_f = B V_o \quad \text{--- (3)}$$

Sub. eq (1) in eq (2)

$$V_o = A (V_{in} - V_f) \quad \text{--- (4)}$$

Sub. eq (3) in eq (4)

$$V_o = A (V_{in} - B V_o)$$

$$\Rightarrow V_o = A V_{in} - B V_o A$$

$$\Rightarrow V_o + B V_o A = A V_{in}$$

$$\Rightarrow V_o (1 + BA) = A V_{in}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{A}{1 + BA} \quad \text{--- (5)}$$

REDMI NOTE 5 PRO  
MI DUAL CAMERA

$$\text{w.k.t } A_{CL} = \frac{A_{OL}(R_I + R_F)}{R_I + R_F + R_I A_{OL}}$$

divide N.Y and D.Y by  $(R_I + R_F)$

$$\Rightarrow A_{CL} = \frac{\frac{A_{OL}(R_I + R_F)}{R_I + R_F}}{\frac{R_I + R_F + R_I A_{OL}}{R_I + R_F}}$$

$$\Rightarrow A_{CL} = \frac{A_{OL}}{1 + A_{OL} \left( \frac{R_I}{R_I + R_F} \right)} \quad \text{--- ⑥}$$

compare eq ⑤ and eq ⑥, we get

$$A = A_{OL}, B = \frac{R_I}{R_I + R_F}$$

$$\Rightarrow A_{CL} = \frac{A}{1 + BA}$$

consider  $1 + BA \approx BA$

$$\Rightarrow A_{CL} = \frac{A}{BA} = \frac{1}{B}$$

$$= \frac{1}{\frac{R_I}{R_I + R_F}} = \frac{R_I + R_F}{R_I}$$

$$\Rightarrow A_{CL} = 1 + \frac{R_F}{R_I}$$

### Integrator :-

The output voltage is the Integration of the Input Voltage.

→ The Integrator circuit can be obtained without using active devices like op-amp, transistors the Integrator called as "Passive Integrator".

Integrator using an Active devices like opamp is called "Active Integrator".

REDMI NOTE 5 PRO

MI DUAL CAMERA


Integrator

(6)

### Ideal Active Integrator :-

From fig,  $V_B = 0$

concept of virtual ground,  $V_A = 0$

 

$$\text{Input side, } I = \frac{V_{in} - V_A}{R_i} = \frac{V_{in} - 0}{R_i}$$

$$= \frac{V_{in}}{R_i} \quad \text{--- (1)}$$

$$\text{output side, } I = C_f \frac{d}{dt} (V_A - V_o)$$

$$= C_f \frac{d}{dt} (0 - V_o) = -C_f \frac{dV_o}{dt} \quad \text{--- (2)}$$

Evaluating eq (1), (2)

$$\Rightarrow \frac{V_{in}}{R_i} = -C_f \frac{dV_o}{dt} \quad \text{--- (3)}$$

Integrating eq (3) on both sides,

$$\Rightarrow \int_0^t \frac{V_{in}}{R_i} dt = -C_f \int \frac{dV_o}{dt} dt$$

$$= -C_f V_o$$

$$\Rightarrow V_o = -\frac{1}{R_i C_f} \int_0^t V_{in} dt \quad \text{--- (4)}$$

$R_i C_f \rightarrow \text{Time constant}$

 


Fig:- Input and output waveform



### Frequency response of Ideal Integrator :-

$$\text{w.k.t } V_o(t) = -\frac{1}{R_1 C_p} \int_0^t V_{in} dt$$

Taking Laplace transform,

$$V_o(s) = -\frac{1}{s R_1 C_p} V_{in}(s)$$

Let  $s = j\omega$ ,

$$\Rightarrow V_o(j\omega) = -\frac{1}{j\omega R_1 C_p} V_{in}(j\omega)$$

$$\Rightarrow \frac{V_o(j\omega)}{V_{in}(j\omega)} = -\frac{1}{j\omega R_1 C_p} \quad \text{--- (5)}$$

$$\text{The magnitude value is, } A = \left| \frac{V_o(j\omega)}{V_{in}(j\omega)} \right| = \left| -\frac{1}{j\omega R_1 C_p} \right|$$

$$\Rightarrow A = \frac{1}{\omega R_1 C_p} = \frac{1}{2\pi f R_1 C_p} \quad \text{--- (6)}$$

$$\Rightarrow A = \frac{f_b}{f} \quad \left\{ \because f_b = \frac{1}{2\pi R_1 C_p} \right. \quad \text{--- (7)}$$

Let  $f=0$ , eq (6) becomes  $A=\infty$

and  $f=f_b \Rightarrow A=1$  i.e 0 dB.

 


Fig:- frequency response of Ideal Integrator.

The gain rolls off at a rate of  $-20\text{dB/decade}$ .

### Errors in an Ideal Integrator:-

- In the presence of input signal, offset voltage and bias current contribute an error voltage at the output. It is not possible to get a true integration of input signal at the output. Output waveform may be distorted due to error voltage.
- Another limitation is Bandwidth is very small. Hence ideal Integrator used for very small frequency range of Input only.


### Practical Integrator:-

From fig,

$$V_B = 0 \Rightarrow V_A = 0$$

Apply KCL at node 'A'

$$I = I_1 + I_2 \quad \text{--- (1)}$$

 

$$\text{From fig, } I = \frac{V_{in} - V_A}{R_1} = \frac{V_{in} - 0}{R_1}$$

$$= \frac{V_{in}}{R_1} \quad \text{--- (2)}$$

$$\text{and } I_1 = C_f \frac{d}{dt} (V_A - V_o) = C_f \frac{d}{dt} (0 - V_o)$$

$$= -C_f \frac{dV_o}{dt} \quad \text{--- (3)}$$

$$\text{and } I_2 = \frac{V_A - V_o}{R_f} = \frac{0 - V_o}{R_f} = -\frac{V_o}{R_f} \quad \text{--- (4)}$$

Sub. eqn (2), (3), (4) in eqn (1)

$$\Rightarrow \frac{V_{in}}{R_1} = -C_f \frac{dV_o}{dt} - \frac{V_o}{R_f}$$

Apply Laplace transform,



$$\frac{V_{in}(s)}{R_1} = -sC_F V_o(s) - \frac{V_o(s)}{R_F} \quad \text{--- (5)}$$

$$= -V_o(s) \left[ sC_F + \frac{1}{R_F} \right]$$

$$= -V_o(s) \left[ \frac{R_F s C_F + 1}{R_F} \right]$$

$$\Rightarrow V_o(s) = -\frac{R_F}{R_1(R_F s C_F + 1)} \cdot V_{in}(s) \quad \text{--- (6)}$$

$$= \frac{-1}{sC_F R_F R_1 + R_1} \cdot V_{in}(s)$$

$$= -\frac{1}{sC_F R_1 + \left( \frac{R_1}{R_F} \right)} \cdot V_{in}(s)$$

when  $R_F$  is large value,  $R_F/R_1$  can be neglected, hence

$$V_o(s) = -\frac{1}{sC_F R_1} V_{in}(s)$$

Apply Inverse Laplace transform,

$$V_o(t) = -\frac{1}{R_1 C_F} \int v_{in}(t) dt$$

Frequency response of practical Integrator :-

$$\text{from eq (6), } \frac{V_o(s)}{V_{in}(s)} = -\frac{R_F/R_1}{1+sR_F C_F}$$

put  $s \rightarrow j\omega$

$$\text{then, } \frac{V_o(j\omega)}{V_{in}(j\omega)} = -\frac{R_F/R_1}{1+j\omega R_F C_F}$$

$$\Rightarrow A = -\frac{R_F/R_1}{1+j2\pi f R_F C_F}$$

(8)

$$\Rightarrow A = - \frac{R_f/R_1}{1+j \frac{f/f_\omega}{}} \quad \left[ \because f_\omega = \frac{1}{2\pi R_f C_f} \right]$$

magnitude,  $|A| = \left| - \frac{R_f/R_1}{1+j(f/f_\omega)} \right|$

$$= \frac{R_f/R_1}{\sqrt{1 + (f/f_\omega)^2}} \quad \text{--- (7)}$$

Let  $f = 0 \rightarrow |A| = R_f/R_1$

$$= 20 \log \left( \frac{R_f}{R_1} \right) \text{ dB}$$

Let  $f = f_\omega \rightarrow |A| = \frac{R_f/R_1}{\sqrt{1+1}} = \frac{R_f/R_1}{\sqrt{2}} = 0.707 \frac{R_f}{R_1}$


i.e.  $20 \log |A| = 20 \log (0.707 \frac{R_f}{R_1})$

$$= 20 \log (0.707) + 20 \log \left( \frac{R_f}{R_1} \right)$$

$$= -3 \text{ dB} + \text{D.C gain}$$

$\rightarrow$  At  $f = f_\omega$ , magnitude of gain drops by 3dB frequency.

which is the break frequency.

 

### Applications of Practical Integrator :-

- Analog computers
- Analog to digital converters
- Various signal wave shaping circuits
- Ramp generators

### Differentiator :-

The circuit which produces the output voltage is the differentiation of input voltage is called differentiator.

### Ideal Active op-amp differentiator :-

From fig,  $V_B = 0$

concept of virtual ground

$$V_A = 0$$

$$\text{Input side, } I_1 = C_1 \frac{d}{dt} (V_{in} - V_A)$$

$$= C_1 \frac{d}{dt} (V_{in} - 0)$$

$$= C_1 \frac{d}{dt} V_{in} \quad \text{--- (1)}$$

$$\text{Output side, } I_1 = \frac{V_A - V_o}{R_f} = \frac{0 - V_o}{R_f} = -\frac{V_o}{R_f} \quad \text{--- (2)}$$


Evaluating eq (1), (2)

$$C_1 \frac{dV_{in}}{dt} = -\frac{V_o}{R_f}$$

$$\Rightarrow V_o = -C_1 R_f \frac{dV_{in}}{dt} \quad \text{--- (3)}$$

where  $C_1 R_f \rightarrow \text{Time const}$

 This equation shows that output is  $C_1 R_f$  times the differentiation of input.



(9)

 


Fig :- Input and output for square wave input.

Frequency response of ideal differentiator :-

$$\omega \cdot K \cdot T \quad V_o(t) = -R_f C_1 \frac{dV_{in}}{dt}$$

Taking Laplace transform,

$$V_o(s) = -s R_f C_1 V_{in}(s)$$

$$\text{put } s = j\omega$$

$$V_o(j\omega) = -j\omega R_f C_1 V_{in}(j\omega)$$

$$\Rightarrow \frac{V_o(j\omega)}{V_{in}(j\omega)} = -j\omega R_f C_1$$

magnitude is ,

$$A = \left| \frac{V_o(j\omega)}{V_{in}(j\omega)} \right| = |-j\omega R_f C_1|$$

$$A = \omega R_f C_1 = 2\pi f R_f C_1 \quad \text{--- (4)}$$



At  $f=0$ ,  $A=0$


From eq(4), as the frequency increases, gain also increases.

From eq(4), consider  $f_{\alpha} = \frac{1}{2\pi R_f C_1}$

then eq(4) changes to  $A = f/f_{\alpha}$  — (5)

At  $f=f_{\alpha}$ , then  $A=1$  (or)  $20 \log 1 = 0 \text{ dB}$ . it gives increase in gain is at a rate of  $20 \text{ dB/decade}$ .

 The frequency response of such Ideal differentiator as shown in fig.



Disadvantages of an ideal differentiator :-

→ Gain increases as frequency increases, At some high frequency, the differentiator may become unstable and break into oscillations.

There is a possibility that op-amp go into saturation.

→ At high frequencies, differentiator circuit suffers from its stability and noise problems.

→ These problems can be corrected by using practical differentiator circuit.

practical differentiator :-

from fig,

$$V_B = 0.$$

concept of virtual ground  $V_A = 0$

from the circuit,

$$I = \frac{V_{in} - V_A}{Z_1} = \frac{V_{in} - 0}{Z_1} = \frac{V_{in}(s)}{Z_1} \quad \text{--- (1)}$$

$$\text{where, } Z_1 = R_1 + C_1$$

APPLY Laplace, then

$$Z_1 = R_1 + \frac{1}{sC_1}$$

$$= \frac{sC_1 \star R_1 + 1}{sC_1} \quad \text{--- (2)}$$

sub. eq(2) in (1)

$$\Rightarrow I = \frac{\frac{V_{in}(s)}{sC_1 R_1 + 1}}{\frac{sC_1}{sC_1}} = \frac{sC_1 V_{in}(s)}{sC_1 R_1 + 1} \quad \text{--- (3)}$$

$$\text{Now } I_1 = \frac{V_A - V_o}{R_f} = \frac{0 - V_o}{R_f} = -\frac{V_o}{R_f} \Rightarrow -\frac{V_o(s)}{R_f} \quad \text{--- (4) } [\because U.T]$$


$$I_2 = C_F \frac{d}{dt} (V_A - V_o)$$

$$= C_F \frac{d}{dt} (0 - V_o) = -C_F \frac{dV_o}{dt}$$

$$= -sC_F V_o(s) \quad \text{--- (5)}$$

APPLY KCL at node 'A'

$$I = I_1 + I_2 \quad \text{--- (6)}$$

 

sub. eq ③, ④, ⑤ in eq ⑥,

$$\begin{aligned}\frac{sc_1 V_{in}(s)}{1+SR_1C_1} &= -\frac{V_o(s)}{R_f} - sc_f V_o(s) \\ &= -\frac{V_o(s) + R_f sc_f V_o(s)}{R_f} \\ &= -V_o(s) \left[ \frac{1+SR_f C_f}{R_f} \right]\end{aligned}$$

$$\Rightarrow V_o(s) = \frac{-SR_f C_1 V_{in}(s)}{(1+SR_f C_f)(1+SR_1C_1)} \quad \text{--- ⑦}$$

If  $R_f C_f = R_1 C_1$ , then eq ⑦ changes to

$$V_o(s) = \frac{-SR_f C_1 V_{in}(s)}{(1+SR_f C_f)^2} \quad \text{--- ⑧}$$

If  $R_f C_1 > R_1 C_1$  (or)  $R_f C_f$

$$\Rightarrow V_o(s) = -SR_f C_1 V_{in}(s)$$

Apply Inverse Laplace,

$$\Rightarrow V_o(t) = -R_f C_1 \frac{dV_{in}(t)}{dt} \quad \text{--- ⑨} \quad [\because s = \frac{d}{dt}]$$

From eq ⑨, output voltage is the  $R_f C_1$  times the differentiation of the input.

(11)

### Frequency response of practical differentiator :-

$$\text{From eq (8), } \frac{V_o(s)}{V_{in}(s)} = \frac{-s R_f C_1}{(1+sR_1C_1)^2}$$

Put  $s = j\omega$

$$\begin{aligned} \frac{V_o(j\omega)}{V_{in}(j\omega)} &= \frac{-j\omega R_f C_1}{(1+j\omega R_1 C_1)^2} \\ &= \frac{-j 2\pi f R_f C_1}{(1+j 2\pi f R_1 C_1)^2} \quad \text{--- (10)} \end{aligned}$$

$$\text{Let } f_b = \frac{1}{2\pi R_1 C_1} \text{ and } f_\alpha = \frac{1}{2\pi R_f C_1}$$

then eq (10) becomes,

$$\frac{V_o(j\omega)}{V_{in}(j\omega)} = \frac{-j(f/f_\alpha)}{1+j(f/f_b)^2} \quad \text{--- (11)}$$

$$\text{magnitude, } A = \left| \frac{V_o(j\omega)}{V_{in}(j\omega)} \right| = \frac{f/f_\alpha}{\sqrt{1+(f/f_b)^2}}$$

$$\Rightarrow A = \frac{f/f_\alpha}{1+(f/f_b)^2}$$

 


Fig :- frequency response of practical differentiator

from fig,

frequency increases, gain increases till  $f=f_b$  at 20dB/decade  
after  $f=f_b$  the gain becomes decreases at 20dB/decade.

### Applications of Practical differentiator :-

- wave shaping circuits
- Rate of change detector in FM demodulators.
- Avoided in Analog computers.

### Summer (or) Adder circuit :-

The output voltage gives addition of applied input voltages.

→ depending upon the sign of the output, summer circuit divided into Inverting summer and Non-Inverting summer.

#### I. Inverting summer :-

In this circuit

Input signals ( $V_1, V_2$ )

are applied to

Inverting terminal.

 


Fig:- Inverting summer

From fig.  $V_B = 0$

concept of virtual ground,  $V_A = 0$

$$\text{Input side, } I_1 = \frac{V_1 - V_A}{R_1} = \frac{V_1 - 0}{R_1} = \frac{V_1}{R_1} \quad \text{--- (1)}$$

$$I_2 = \frac{V_2 - V_A}{R_2} = \frac{V_2 - 0}{R_2} = \frac{V_2}{R_2} \quad \text{--- (2)}$$

output side,  $I = \frac{V_A - V_0}{R_f} = \frac{0 - V_0}{R_f} = -\frac{V_0}{R_f} \quad \text{--- (3)}$

apply KCL at node 'A'

$$I = I_1 + I_2 \quad \text{--- (4)}$$

sub. eq (1), (2), (3) in (4)

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = -\frac{V_0}{R_f}$$

$$\Rightarrow V_0 = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} \right] \quad \text{--- (5)}$$

If  $R_f = R_1 = R_2$

$$\Rightarrow V_0 = -(V_1 + V_2)$$

'-' indicates phase difference between Input & output

## 2. Non-Inverting summing Amplifier :-

In this circuit we are applying Input Voltages to non-inverting terminal.

 


Fig:- Non-Inverting summer

Input side,

$$I_1 = \frac{V_1 - V_B}{R_1} \quad \text{and} \quad I_2 = \frac{V_2 - V_B}{R_2}$$

Input current of OP-Amp zero i.e

$$I_1 + I_2 = 0$$

$$\frac{V_1 - V_B}{R_1} + \frac{V_2 - V_B}{R_2} = 0$$

$$\Rightarrow \frac{V_1}{R_1} - \frac{V_B}{R_1} + \frac{V_2}{R_2} - \frac{V_B}{R_2} = 0$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_B}{R_1} + \frac{V_B}{R_2}$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} = V_B \left[ \frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$= V_B \left[ \frac{R_1 + R_2}{R_1 R_2} \right]$$

$$\Rightarrow V_B = \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) \frac{R_1 R_2}{R_1 + R_2}$$

$$= \left[ \frac{V_1 R_2 + V_2 R_1}{R_1 R_2} \right] \cdot \frac{R_1 R_2}{R_1 + R_2}$$

$$\Rightarrow V_B = \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2} \quad \text{--- (1)}$$

At node 'A'

$$I = \frac{V_o - V_A}{R_f} = \frac{V_o - V_B}{R_f} \quad \text{--- (2)} \quad [ \because V_A = V_B ]$$

$$\text{and} \quad I = \frac{V_A - 0}{R} = \frac{V_A}{R} = \frac{V_B}{R} \quad \text{--- (3)} \quad [ \because V_A = V_B ]$$

evaluate eqn (2), (3)

$$\Rightarrow \frac{V_o - V_B}{R_f} = \frac{V_B}{R}$$

$$\Rightarrow \frac{V_o}{R_f} - \frac{V_B}{R_f} = \frac{V_B}{R}$$

$$\Rightarrow \frac{V_o}{R_f} = \frac{V_B}{R} + \frac{V_B}{R_f}$$

$$= V_B \left[ \frac{1}{R} + \frac{1}{R_f} \right]$$

$$\frac{V_o}{R_f} = V_B \left[ \frac{R_f + R}{RR_f} \right]$$

$$\Rightarrow V_o = R_f \cdot V_B \left[ \frac{R_f + R}{R R_f} \right]$$

$$\Rightarrow V_o = V_B \left[ \frac{R_f + R}{R} \right] \quad \text{--- (4)}$$

sub. eq(1) in (4)

$$\Rightarrow V_o = \left[ \frac{V_1 R_2 + V_2 R_1}{R_1 + R_2} \right] \left[ \frac{R_f + R}{R} \right]$$

$$= \frac{V_1 R_2}{R_1 + R_2} \cdot \left[ \frac{R_f + R}{R} \right] + \frac{V_2 R_1}{R_1 + R_2} \cdot \left[ \frac{R_f + R}{R} \right]$$

$$V_o = \frac{R_2 (R_f + R) V_1}{R(R_1 + R_2)} + \frac{R_1 (R + R_f) V_2}{R(R_1 + R_2)} \quad \text{--- (5)}$$

If  $R_1 = R_2 = R_f = R$ ,

then

$$V_o = V_1 + V_2$$

There is no phase difference between Input and Output.

### Note

Average of Inverting summer circuit  $V_o = -\left[ \frac{V_1 + V_2}{2} \right]$

The output voltage is average of 2 input voltages so circuit called as averager.

REDMI NOTE 5 PRO  
MI DUAL CAMERA




## Subtractor (or) Difference Amplifier :-

The subtraction of 2 input voltages is possible with help of op-amp circuit is called subtractor (or) difference amplifier.

Method-1

 
To find relation between inputs and output use superposition principle.



Case ① :- Input applied to Inverting terminal and  $V_2$  considered to zero

We know that,

Inverting OP-amp

 


$$V_{01} = -\frac{R_f}{R_1} \cdot V_1 \quad \text{--- ①}$$

Case ② :- Input applied to Non-Inverting terminal and  $V_1$  considered as zero.

It is Non-Inverting OP-Amp
 
$$V_{02} = \left(1 + \frac{R_f}{R_2}\right) V_B \quad \text{--- ②}$$



Apply voltage divider rule at Node 'B'

$$V_B = \left(\frac{R_f}{R_2 + R_f}\right) V_2 \quad \text{--- ③}$$

sub. eq(3) in eq(2)

$$V_{O2} = \left(1 + \frac{R_f}{R_1}\right) \frac{R_f V_2}{R_2 + R_f} \quad \text{--- (4)}$$

According to super position principle,

$$\begin{aligned} V_o &= V_{O1} + V_{O2} \\ &= -\frac{R_f}{R_1} V_1 + \left[1 + \frac{R_f}{R_1}\right] \cdot \frac{R_f V_2}{R_2 + R_f} \\ &= -\frac{R_f}{R_1} V_1 + \left[\frac{R_1 + R_f}{R_1}\right] \frac{R_f V_2}{R_2 + R_f} \end{aligned}$$

If  $R_1 = R_2 = R_f = R$ , then

$$V_o = -V_1 + V_2$$

$$\Rightarrow V_o = V_2 - V_1$$


The output voltage is proportional to the difference between 2 voltages.

(or)

Method-2 :-

$V_1, V_2$  are Input Voltages

and  $V_o$  is the Output Voltage.

 

→ The output voltage connected to inverting terminal through  $R_f$ . So it is -ve feedback and

current  $I_A = 0, I_B = 0$

i)  $I_A = 0, I_B = 0$

ii)  $V_B = V_A$  [ $\because$  concept of virtual ground]

suppose, Input applied to Inverting terminal so,  $V_B = 0$ .

If  $V_B = 0$  it act as open circuit.

voltage divider rule at 'B',

$$V_B = \frac{R_f}{R_f + R_2} V_2 \quad \text{--- (1)}$$

At Node 'A'

$$\text{Input side, } I = \frac{V_1 - V_A}{R_1} \quad \text{--- (2)}$$

$$\text{output side, } I = \frac{V_A - V_0}{R_f} \quad \text{--- (3)}$$

evaluate eq (2), (3)

$$\frac{V_1 - V_A}{R_1} = \frac{V_A - V_0}{R_f}$$

$$\Rightarrow (V_1 - V_A) R_f = (V_A - V_0) R_1$$

$$\Rightarrow V_1 R_f - V_A R_f = V_A R_1 - V_0 R_1$$

$$\Rightarrow V_0 R_1 = V_A R_1 - V_1 R_f + V_A R_f$$

$$= V_A (R_1 + R_f) - V_1 R_f$$

$$\Rightarrow V_0 = \frac{V_A}{R_1} (R_1 + R_f) - \frac{V_1}{R_1} R_f \quad \text{--- (4)}$$

If  $V_B = V_A$ ,

sub. eq (1) in (4)

$$\Rightarrow V_0 = \left( \frac{R_f}{R_f + R_2} \right) V_2 \left( \frac{R_1 + R_f}{R_1} \right) - \frac{V_1}{R_1} R_f$$

consider  $R_1 = R_2$

$$\Rightarrow V_o = \left( \frac{R_f}{R_f + R_i} \right) V_2 - \left[ \frac{R_i \times R_f}{R_i} \right] - V_i \frac{R_f}{R_i}$$

$$= \frac{R_f V_2}{R_i} - V_i \frac{R_f}{R_i}$$

$$V_o = \frac{R_f}{R_i} (V_2 - V_i)$$

If  $R_i = R_f$

$$\Rightarrow \boxed{V_o = V_2 - V_i}$$

### A.C Amplifier :-

The op-amp can amplify A.C signals is called A.C Amplifier.

#### 1. Inverting A.C Amplifier :-


The input applied

to inverting terminal and

input consists of A.C signal and

D.C signals.

 → The capacitor is used to block d.c signals and allows only A.C signals.



$$\text{we know that, } V_o = -\frac{R_f}{R_i} \cdot V_s \quad \text{--- (1)}$$

From fig (2),

$$I = \frac{V_i}{R_i + C} = \frac{V_i}{R_i + \frac{1}{j\omega C}} \quad \text{--- (2)}$$

$$\text{and } V_s = IR_i \quad \text{--- (3)}$$

 


Fig:- (2)

Sub. eq ② in eq ③,

$$v_s = \left[ \frac{V_i}{R_1 + \frac{1}{j\omega C}} \right] R_1$$

$$= \frac{V_i R_1}{R_1 \left[ 1 + \frac{1}{j\omega C R_1} \right]} = \frac{V_i}{1 + \frac{1}{j\omega C R_1}} = \frac{V_i}{1 + \frac{j}{j\omega C R_1 \cdot j}}$$

$$= \frac{V_i}{1 + \frac{j}{j^2 \pi f C R_1}}$$

$$= \frac{V_i}{1 - \frac{j}{2\pi f C R_1}} \quad [ \because j^2 = -1 ]$$

$$\text{Let } f_L = \frac{1}{2\pi f C R_1}$$

$$\Rightarrow v_s = \frac{V_i}{1 - j \left( \frac{f_L}{f} \right)} \quad \text{--- ④}$$

Sub. eq ④ in ①

$$\Rightarrow v_o = -\frac{R_f}{R_1} \left[ \frac{V_i}{1 - j \left( \frac{f_L}{f} \right)} \right]$$

$$\Rightarrow \frac{v_o}{V_i} = -\frac{R_f}{R_1} \left[ \frac{1}{1 - j \left( \frac{f_L}{f} \right)} \right]$$

$$\text{magnitude is } \left| \frac{v_o}{V_i} \right| = -\frac{R_f}{R_1} \cdot \frac{1}{\sqrt{1 + \left( \frac{f_L}{f} \right)^2}}$$

$$= -\frac{R_f}{R_1} \cdot \frac{1}{\sqrt{1+0}} \quad [ \because f \ll f_L \quad (\text{or}) \quad \frac{f_L}{f} \gg 1 ]$$

$$\boxed{A_{CL} = -\frac{R_f}{R_1}} \quad \text{--- ⑤}$$


The coupling capacitor  $C_C$  controls the low frequency limit.

## 2. Non-Inverting A.C Amplifier :-

we know that,

$$\frac{V_o}{V_s} = 1 + \frac{R_f}{R_1}$$
 
$$\Rightarrow V_o = \left(1 + \frac{R_f}{R_1}\right) V_s \quad \text{--- (6)}$$



sub. eqn (4) in (6)

$$\Rightarrow V_o = \left(1 + \frac{R_f}{R_1}\right) \left[ \frac{V_i}{1 - j(\frac{f_L}{f})} \right]$$

$$\Rightarrow \frac{V_o}{V_i} = \left(1 + \frac{R_f}{R_1}\right) \left[ \frac{1}{1 - j(\frac{f_L}{f})} \right]$$

$$\text{magnitude, } \left| \frac{V_o}{V_i} \right| = \left(1 + \frac{R_f}{R_1}\right) \frac{1}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

If  $f \ll f_L$  (or)  $\frac{f_L}{f} \gg 1$

$$\Rightarrow A = 1 + \frac{R_f}{R_1} \quad \text{--- (7)}$$

The lower cut-off frequency again controlled by coupling capacitor  $C_C$ .

## 3. A.C Voltage follower :-

The capacitors used to

Allows A.C signals only.

→ The output voltage

follows the Input.


 


Fig :- A.C Voltage follower.

The frequency response characteristics are

 - The frequencies below  $f_L$  can not be allowed so it indicates "stop band" and allows only higher frequencies indicates "pass band".



Voltage follower (Buffer) :-


The output follows Input so it gives voltage follower.

$$\text{From fig. } V_B = V_{in}$$

$$\Rightarrow V_A = V_{in} \quad [\because V_A = V_B]$$

$$\Rightarrow V_A = V_B = V_{in}$$

$$\Rightarrow \boxed{V_o = V_{in}}$$

 

The characteristics are

- i) Gain = 1
- ii) Input resistance ' $\infty$ '
- iii) Output resistance '0'.

 


Fig :- V-I converter with grounded load.

From the figure,

$$i_1 = \frac{V_{in} - V_1}{R} \quad \text{and} \quad i_2 = \frac{V_o - V_1}{R}$$

Apply KCL at Node 'a'

$$i_1 + i_2 = i_L \quad \text{--- (1)}$$

$$\Rightarrow \frac{V_{in} - V_1}{R} + \frac{V_o - V_1}{R} = i_L$$

$$\Rightarrow V_{in} - V_1 + V_o - V_1 = i_L R$$

$$\Rightarrow V_{in} + V_o - 2V_1 = i_L R \quad \text{--- (2)}$$

$$\Rightarrow V_1 = \frac{V_{in} + V_o - i_L R}{2} \quad \text{--- (3)}$$

In this circuit, OP-Amp is connected to Non-Inverting mode

we know that gain of the circuit is

$$A = 1 + \frac{R_f}{R}$$

In this circuit,  $R_f = R$

$$\Rightarrow A = 1 + \frac{R}{R} \Rightarrow A = 2 \quad \Rightarrow \frac{V_o}{V_{in}} = 2 \quad \left[ \because A = \frac{V_o}{V_{in}} \right]$$



$$\Rightarrow V_0 = 2V_1 \quad \text{--- (3)}$$

sub. eqn (3) in (2)

$$\Rightarrow V_{in} + 2V_1 - 2V_1 = i_L R$$

$$\Rightarrow V_{in} = i_L R \quad \Rightarrow \boxed{i_L = \frac{V_{in}}{R}}$$

### Applications:-

- used in LEDs.
- used as Low voltage dc and AC voltmeter
- zener diode tester.

### current to voltage converter (Transresistance Amplifier) :-

The circuit which converts the input current into output voltage is called current to voltage converter.

→ The output voltage of I/V converter is directly proportional to input current.

From fig.  $V_B = 0$

concept of virtual ground

$$V_A = 0$$


At node A,

$$I_i = \frac{V_A - V_{out}}{R_f} = \frac{0 - V_{out}}{R_f} = -\frac{V_{out}}{R_f}$$

$$\Rightarrow \boxed{V_{out} = -I_i R_f}$$

$$\Rightarrow V_{out} \propto I_i$$

 Thus, output voltage is proportional to input current and circuit works as current to voltage converter. It also referred as current controlled voltage source (CCVS).




### Applications:-

1. photo diode detector
2. photo FET detector
 
### photo diode detector:-

The photo diode produces electrical current in response to Incident light. This current flows through  $R_f$ . The voltage across  $R_f$ , the output voltage is proportional to diode current.



### Instrumentation Amplifier :-

The Amplifier which is used for low level amplification with high CMRR, high Input Impedance to avoid loading, low power consumption and some other features is called Instrumentation Amplifier.

- It is also called data Amplifier.
- The important features (or) characteristics of Instrumentation Amplifier are

- i) high gain Accuracy
- ii) high CMRR
- iii) High Input Impedance
- iv) Low Output Impedance
- v) Low Power consumption
- vi) high gain stability with low temp. coefficient
- vii) High slew rate

Fig. shows difference Amplifier.  
we know that,

From difference amplifier

$$V_o = \frac{R_f}{R_1} (V_2 - V_1) \quad \text{--- ①}$$

 


Fig:- Differential Amplifier using single OP-AMP

Three OP-Amp Instrumentation Amplifier :-

This circuit provides high input resistance for accurate measurement of signals from transducers.

 


Fig:- Three OP-Amp Instrumentation Amplifier

It contains 2 stages, input and output stage

→ Input stage contains 2-OPamps A<sub>1</sub>, A<sub>2</sub> are used for high input impedance. [2-OPamps are identical, IIP's connected to Non-Inverting terminal]

→ Output stage contains OP-amp A<sub>3</sub> it's difference Amplifier.

### Analysis :-

From the circuit, output stage is similar to basic difference

Amplifier (or) subtractor.

$$\text{w.r.t } V_o = \frac{R_f}{R_i} (V_2 - V_1) \quad \text{--- (2)}$$

Now consider first stage (or) input stage.

→ Node 'A' potential of


OP-AMP  $A_1$  is  $V_1$ . So, Node 'B'

is also  $V_1$ . Hence potential of  $G_1$  is  $V_1$ .

→ Node 'D' potential of OP-amp

$A_2$  is  $V_2$ . So, Node 'C' also  $V_2$

 and hence potential of  $H$  is  $V_2$ .  $V_2$



→ Input current of OP-amp  $A_1, A_2$  both are zero. Hence current  $I$  remains same through  $R_{f1}, R_G, R_{f2}$ .

Apply ohm's law between nodes E, F we get,

$$I = \frac{V_{01} - V_{02}}{R_{f1} + R_G + R_{f2}} \quad \text{--- (3)}$$

Let  $R_{f1} = R_{f2} = R_f$

$$\Rightarrow I = \frac{V_1 - V_2}{2R_f + R_G} \quad \text{--- (4)}$$

At Nodes  $G_1$  and  $H$ ,

$$I = \frac{V_{G_1} - V_H}{R_G} = \frac{V_1 - V_2}{R_G} \quad \text{--- (5)} \quad [ \because V_{G_1} = V_1 \\ V_H = V_2 ]$$

Evaluating eq (4), (5)

$$\frac{V_{01} - V_{02}}{2R_f + R_G} = \frac{V_1 - V_2}{R_G}$$

$$\Rightarrow \frac{V_{O2} - V_{O1}}{2R_f + R_G} = \frac{V_2 - V_1}{R_G} \quad \text{--- ⑥}$$

$$\Rightarrow V_{O2} - V_{O1} = \frac{(2R_f + R_G)(V_2 - V_1)}{R_G} \quad \text{--- ⑦}$$


Sub. eq ⑦ in eq ②,

$$\Rightarrow V_o = \frac{R_f}{R_i} \left[ \frac{(2R_f + R_G)(V_2 - V_1)}{R_G} \right]$$

$$V_o = \frac{R_f}{R_i} \left( 1 + \frac{2R_f}{R_G} \right) (V_2 - V_1) \quad \text{--- ⑧}$$

This is the overall gain of the circuit.

 Instrumentation amplifier using transducer bridge :-



$R_T$  be the resistance of the transducer device which is one of the arms of the resistive bridge, while  $\Delta R$  is the change in resistance  $R_T$ . So, effective resistance of transducer is  $R_T \pm \Delta R$ .

The bridge balanced condition, is

$$\frac{R_C}{R_B} = \frac{R_T}{R_A} \quad \text{--- (1)}$$

This condition is generally established by the designer and depends on transducer device characteristics, type of the physical energy to be measured and desired application.

When there is a change in physical quantity to be measured, the voltage  $V_a$  no longer remains same as  $V_b$ . This is due to fact that the resistance of transducer device changes from  $R_T$  to  $R_T + \Delta R$ . and hence balancing of the bridge gets disturbed. This produces differential input for the Instrumentation Amplifier.

The resistances  $R_B, R_C$  are constant and voltage  $V_b$  will remain same,

$$V_b = \frac{R_B \cdot V_{dc}}{R_B + R_C} \quad \text{--- (2)}$$

Due to change in resistance of the transducer device,  $V_a$  becomes

$$V_a = \frac{R_A (V_{dc})}{R_A + R_T + \Delta R} \quad \text{--- (3)}$$

$$\therefore V_{ab} = V_b - V_a$$

$$= \frac{R_B \cdot V_{dc}}{R_B + R_C} - \frac{R_A \cdot V_{dc}}{R_A + R_T + \Delta R} \quad \text{--- (4)}$$

If  $R_A = R_B = R_C = R_T = R$ , then

$$V_{ab} = \frac{R V_{dc}}{2R} - \frac{R V_{dc}}{2R + \Delta R}$$

$$V_{ab} = \frac{R V_{dc} (2R + \Delta R) - R V_{dc} (2R)}{2R(2R + \Delta R)}$$

$$= \frac{2R V_{dc} + R \Delta R V_{dc} - 2R V_{dc}}{2R(2R + \Delta R)}$$

$$\Rightarrow V_{ab} = \frac{\Delta R V_{dc}}{2(2R + \Delta R)} \quad \text{--- (5)}$$

The +ve  $V_{ab}$  i.e.  $V_b - V_a$  indicates  $V_b > V_a$

Now the gain of 1<sup>st</sup> stage of Instrumentation amplifier is unity  
as its voltage follower circuit and gain of 2<sup>nd</sup> stage is  $-R_f/R_1$

$$\begin{aligned} \therefore V_o &= V_{ab} \times \left( -\frac{R_f}{R_1} \right) \\ &= -\frac{R_f}{R_1} \left[ \frac{\Delta R V_{dc}}{2(2R + \Delta R)} \right] \end{aligned}$$

AS  $\Delta R \ll 2R$ , neglecting it

$$\Rightarrow V_o = -\frac{R_f}{R_1} \frac{\Delta R}{4R} \cdot V_{dc} \quad \text{--- (6)}$$

thus, the output voltage is proportional to change in resistance  $\Delta R$ . Thus the meter connected to output can be calibrated in terms of units of physical quantity to be measured.

In general, gain of Instrumentation amplifier whether it is any instrumentation Amplifier circuit,

$$V_o = \frac{A \Delta R}{4R} V_{dc} \quad \text{--- (7)} \qquad \left[ \because A = -\frac{R_f}{R_1} \right]$$



### Applications:-

- 1) Temperature indicator
- 2) Temperature controller
- 3) Light Intensity meter
- 4) Analog weight scale.

### Comparators:-

A circuit which compares a signal voltage applied at one input and reference voltage at other input and produces output voltage.

The output voltage is high value (or) low value depending upon input.

$V_N$  → Voltage of Inverting terminal

$V_P$  → Voltage of Non Inverting terminal

Two voltages compared with each other

and  $V_o$  is either  $+V_{sat}$  (or)  $-V_{sat}$ .

 


Fig :- op-amp as comparator


Depending upon terminals, they are classified into 2 types

i) Non Inverting comparator

ii) Inverting comparator

### 1. Inverting comparator :-

The Input Voltage is applied to Inverting terminal and reference Voltage is applied to Non-Inverting terminal.

 


case 1 :-  $V_{in} < V_{ref}$

In this case, the output voltage  $V_o = +V_{sat} (+V_{cc})$


case 2 :-  $V_{in} > V_{ref}$

In this case, the output voltage  $V_o = -V_{sat} (-V_{ee})$

### Input and output waveforms :-

 


a) Taking +ve  $V_{ref}$

 

b) Taking  $-V_{ref}$


### Transfer characteristics :-

 
 
### 2. Non-Inverting comparator :-

In Non-Inverting comparator,

Input  $V_{in}$  applied to  
Non-Inverting terminal and  
 $V_{ref}$  applied to Inverting terminal.



case ①  $V_{in} > V_{ref}$

In this case, output voltage  $V_o = V_{sat} (+V_{cc})$

case ②  $V_{in} < V_{ref}$

In this case, output voltage  $V_o = -V_{sat} (-V_{ee})$

### Input and output waveforms :-

 


Fig :- Taking  $+V_{ref}$


 


Fig :- Taking  $-V_{ref}$

### Transfer characteristics:-

 


### Practical comparator:-

The circuit consists of protective diodes and Potentiometer to adjust the reference voltage.

The diodes  $D_1$ ,  $D_2$  are connected to protect the op-amp from damage due to Excessive input Voltage  $V_{in}$ ,  $V_{im}$ .

 → From these diodes, the difference input voltage  $V_{id}$  always less than  $0.7V$  (or)  $-0.7V$



→ In case of Excess Input voltage, difference Input voltage  $V_{id}$  of the OP-amp is clamped to either  $0.7V$  (or)  $-0.7V$  due to forward biasing of diodes hence these diodes are called clamp diodes.

### Characteristics of comparator :-

- Accuracy
- Logic threshold
- Strobe function
- Response time
- positive output level
- negative output level
- Strobe current
- Strobe release time
- saturation voltage

### Applications of comparator :-

#### 1. zero crossing detector:-

During +ve half cycle, the input voltage is +ve ie above reference Voltage the output is  $V_{sat}$ .

- During -ve half cycle, Input voltage  $v_{in}$  is -ve i.e. below reference voltage the output voltage is  $-V_{sat}$ .

- The output voltage switches between  $+V_{sat}$  and  $-V_{sat}$  whenever the input signal crosses the zero level.


 


Fig :- zero-crossing detector

 

b) output waveform

#### Application :-

- Sine wave to square wave converter.


#### 2) Level detector :-

The Non-Inverting terminal is biased to  $V_{level}$  voltage which is drop across  $R_2$  can be set to a level to be detected.

- As  $v_{in}$  increases above  $V_{level}$ , output changes from  $+V_{sat}$  to  $-V_{sat}$ .

- As  $v_{in}$  falls below  $V_{level}$ , output changes from

$-V_{sat}$  to  $+V_{sat}$ .

 


 



Fig:- waveforms of voltage level detector
 
### 3. Time marker generator :-

In this circuit, output of zero crossing detector is differentiated using RC circuit. This produces train of +ve & -ve pulses denoted as  $V_{01}$  &  $-V_{01}$ .



 Then the output is a train of +ve pulses.




## Regenerative comparator (schmitt trigger) :-

It is used to avoid unwanted noise, which is basically uses a +ve feed back.
 
### 1. Inverting schmitt trigger circuit:

→ As the Input applied to Inverting terminal, produces opposite polarity output.



→ This is feed back to Non-Inverting Input which is same polarity of output.

case 1 :-  $V_{in} > V_{ref}$

The output goes to  $-V_{sat}$ .

case 2 :-  $V_{in} < V_{ref}$

The output goes to  $+V_{sat}$ .

→ The output voltage is always at  $+V_{sat}$  and  $-V_{sat}$ .

Apply voltage divider at  $V_{ref}$ , then

$$+V_{ref} = \frac{R_2}{R_1 + R_2} \cdot V_o = \frac{V_{sat} R_2}{R_1 + R_2} \quad [ \because V_o = +V_{sat} ]$$

and

$$-V_{ref} = \frac{V_o R_2}{R_1 + R_2} = \frac{-V_{sat} R_2}{R_1 + R_2} \quad [ \because V_o = -V_{sat} ]$$

→  $+V_{ref}$  is +ve saturation when  $V_o = +V_{sat}$  is called upper threshold voltage ( $V_{UT}$ ).

→  $-V_{ref}$  is -ve saturation when  $V_o = -V_{sat}$  is called lower threshold voltage ( $V_{LT}$ ).



then,  $V_{UT} = \frac{+V_{sat} R_2}{R_1 + R_2}$

$$V_{LT} = -\frac{V_{sat} R_2}{R_1 + R_2}$$

Transfer characteristics :-

→ The graph is drawn between Input Voltage & output voltage is called transfer characteristics.

→ Output changes its state, there is an input voltage crosses any of the threshold voltage levels. This is called "Hysteresis". It is also called dead band (or) dead zone.

→ Difference between  $V_{UT}$  and  $V_{LT}$  is called width of hysteresis denoted by  $H$ .

$$H = V_{UT} - V_{LT}$$

$$= \frac{V_{sat} R_2}{R_1 + R_2} - \left[ -\frac{V_{sat} R_2}{R_1 + R_2} \right]$$

$$H = \frac{2V_{sat} R_2}{R_1 + R_2}$$

→ As  $V_{in} > V_{UT}$  → Output voltage  $V_o = -V_{sat}$

→ As  $V_{in} < V_{LT}$  → Output voltage  $V_o = +V_{sat}$

→  $V_{LT} < V_i < V_{UT}$  →  $V_o$  = Previous state achieved.

 
 


Fig :- Input & output waveforms

## Q. Non Inverting schmitt trigger :-

Input applied to Non-Inverting terminal.

→ AS  $V_{in} > V_{UT}$  → output voltage  $V_o = +V_{sat}$

→ AS  $V_{in} < V_{UT}$  → output voltage  $V_o = -V_{sat}$

Transfer characteristics :-

From fig, at Point 'A',

$$V_A = I_{in} R_2 \\ = V_{UT}$$

$$\text{From fig, } I_{in} = \frac{V_A + V_o}{R_1} = \frac{0 + V_o}{R_1} = \frac{V_o}{R_1} \quad [\because V_A = 0] \\ = \frac{+V_{sat}}{R_1}$$

$$\therefore V_{UT} = I_{in} R_2$$

$$= V_{sat} \cdot \frac{R_2}{R_1}$$

$$\text{and } V_{LT} = \frac{R_2}{R_1} (-V_{sat})$$

$$\therefore H = V_{UT} - V_{LT}$$

$$= V_{sat} \frac{R_2}{R_1} - \left[ (-V_{sat}) \frac{R_2}{R_1} \right]$$

$H = 2V_{sat} \frac{R_2}{R_1}$


 
 
 


Fig:- Input and output waveform

## Schmitt trigger with different UTP and LTP levels :-

In this circuit, an additional voltage source of 'x' volts connected in series between  $R_1$  & ground.  
 → The voltage  $V_i$  depends on 'x' and decides UTP and LTP levels.

APPLY KVL to output circuit,

 

$$V_o - IR_2 - IR_1 - x = 0$$

$$\Rightarrow V_o = I(R_1 + R_2) + x$$

$$\Rightarrow I = \frac{V_o - x}{R_1 + R_2} \quad \text{--- (1)}$$

$$\text{and } V_i = IR_1 + x \quad \text{--- (2)}$$

sub. eq(1) in (2)

$$V_i = \left[ \frac{V_o - x}{R_1 + R_2} \right] R_1 + x \quad \text{--- (3)}$$

FOR  $V_i = V_{UT}$ ,  $V_o = +V_{sat}$

$$V_{UT} = \left[ \frac{V_{sat} - x}{R_1 + R_2} \right] R_1 + x \quad \text{--- (4)}$$

FOR  $V_i = V_{LT}$ ,  $V_o = -V_{sat}$

$$V_{LT} = \left[ \frac{-V_{sat} - x}{R_1 + R_2} \right] R_1 + x \quad \text{--- (5)}$$

subtracting eq(5) from eq(4)

$$\begin{aligned} V_{UT} - V_{LT} &= \frac{V_{sat} - x}{R_1 + R_2} \cdot R_1 + x - \left[ \frac{-V_{sat} - x}{R_1 + R_2} \cdot R_1 + x \right] \\ &= \frac{2V_{sat}R_1}{R_1 + R_2} \quad \text{--- (6)} \end{aligned}$$

From eq(6),  $R_{comp} = R_1 // R_2$

## Multi vibrators using op-amp :-

These are used in timing applications. The multivibrators are classified as

1. mono stable multivibrators
2. Astable multivibrators

### 1. mono stable multivibrators :- (or) one-shot multivibrator :-

~~It contains one stable state and one quasi stable state.~~  
when an External trigger is applied, the output changes its state from stable state to quasi stable state. after some time it returns back to its original state. usually, the charging and discharging of a capacitor provides this internal trigger signal.

 


Fig :- OP-AMP monostable multivibrator

### Operation:-


Let us assume that output  $V_0$  is at  $+V_{sat}$  i.e. in stable state. The diode  $D_1$  conducts and voltage across capacitor is  $V_c$ .

gets clamped to  $0.7V$ . Voltage at non inverting terminal is  $\beta V_{sat}$  in the stable state.

→ If  $V_t$ , -ve voltage applied to Non-Inverting terminal then the output of OP-Amp changes its state from  $+V_{sat}$  to  $-V_{sat}$ . diode is reverse biased and capacitor starts charging exponentially to  $-V_{sat}$ . The voltage at Non Inverting terminal is now  $-\beta V_{sat}$ .

→ When the capacitor voltage  $V_c$  becomes more negative than  $-\beta V_{sat}$ , output of op-amp changes its state back to  $+V_{sat}$ .

waveforms:-

 

Expression for pulse width ( $T$ ):-

$$\text{w.r.t } V_0 = V_f - (V_f - V_{in}) e^{-t/RC} \quad \dots \textcircled{1}$$

$$\text{where, } V_0 = V_c, \quad V_{in} = V_{D1}, \quad V_f = -V_{sat}$$

$$\Rightarrow V_c = -V_{sat} - (-V_{sat} - V_{D1}) e^{-t/RC}$$

$$\text{At } t=T, \quad V_c = -\beta V_{sat}$$

$$\Rightarrow -\beta V_{sat} = -V_{sat} + (V_{sat} + V_{D1}) e^{-T/RC}$$

$$\Rightarrow (V_{sat} + V_{D1}) e^{-T/RC} = -V_{sat} \cdot \beta + V_{sat}$$

$$= V_{sat} (1 - \beta)$$

$$\Rightarrow e^{-T/RC} = \frac{V_{sat} (1 - \beta)}{V_{sat} + V_{D1}}$$

$$\Rightarrow e^{T/RC} = \frac{V_{sat} + V_{D1}}{V_{sat} (1 - \beta)}$$

Apply ' $\ln$ ' on both sides,

$$T/RC = \ln \left( \frac{V_{sat} + V_{D1}}{V_{sat} (1 - \beta)} \right)$$

$$\Rightarrow T = RC \ln \left( \frac{V_{sat} + V_{D1}}{V_{sat} (1 - \beta)} \right) = RC \ln \left( \frac{\frac{V_{sat} (1 + \frac{V_{D1}}{V_{sat}})}{V_{sat}}}{V_{sat} (1 - \beta)} \right)$$

$$T = RC \ln \left( \frac{1 + \frac{V_{D1}}{V_{sat}}}{1 - \beta} \right) \quad \dots \textcircled{2}$$

$$\text{At } V_{sat} \gg V_{D1}, \text{ from fig. } \beta = \frac{R_2}{R_1 + R_2},$$

$$\text{If } R_1 = R_2 \text{ then } \beta = \frac{R_1}{2R_1} = \frac{1}{2} = 0.5$$

sub. 'β' value in eq ②,


$$\Rightarrow T = RC \ln \left( \frac{1}{1-0.5} \right) \quad [ \because V_{sat} \gg V_{D1} ]$$
$$= RC \ln \left[ \frac{1}{0.5} \right]$$
$$= RC \ln(2)$$

$T = 0.69 RC$

 2. Astable multivibrator :- (or) free running multivibrator :-

→ It contains 2 quasi-stable states and no stable states i.e. circuit oscillate between 2 quasi stable states.

→ No external trigger is applied to changes the states.



The circuit looks like a comparator (schmitt trigger) except that Input voltage is replaced by a capacitor.

i) when  $V_0$  is at  $+V_{sat}$

Feed back voltage is called upper threshold voltage  $V_{UT}$

$$\text{i.e. } V_{UT} = \frac{R_1 (+V_{sat})}{R_1 + R_2} \quad \text{--- ①}$$

ii) when  $V_0$  is at  $-V_{sat}$


Feed back voltage is called lower threshold voltage  $V_{LT}$

$$\text{i.e. } V_{LT} = \frac{R_1 (-V_{sat})}{R_1 + R_2} \quad \text{--- ②}$$



 
i) when  $V_o = +V_{sat}$  :-

In this case, capacitor starts charging towards  $+V_{sat}$  through the feedback path provided by resistor  $R_f$  to inverting input.



 
ii) when  $V_o = -V_{sat}$  :-

In this case, capacitor starts discharging towards  $-V_{sat}$  through the feedback path provided by resistor  $R_f$ .



Output waveforms :-

 The initial voltage  $V_{LT}$  & capacitor discharge from  $V_{LT}$  to 0V and recharge to  $V_{LT}$  the process is repeating.



Frequency of oscillation :-

We know that,

$$V_o = V_f - (V_f - V_{im}) e^{-t/RC} \quad \text{--- (1)}$$

From fig,  $V_{im} = V_{LT}$ ,  $V_f = +V_{sat}$ ,  $V_o = V_{LT}$

$$V_{UT} = V_{sat} - (V_{sat} - V_{LT}) e^{-T_1/RC} \quad [ \because t = T_1 ]$$

$$\Rightarrow (V_{sat} - V_{LT}) e^{-T_1/RC} = V_{sat} - V_{UT}$$

$$\Rightarrow e^{-T_1/RC} = \frac{V_{sat} - V_{UT}}{V_{sat} - V_{LT}}$$

$$\Rightarrow e^{T_1/RC} = \frac{V_{sat} - V_{LT}}{V_{sat} - V_{UT}}$$

Apply 'ln' on both sides,

$$\frac{T_1}{RC} = \ln \left( \frac{V_{sat} - V_{LT}}{V_{sat} - V_{UT}} \right)$$

$$\Rightarrow T_1 = RC \ln \left( \frac{V_{sat} - V_{LT}}{V_{sat} - V_{UT}} \right) \quad \text{--- (2)}$$

consider  $T = 2T_1$ , because capacitor charge from  $V_{UT}$  to  $V_{LT}$   
is same as time required for charging capacitor from  $V_{LT}$  to  $V_{UT}$

$$\Rightarrow T = 2RC \ln \left[ \frac{V_{sat} - V_{LT}}{V_{sat} - V_{UT}} \right] \quad \text{--- (3)}$$

$$\text{and } f = \frac{1}{2RC \ln \left[ \frac{V_{sat} - V_{LT}}{V_{sat} - V_{UT}} \right]}$$

sub.  $V_{UT}$  and  $V_{LT}$  in eq (3),

$$T = 2RC \ln \left[ \frac{\frac{V_{sat} - (R_1 \times V_{sat}) / R_1 + R_2}{V_{sat} - (R_1 \times V_{sat}) / R_1 + R_2}}{\frac{V_{sat} - (R_1 \times V_{sat}) / R_1 + R_2}{V_{sat} - (R_1 \times V_{sat}) / R_1 + R_2}} \right]$$


magnitudes of  $+V_{sat}$  &  $-V_{sat}$  are equal

$$\Rightarrow T = 2RC \ln \left[ \frac{\frac{V_{sat} \left( 1 + \frac{R_1}{R_1 + R_2} \right)}{V_{sat} \left( 1 - \frac{R_1}{R_1 + R_2} \right)}}{\frac{V_{sat} \left( 1 - \frac{R_1}{R_1 + R_2} \right)}{V_{sat} \left( 1 + \frac{R_1}{R_1 + R_2} \right)}} \right]$$

$$\Rightarrow T = 2RC \ln \left( \frac{2R_1 + R_2}{R_2} \right)$$
 
## Triangular / rectangular wave generator :-

The output of Integrator is triangular if its input is square wave input. While output of a Schmitt trigger is square wave for any input. Thus if output of Schmitt trigger is applied to Input of Integrator and output of Integrator as input to Schmitt trigger then circuit works as triangular / rectangular wave generator.



The OP-amp A circuit is Schmitt trigger while OP-amp B is an Integrator. The output of Schmitt trigger is rectangular wave applied to Inverting input of Integrator and produces triangular wave output.

### Operation:-

Let the output of Schmitt trigger is  $+V_{sat}$ . This forces current  $+V_{sat}/R_1$  through  $C_1$ , charging  $C_1$  with polarity +ve to left & -ve to right.


It produces -ve going ramp at its output, for the interval  $t_1$  to  $t_2$

→ At  $t_2$ , when ramp voltage equal to LTP of schmitt trigger, output of schmitt trigger changes its state from  $+V_{sat}$  to  $-V_{sat}$ .

→ Now direction of current through C, reverses. It discharges and recharges in opposite direction with polarity +ve to right and -ve to left. This produces +ve going ramp at its output, for the interval  $t_2$  to  $t_3$ .

→ At  $t_3$ , when ramp voltage equal to UTP of schmitt trigger, output of schmitt trigger changes its state from  $-V_{sat}$  to  $+V_{sat}$ .

wave forms :-

 

when the Schmitt trigger output is at  $+V_{sat}$ , effective voltage at point 'P' is

$$-V_{ramp} + \frac{R_2}{R_2+R_3} [ +V_{sat} - (-V_{ramp}) ] \quad \text{--- (1)}$$

when the effective voltage at 'P' becomes zero, ie

$$-V_{ramp} + \frac{R_2}{R_2+R_3} [ +V_{sat} - (-V_{ramp}) ] = 0$$

---


$$\frac{-V_{ramp}}{R_2+R_3} (V_{ramp}) + \frac{R_2}{R_2+R_3} (V_{sat}) = 0$$

$$V_{ramp} \left[ -1 + \frac{R_2}{R_2+R_3} \right] = -\frac{R_2}{R_2+R_3} (V_{sat})$$

$$V_{ramp} \left[ \frac{-R_2-R_3+R_2}{R_2+R_3} \right] = -\frac{R_2}{R_2+R_3} (V_{sat})$$

$$V_{ramp} \left[ \frac{-R_3}{R_2+R_3} \right] = -\frac{R_2}{R_2+R_3} V_{sat}$$

$$\Rightarrow -V_{ramp} = -\frac{R_2}{R_3} V_{sat} \quad \text{--- (2)}$$

If output is at  $-V_{sat}$ ,  $+V_{ramp} = -\frac{R_2}{R_3} (-V_{sat}) \quad \text{--- (3)}$

Peak to Peak amplitude of triangular wave is given by

$$V_{out(P-P)} = +V_{ramp} - (-V_{ramp})$$

$$= -\frac{R_2}{R_3} V_{sat} - \left[ -\frac{R_2}{R_3} V_{sat} \right] \quad \text{--- (4)}$$

If  $|+V_{sat}| = |-V_{sat}|$ , then

$$V_{out(P-P)} = \frac{R_2}{R_2} V_{sat} + \frac{R_2}{R_3} V_{sat} = \frac{2R_2}{R_3} V_{sat} \quad \text{--- (5)}$$

The time taken by the output to swing from  $-V_{\text{ramp}}$  to  $+V_{\text{ramp}}$  is equal to half the time period  $T/2$ .

$$\begin{aligned} V_{\text{out (P-P)}} &= -\frac{1}{R_1 C_1} \int_0^{T/2} (-V_{\text{sat}}) dt \\ &= \frac{V_{\text{sat}}}{R_1 C_1} \int_0^{T/2} dt = \frac{V_{\text{sat}}}{R_1 C_1} (t) \Big|_0^{T/2} \\ &= \frac{V_{\text{sat}}}{R_1 C_1} \left(\frac{T}{2}\right) \quad \text{--- (6)} \end{aligned}$$

$$\Rightarrow T = \frac{V_{\text{out (P-P)}} \cdot 2 R_1 C_1}{V_{\text{sat}}} \quad \text{--- (7)}$$

sub. eq (5) in (7),


$$T = \frac{\left(\frac{2 R_2}{R_3} V_{\text{sat}}\right) \cdot 2 R_1 C_1}{V_{\text{sat}}}$$

$$T = \frac{4 R_1 R_2 C_1}{R_3} \quad \text{--- (8)}$$

$\therefore$  frequency of oscillation

$$f_0 = \frac{R_3}{4 R_1 R_2 C_1} \quad \text{--- (9)}$$

 Another form of Triangular wave generator:-



### Log Amplifiers:-


The circuit whose output is proportional to the logarithm of applied input voltage is called "logarithmic Amplifier".

#### i) Log Amplifier using diode:-

From fig,  $V_A = 0$

concept of virtual ground

$$V_B = 0$$

 

$$\therefore I = \frac{V_{im} - V_B}{R} = \frac{V_{im}}{R} \quad \text{--- (1)}$$

w.k.t diode equation,  $I = I_0 (e^{\frac{V_B}{\eta V_T}} - 1)$

$$\text{forward current is, } I_f = I_0 e^{\frac{V_B}{\eta V_T}} \quad \text{--- (2)} \quad [\because I \ll e^{\frac{V_B}{\eta V_T}}]$$

Taking 'ln' on both sides,

$$\begin{aligned} \ln[I_f] &= \ln[I_0 e^{\frac{V_B}{\eta V_T}}] \\ &= \ln[I_0] + \ln[e^{\frac{V_B}{\eta V_T}}] \\ &= \ln[I_0] + \frac{V_B}{\eta V_T} \end{aligned}$$

$$\Rightarrow \frac{V_B}{\eta V_T} = \ln[I_f] - \ln[I_0]$$

$$\Rightarrow V_B = \eta V_T [\ln[I_f] - \ln[I_0]]$$

$$\Rightarrow V_B = \eta V_T \ln \left[ \frac{I_f}{I_0} \right] \quad \text{--- (3)}$$

From fig,  $I_f = V_B - V_o$

$$= 0 - V_o = -V_o \quad \text{--- (4)}$$

(or)  $\because V_B = V_i + V_o$   
 $0 = V_i + V_o \Rightarrow V_i = -V_o$

$$\therefore \text{eq(3) can be } -V_o = \eta V_T \ln \left[ \frac{I_f}{I_0} \right] \quad \text{--- (5)}$$

sub.  $I_f = I = \frac{V_{in}}{R}$  then eq(5) changes to

$$V_o = -\eta V_T \ln \left[ \frac{V_{in}}{R I_0} \right] \quad \text{--- (6)}$$

consider  $V_{ref} = R \cdot I_0$  then eq(6) changes to

$$\frac{V_{ref}}{V_{in}} V_o = -\eta V_T \ln \left[ \frac{V_{in}}{V_{ref}} \right] \quad \text{--- (7)}$$

Thus, output voltage is proportional to logarithm of input voltage  
The circuit gives natural  $\log(\ln)$ , one can find  $\log_{10}$  by

proper scaling as,

$$\log_{10} x = 0.4343 \ln(x)$$

### ii) Log Amplifier using transistor:-


From fig,  $V_A = 0$

concept of virtual ground

$$V_B = 0$$

and current,
 
$$I = \frac{V_{in} - V_B}{R} = \frac{V_{in}}{R} \quad \text{--- (1)}$$



w.r.t., the equation for collector current in BJT,

$$I_C = I_S (e^{V_{BE}/V_T} - 1)$$

$$I_C = I_S (e^{V_{BE}/V_T}) \quad \left[ \because I \ll e^{V_{BE}/V_T} \right]$$

Taking ' $\ln$ ' on both sides

$$\ln(I_C) = \ln(I_S (e^{V_{BE}/V_T}))$$



$$\Rightarrow \ln\left(\frac{I_C}{I_S}\right) = \frac{V_{BE}}{V_T}$$

$$\Rightarrow V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) \quad \text{--- (2)}$$

From fig,  $V_B = V_0 + V_{BE}$

$$0 = V_0 + V_{BE}$$

$$\Rightarrow V_0 = -V_{BE} \quad \text{--- (3)}$$

and current  $I = I_C = \frac{V_{in}}{R} \quad \text{--- (4)}$


Sub. eq (3), (4) in eq (2)

$$\Rightarrow -V_0 = V_T \ln\left(\frac{V_{in}}{R I_S}\right) \quad \text{--- (5)}$$

Let  $I_S R = V_{ref}$ , then eq (5) changes to

$$V_0 = -V_T \ln\left(\frac{V_{in}}{V_{ref}}\right)$$
 
### iii) Temperature compensated Log Amplifier :-



→ In this technique, 2 log amplifiers are used · one used for reference voltage  $V_{ref}$  and other used for  $V_{in}$ .

→ Two transistors used in the two log Amplifier circuits are integrated close together in the same silicon wafer. This provides a close match of saturation currents and ensures good thermal tracking.

$$\text{Assume , } I_{S_1} = I_{S_2} = I_S \quad \text{--- ①}$$

$$\text{voltages } V_{O_1} = -V_T \ln \left[ \frac{V_{in}}{R_1 I_S} \right] \quad \text{--- ②}$$

$$V_{O_2} = -V_T \ln \left[ \frac{V_{ref}}{R_1 I_S} \right] \quad \text{--- ③}$$

OP-AMP A<sub>3</sub> act as difference Amplifier,

$$\begin{aligned} V_x &= V_{O_2} - V_{O_1} \\ &= -V_T \ln \left[ \frac{V_{ref}}{R_1 I_S} \right] - \left[ -V_T \ln \left( \frac{V_{in}}{R_1 I_S} \right) \right] \\ &= -V_T \left[ \ln \left( \frac{V_{ref}}{R_1} \right) + \ln \left( \frac{1}{I_S} \right) - \ln \left( \frac{V_{in}}{R_1} \right) - \ln \left( \frac{1}{I_S} \right) \right] \\ &= -V_T \left[ \ln \left( \frac{V_{ref}}{R_1} \right) + \ln \left( \frac{R_1}{V_{in}} \right) \right] \end{aligned}$$

$$V_x = -V_T \ln \left( \frac{V_{ref}}{V_{in}} \right) \quad \text{--- ④}$$

(or)

$$V_x = V_T \ln \left[ \frac{V_{in}}{V_{ref}} \right] \quad \text{--- ⑤}$$

$V_{ref}$  is decided by external battery & it is not temp. dependent.

Last stage of OP-AMP  $A_4$  it act as Non-Inverting Amplifier with gain of  $(1 + \frac{R_2}{R_T})$

$$\therefore \text{output voltage } V_o = V_x \left(1 + \frac{R_2}{R_T}\right) \\ = \frac{(R_2 + R_T)}{R_T} \ln\left(\frac{V_{in}}{V_{ref}}\right) \quad \text{--- (6)}$$

where  $R_T$  is <sup>+ve</sup><sub>x</sub> temperature coefficient (sensistor).

From eq (6), output voltage is proportional to logarithm of Input and temperature independent.

### Antilog Amplifier:-

The log Amplifier can easily turned around to provide the Antilog (or) exponential function is called "Antilog Amplifier".

#### i) Anti log Amplifier using diode:-

From fig,  $V_A=0$

concept of virtual ground,  $V_{in}$

$$V_B=0$$

w.k.t, diode current equation


$$I_f = I_0 e^{V_{in}/\eta V_T} \quad \text{--- (1)}$$

$$\text{From fig, } I = I_f = \frac{V_B - V_o}{R_f} = -\frac{V_o}{R_f} \quad \text{--- (2)} \quad [\because V_B = 0]$$

evaluating eq (1), (2)

$$I_0 e^{V_{in}/\eta V_T} = -\frac{V_o}{R_f}$$
 
$$\Rightarrow V_o = -I_0 R_f \cdot e^{V_{in}/\eta V_T} \quad \text{--- (3)}$$




Let  $V_{ref} = I_s R_f$ , then

$$V_o = -V_{ref} e^{V_{in}/V_T} \quad \text{--- (4)}$$

Thus, the output voltage is proportional to exponential function of  $V_{in}$ . So, the circuit works as Antilog Amplifier.

 ii) Antilog Amplifier using transistor :-



$$\text{and } V_{BE} = V_{in}$$

$$\text{w.k.T} \quad I_c = I_s e^{V_{BE}/V_T} \\ = I_s e^{V_{in}/V_T} \quad \text{--- (5)} \quad [\because V_{in} = V_{BE}]$$

$$\text{From fig, } I = I_c = \frac{V_B - V_o}{R_f} = \frac{-V_o}{R_f} \quad [\because V_B = 0] \quad \text{--- (6)}$$

Evaluating eq (5), (6)

$$-\frac{V_o}{R_f} = I_s e^{V_{in}/V_T} \\ \Rightarrow V_o = -I_s R_f e^{V_{in}/V_T} \quad \text{--- (7)}$$


Consider  $V_{ref} = I_s R_f$ , then

$$V_o = -V_{ref} e^{V_{in}/V_T} \quad \text{--- (8)}$$

Thus output voltage is proportional to exponential of  $V_{in}$  i.e. Antilog of  $V_{in}$ . Thus circuit works as Antilog Amplifier.
 
### iii) Temperature compensated Antilog Amplifier :-

The Temperature compensation can be provided using diodes.



The OP-Amp  $A_1$ , Non-Inverting terminal, Apply voltage divider rule,

$$V_x = \frac{R_2}{R_1 + R_2} V_{in} \quad \text{--- (9)}$$

$$\text{From fig, } V_{o1} = V_x - V_{f1} \quad \text{--- (10)}$$

$$\text{w.k.T } V_{f1} = \eta V_T \ln \left( \frac{I_f}{I_o} \right) \quad \text{--- (11)}$$

Sub. eq (9), (11) in (10),

$$V_{o1} = \frac{R_2}{R_1 + R_2} V_{in} - \left[ \eta V_T \ln \left( \frac{I_f}{I_o} \right) \right] \quad \text{--- (12)}$$

OP-Amp  $A_2$ ,  $V_A=0$  so,  $V_B=0$

$$\Rightarrow V_{o1} = -V_{f2} \quad \text{--- (13)}$$

$$\text{and } V_{f2} = \eta V_T \ln \left( \frac{I_{f2}}{I_o} \right) \quad \text{--- (14)}$$

$$\text{where } I_{f2} = I = \frac{V_o - V_B}{R_f} = \frac{V_o}{R_f} \quad \text{--- (15)} \quad [\because V_B = 0]$$

Sub. eq (15) in (14),

$$V_{f2} = \eta V_T \ln \left[ \frac{V_o}{R_f I_o} \right] \quad \text{--- (16)}$$

$$\text{from eq (13)} \quad V_o = -V_{f2}$$

$$\Rightarrow V_{O_1} = -\eta V_T \ln\left(\frac{V_o}{I_0 R_f}\right) \quad \text{--- (17)}$$

Evaluating eq (12), (17)

$$V_{in}\left(\frac{R_2}{R_1+R_2}\right) - \eta V_T \ln\left(\frac{I_{ref}}{I_0}\right) = -\eta V_T \ln\left(\frac{V_o}{I_0 R_f}\right) \quad [\because I_f = I_{ref}]$$

$$V_{in}\left(\frac{R_2}{R_1+R_2}\right) = \eta V_T \left[ \ln\left(\frac{I_{ref}}{I_0}\right) - \ln\left(\frac{V_o}{I_0 R_f}\right) \right]$$

$$= \eta V_T \left[ \ln(I_{ref}) - \ln(I_0) - \ln\left(\frac{V_o}{R_f}\right) + \ln(I_0) \right]$$

$$= \eta V_T \left[ \ln\left(\frac{I_{ref} R_f}{V_o}\right) \right] \quad [\because \ln\left(\frac{V_o}{R_f}\right) = \ln\left(\frac{V_o}{V_{in}}\right)]$$

$$= -\eta V_T \ln\left(\frac{V_o}{I_{ref} R_f}\right)$$

$$\Rightarrow \ln\left(\frac{V_o}{I_{ref} R_f}\right) = -V_{in}\left(\frac{R_2}{R_1+R_2}\right)/\eta V_T$$

$$\Rightarrow V_o = I_{ref} R_f \ln^{-1} \left[ \frac{-V_{in} R_2}{\eta V_T (R_1+R_2)} \right] \quad \text{--- (18)}$$

From eq (18), output voltage is proportional to the Antilog ( $\ln^{-1}$ ) of the input.


### Precision rectifiers :-

→ Rectifier is a device which converts A.C to pulsating D.C

→ The main drawback in rectifier circuit is it does not correct

→ rectify voltages below 0.7V.

 → In precision rectifiers it can rectify voltages having Amplitude less than 0.7V.



precision rectifiers are 2 types

1. precision Half wave rectifier
2. Precision full wave rectifier


### 1. Precision Half wave rectifier :-

#### i) Positive Precision half wave rectifier :- (or) Non-Inverting half wave precision rectif

$$\text{From fig, } V_{in} = V_p$$


concept of virtual ground

$$V_n = V_p = V_{in}$$

 


case①  $\underline{\underline{V_{in} > 0V}}$

 In this case, +ve input voltage applied so the diode act as forward bias condition and  $D_1$  becomes short circuit (ON position) it produces output in the +ve half cycle.




case②  $\underline{\underline{V_{in} < 0V}}$

 In this case -ve Input Voltage is applied, diode is in reverse bias condition i.e.  $D_1$  becomes open circuit (OFF position) so it produces NO output (zero output) in the -ve half cycle.




Output waveforms:-

 

 
ii) Negative precision half wave rectifier (or) Inverting half wave rectifier

case①  $V_{in} > 0V$

In this case, we are applying +ve input voltage, so the diode reverse biased making it open.



 
Thus output voltage  $V_o = 0V$  so no current passes through  $R_L$ .




case②  $V_{in} < 0V$

In this case, we are applying -ve input voltage, so the diode forward biased making it open.

 Thus output voltage is same as the input voltage.



Output waveforms :-

 

2 Precision full wave rectifiers :-

The full wave rectifier circuit accept an A.C signal at the input, Inverts either -ve (or) +ve half, and delivers both inverted and non inverted halves at the output.


 


Fig:- +ve and -ve full wave rectifiers

The operation of +ve full wave rectifier is

$$V_o = |V_i| \quad \text{--- ①}$$

and -ve rectifier as  $V_o = -|V_i| \quad \text{--- ②}$

 


case ①  $V_i > 0V$

positive Input voltage is applied to input of Inverting terminal of OP-AMP A<sub>1</sub>, hence output is -ve Voltage.

This -ve Voltage is given to diodes D<sub>1</sub>, D<sub>2</sub> hence D<sub>1</sub> is forward bias and D<sub>2</sub> is reverse bias, so D<sub>1</sub> ON & D<sub>2</sub> OFF.

The equivalent circuit as

 

From fig,


$$\text{output voltage } V_o = \boxed{\text{---}} + \left(\frac{R}{R}\right) V_i$$

$$V_o = -V_i \Rightarrow \boxed{V_o = +V_i}$$

case ②  $V_i < 0V$

Apply -ve voltage output of OP-AMP A<sub>1</sub> has +ve voltage it makes D<sub>1</sub> reverse bias and D<sub>2</sub> forward bias.

The equivalent circuit as

 

Apply KCL at node 'a'

$$\frac{V_i}{R} + \frac{V}{2R} + \frac{V}{R} = 0 \quad \text{--- (1)}$$

$$\therefore i = \frac{V_i}{R} \text{ & } i = \frac{V}{2R}, \\ i = \frac{V}{R}$$

$$\Rightarrow \frac{V}{2R} + \frac{V}{R} = -\frac{V_i}{R}$$

$$\Rightarrow V \left[ \frac{1}{2R} + \frac{1}{R} \right] = -\frac{V_i}{R}$$

$$\Rightarrow V \left[ \frac{R+2R}{R(2R)} \right] = -\frac{V_i}{R}$$

$$\Rightarrow V \left[ \frac{3R}{2R \cdot R} \right] = -\frac{V_i}{R}$$

$$\Rightarrow V = -\frac{2}{3} V_i \quad \text{--- (2)}$$


consider equivalent circuit,

from fig,

$$V_o = \left(1 + \frac{R}{2R}\right) V$$

$$= \left(\frac{2R+R}{2R}\right) V$$

 
$$= \frac{3R}{2R} V = \frac{3}{2} V \quad \text{--- (3)}$$



sub. eq (2) in (3)

$$\Rightarrow V_o = \frac{3}{2} \left[ -\frac{2}{3} \right] V_i \Rightarrow V_o = -V_i$$

output wave forms :-

 

→ Input signal

→ output signal

REDMI NOTE 5 PRO  
MI DUAL CAMERA

## 4. Active filters & Analog multipliers & modulators

G.Venkata Hanuman  
Asst. prof

Filter → It is a circuit that designed to pass a Specified band of frequencies while attenuating all the signals outside that band.

Filters are classified into 2 types

1. Passive filter → contain Passive elements resistor, Inductor, capacitor
2. Active filter
  - ↳ contains Active elements such as OP-AMPS, transistors


Advantages of Active filters :-

1. Reduction of size and weight
2. Low cost
3. Due to availability of modern ICs, Variety of cheaper OP-AMPS are available.
4. The OP-Amp gain can be easily controlled in closed loop fashion.
5. Due to flexibility in gain and frequency adjustments, active filters can be easily tuned.
6. The OP-Amp has high Input Impedance, low output impedance. hence the active filters using OP-AMPS

7. The Inductors are absent in the active filters. hence the modern active filters are more economical.
8. Active filters can be realized under no.of class of functions such as Butterworth, chebyshev, Thomson etc..
9. Active filters provide Voltage gain.
10. The design procedure is simpler than that of passive filters.

### Frequency response characteristics of filters :-

#### I. Low Pass filter (LPF) :-

 


a) Ideal LPF

The circuit allows the range of frequencies from 0 to  $f_H$  is called "pass band" and range of frequencies beyond  $f_H$

is completely attenuated is called "stop band".

 Practically, gain of filter decreases as frequency increases and if  $f = f_H$ , gain is down by 3dB after  $f_H$ , it decreases at higher rate. After end of transition band, gain becomes zero.





b) Practical

2. High Pass filter (HPF) :-

It allows high frequencies and reject (attenuates)

Low frequencies.

  


b) Practical

## a) Ideal

The range of frequency  $0 < f < f_L$  is the stop band where  $f$  is the operating frequency while the range of frequency  $f > f_L$  is the pass band.

 
3. Band Pass filter (BPF) :-

It allows only certain band of frequencies (passband) and attenuates remaining all frequencies (stop band).



 a) Ideal


The range of frequency  $0 < f < f_L$  and range of frequency  $f_H < f < \infty$  are 2 stop bands while range  $f_L < f < f_H$  is passband.



b) Practical


4. Band reject filter :- It also called Band elimination filter

(or) Band stop filter.

 

there are 2 pass bands while one stop band.  
the stop band between 2 frequencies  $f_L, f_H$ . The two ranges  
 $0 < f < f_L$  and  $f_H < f < \infty$  are two pass bands.

 The frequency response characteristics of band elimination filter is shown in fig:



### b) Practical

→ At frequency  $f = f_c$ , practical characteristics shows a notch and hence filter is called "Notch filter".

### All Pass filter:-

All pass filter passes all frequencies but it produces phase shift between Input and output.


The output and input voltages are equal in Amplitude for all frequencies but with phase shift between the two.

Applications :- audio applications include filter banks.
 
## First order Low Pass Butterworth filter :-

The No. of RC sections used in circuit gives the order of filter.

Here only one RC section used for 1<sup>st</sup> order LPF.



From fig,

Potential divider rule at node 'A',

$$V_A = \frac{-jX_C}{R-jX_C} \cdot V_{in} \quad \text{--- (1)}$$

$$\text{we know that } X_C = \frac{1}{2\pi f C}$$

$$V_A = \frac{-j \left( \frac{1}{2\pi f C} \right)}{R - j \left( \frac{1}{2\pi f C} \right)} \cdot V_{in}$$

$$= \frac{-j}{R(2\pi f C) - j} \cdot V_{in}$$

$$= \frac{-j}{-j \left( 1 - \frac{2\pi f R C}{j} \right)} \cdot V_{in} = \frac{1}{1 - \frac{2\pi f R C}{j}} \cdot V_{in}$$

$$\text{But } -j = \frac{1}{j}$$

$$\Rightarrow V_A = \frac{V_{in}}{1 + j 2\pi f R C} \quad \text{--- (2)}$$

Input is given to Non-Inverting terminal,

we know that  $A = 1 + \frac{R_f}{R_i}$

$$\frac{V_o}{V_A} = 1 + \frac{R_f}{R_i}$$

$$\Rightarrow V_o = \left(1 + \frac{R_f}{R_i}\right) V_A \quad \text{--- (3)}$$

Substitute eq (2) in (3)

$$V_o = \left(1 + \frac{R_f}{R_i}\right) \left( \frac{V_{in}}{1 + j2\pi f R C} \right)$$

$$\Rightarrow \frac{V_o}{V_{in}} = \left(1 + \frac{R_f}{R_i}\right) \cdot \frac{1}{1 + j(f/f_H)} \quad \left[ \because f_H = \frac{1}{2\pi R C} \right]$$

$$\Rightarrow \boxed{\frac{V_o}{V_{in}} = \frac{A_F}{1 + j(f/f_H)}} \quad \text{--- (4)} \quad \left[ \because A_F = 1 + \frac{R_f}{R_i} \right]$$

where,  $A_F \rightarrow$  Gain of filter in Passband

$f_H \rightarrow$  High cut off frequency of filter (or) corner (or)  
Break frequency

$f \rightarrow$  frequency

eq (4) expressed in Polar form as,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (f/f_H)^2}} \quad \text{--- (5)}$$

$$\text{and } \phi = -\tan^{-1}\left(\frac{f}{f_H}\right) \quad \text{--- (6)}$$

case ① :- At  $f < f_H$ ,

$$\left| \frac{V_o}{V_{in}} \right| \cong A_F \text{ i.e. constant}$$

case 2 :- At  $f = f_H$ ,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1+(1)^2}} = \frac{A_F}{\sqrt{2}} = 0.707 A_F$$

i.e. 3dB down to the level of

case 3 :- At  $f > f_H$ ,

$$\left| \frac{V_o}{V_{in}} \right| < A_F$$

characteristics:-

 


Fig :- frequency response

→ At  $f = f_H$ , gain reduces to  $0.707 A_F$  i.e. 3dB down from  $A_F$ .

→ As frequency increases than  $f_H$ , gain decreases at a rate of 20dB/decade.

→ The frequency  $f_H$  is called cut-off frequency, break frequency or -3dB frequency.


### Design steps:-

1. choose the cut-off frequency  $f_H$  i.e.  $f_H = \frac{1}{2\pi RC}$
2. choose capacitor  $C=0.001$  and  $1\text{MF}$ . Generally it selected as  $1\text{MF}$
3. The resistances  $R_f, R_1$  can be selected depending on gain in pass band.


$$A_F = 1 + \frac{R_f}{R_1}$$
 
### Second order lowpass Butterworth filter :-

\* 1st order filter can be converted to 2nd order type by using an additional RC network.



 Analysis:- The Input RC network can be represented in Laplace-domain as shown in fig.



APPLY KCL,

$$I_1 = I_2 + I_3 \quad \text{---} \textcircled{1}$$

$$\Rightarrow \frac{V_{in} - V_1}{R_2} = \frac{V_1 - V_o}{1/sc_2} + \frac{V_1 - V_A}{R_3} \quad \text{--- (2)}$$

using potential divider rule, at  $V_A$

$$V_A = \left[ \frac{\frac{1}{sc_3}}{R_3 + \frac{1}{sc_3}} \right] V_1 \quad \text{--- (3)}$$

$$V_A = \frac{V_1}{1 + R_3 sc_3} \quad \text{--- (4)}$$

$$\Rightarrow V_1 = V_A (1 + R_3 sc_3) \quad \text{--- (5)}$$

substitute eq (5) in (2),

$$\frac{V_{in} - V_A (1 + R_3 sc_3)}{R_2} = \frac{V_A (1 + SR_3 c_3) - V_o}{1/sc_2} + \frac{V_A (1 + R_3 sc_3) - V_A}{R_3}$$

$$\Rightarrow \frac{V_{in}}{R_2} - \frac{V_A (1 + SR_3 c_3)}{R_2} = \frac{V_A (1 + SR_3 c_3)}{1/sc_2} - \frac{V_o}{1/sc_2} + \frac{V_A (1 + SR_3 c_3)}{R_3} - \frac{V_A}{R_3}$$

$$\Rightarrow \frac{V_{in}}{R_2} + \frac{V_o}{1/sc_2} = \frac{V_A}{R_2} (1 + SR_3 c_3) + \frac{V_A}{1/sc_2} [1 + SR_3 c_3] + \frac{V_A}{R_3} (1 + SR_3 c_3) - \frac{V_A}{R_3}$$

$$\Rightarrow \frac{V_{in}}{R_2} + V_o (sc_2) = V_A \left[ \frac{1 + SR_3 c_3}{R_2} + \frac{1 + SR_3 c_3}{1/sc_2} + \frac{1 + SR_3 c_3}{R_3} - \frac{1}{R_3} \right]$$

$$= V_A \left[ \frac{R_3 (1 + SR_3 c_3) + R_2 R_3 sc_2 (1 + SR_3 c_3) + R_2 (1 + SR_3 c_3) - R_2}{R_2 R_3} \right]$$

$$\Rightarrow \left( \frac{V_{in}}{R_2} + V_o sc_2 \right) R_2 R_3 = V_A \left[ (1 + SR_3 c_3) [R_3 + R_2 R_3 sc_2 + R_2] - R_2 \right]$$

$$\Rightarrow V_{in} R_3 + V_o R_2 R_3 sc_2 = V_A [(1 + SR_3 c_3) (R_3 + R_2 R_3 sc_2 + R_2) - R_2]$$

$$V_A = \frac{V_{in}R_3 + V_o S R_2 R_3 C_2}{[(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2]} \quad (6)$$

Op-Amp in Non-Inverting configuration,

$$\text{w.r.t } \frac{V_o}{V_A} = 1 + \frac{R_F}{R_1}$$

$$\left[ \because A_F = 1 + \frac{R_F}{R_1} \right]$$

$$\frac{V_o}{V_A} = 1 + \frac{R_F}{R_1}$$

$$\Rightarrow \frac{V_o}{V_A} = A_F \Rightarrow V_o = A_F \cdot V_A$$

$$V_o = A_F \left[ \frac{R_3 V_{in} + V_o S R_2 R_3 C_2}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2} \right]$$

$$\Rightarrow V_o = \frac{A_F R_3 V_{in}}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2} + \frac{A_F V_o S R_2 R_3 C_2}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2}$$

$$\Rightarrow V_o - \frac{A_F V_o S R_2 R_3 C_2}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2} = \frac{A_F R_3 V_{in}}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2}$$

$$\Rightarrow V_o \left[ 1 - \frac{A_F S R_2 R_3 C_2}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2} \right] = \frac{A_F R_3 V_{in}}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2}$$

$$\Rightarrow V_o \left[ \frac{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2 - A_F S R_2 R_3 C_2}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2} \right] = \frac{A_F R_3 V_{in}}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2}$$

$$\Rightarrow A_F R_3 V_{in} = V_o \left[ (1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2 - S R_2 R_3 C_2 A_F \right] \quad (7)$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{A_F R_3}{(1+SR_3C_3)(R_3 + R_2 R_3 S C_2 + R_2) - R_2 - S R_2 R_3 C_2 A_F}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{A_F}{s^2 + \frac{(R_3C_3 + R_2C_3 + R_2C_2 - A_F R_2 C_2)s}{R_2 R_3 C_2 C_3} + \frac{1}{R_2 R_3 C_2 C_3}}$$

The order of 's' in the above expression is two, the filter is called "2<sup>nd</sup> order filter"

The standard form of the transfer function of any 2<sup>nd</sup> order system is

$$\frac{V_o(s)}{V_{in}(s)} = \frac{A}{s^2 + 2\xi\omega_n s + \omega_n^2} \quad \text{--- (9)}$$

compare eq(8), (9)

$$\omega_n^2 = \frac{1}{R_2 R_3 C_2 C_3}$$

In case of filters, frequency is cut-off frequency,  $\omega_H$

$$\Rightarrow \omega_H^2 = \frac{1}{R_2 R_3 C_2 C_3}$$

$$\Rightarrow (2\pi f_H)^2 = \frac{1}{R_2 R_3 C_2 C_3}$$


$$\Rightarrow f_H^2 = \frac{1}{4\pi^2 R_2 R_3 C_2 C_3}$$

$$\Rightarrow f_H = \boxed{\frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}} \quad \text{--- (10)}$$

In Polar form,  $\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + \left(\frac{f}{f_H}\right)^4}}$  --- (11)

The frequency response is shown in fig.

 - The cut-off frequency  $f_H$ , gain is  $0.707 A_F$  i.e. 3dB down from its 0Hz level.
- After  $f_H$ , gain rolls off at a rate of 40 dB/decade.



### Design Steps :-

To design 2<sup>nd</sup> order low pass Butterworth filter having

1. choose cut-off frequency  $f_H$ .
2. Design can be simplified by selecting  $R_2 = R_3 = R$  and  $c_2 = c_3 = c$  choose 'c' value less than (or) equal to 14F
3. calculate value of 'R' from equation;

$$f_H = \frac{1}{2\pi\sqrt{R_2 R_3 c_2 c_3}} = \frac{1}{2\pi R C}$$

4. AS  $R_2 = R_3 = R$  and  $c_2 = c_3 = c$ , pass band voltage gain  $A_F = 1 + \frac{R}{R}$  of the 2<sup>nd</sup> order filter equal to 1.586

### Note:-

To ensure Butterworth response, gain  $A_F$  is 1.586

$$\text{i.e. } 1.586 = 1 + \frac{R_f}{R_i}$$


$$\Rightarrow R_f = 0.586 R_i$$

## First order High pass Butterworth filter :-

- A High Pass filter is a circuit that attenuates all signals below specified cut-off frequency  $f_L$ .
- By interchanging the elements R and C in a 1<sup>st</sup> order Low Pass filter circuit it forms High pass filter circuit.

From fig,

 By using voltage divider rule  
at node 'A'



$$V_A = \left[ \frac{R}{R - jX_C} \right] V_{in} \quad \text{--- (1)}$$

$$= \left[ \frac{R}{-jX_C \left( \frac{R}{-jX_C} + 1 \right)} \right] V_{in}$$

$$= \left[ \frac{\left( \frac{-R}{jX_C} \right)}{\left( \frac{-R}{jX_C} \right) + 1} \right] V_{in} \quad \text{--- (2)}$$

$$\Rightarrow V_A = \left[ \frac{j2\pi f R C}{j2\pi f R C + 1} \right] V_{in} \quad \text{--- (3)}$$

$$\begin{aligned} \because -\frac{1}{jX_C} &= \frac{j}{X_C} \\ &= \frac{j}{2\pi f C} \end{aligned}$$

$$\text{consider } f_L = \frac{1}{2\pi R C} \rightarrow \text{low cut-off frequency} = j2\pi f_C \quad \text{--- (3)}$$

$$\Rightarrow V_A = \left[ \frac{j \left( \frac{f}{f_L} \right)}{j \left( \frac{f}{f_L} \right) + 1} \right] V_{in} \quad \text{--- (4)}$$

The OP-Amp in Non-Inverting configuration,

$$\frac{V_o}{V_A} = \left(1 + \frac{R_f}{R_1}\right)$$

$$A_F = \left(1 + \frac{R_f}{R_1}\right)$$

$$\Rightarrow V_o = V_A \left[1 + \frac{R_f}{R_1}\right] \quad \text{--- (5)} \Rightarrow V_o = V_A \cdot A_F \quad \text{--- (5)}$$

Substitute eq(4) in (5)

$$\Rightarrow V_o = A_F \cdot \left[ \frac{j(f/f_L)}{j(f/f_L) + 1} \right] V_{in}$$

$$\Rightarrow \frac{V_o}{V_{in}} = A_F \left[ \frac{j(f/f_L)}{j(f/f_L) + 1} \right] \quad \text{--- (6)}$$

Magnitude is given by,

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F (f/f_L)}{\sqrt{1 + (f/f_L)^2}} \quad \text{--- (7)}$$

eq(7), describes the behaviour of high pass filter.

1. At low frequencies,  $f < f_L$

$$\left| \frac{V_o}{V_{in}} \right| < A_F$$


2. At  $f = f_L$ ,  $\left| \frac{V_o}{V_{in}} \right| = 0.707 A_F$  i.e. 3dB down from the level of

3. At  $f > f_L$ , i.e. high frequencies,

$$\left| \frac{V_o}{V_{in}} \right| \approx A_F \text{ i.e. constant.}$$

- The circuit act as a high pass filter with a pass band gain  $A_F$ .
- At  $f < f_L$ , gain increases till  $f = f_L$  at a rate of  $+20\text{dB/decade}$ .  
Hence slope of frequency response in stopband is  $+20\text{dB/decade}$  for 1<sup>st</sup> order high pass filter.

Frequency response is shown in fig.

 

### Second order High Pass Butterworth filter :-

This filter can be obtained by interchanging positions of R and c in 2<sup>nd</sup> order low pass Butterworth filter.

 



Fig:- second order high pass Butterworth filter

The Analysis, design and procedures for this filter is exactly same as that of 2<sup>nd</sup> order low pass Butterworth filter.

i.e. 
$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (f_L/f)^4}}$$

$$f_L = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}}$$

 The frequency response of this filter as shown in fig.




### Band Pass filters:-

It allows one particular band of frequencies to pass. Thus, pass band in between  $f_H$  and  $f_L$ .

→ Pass band which is between  $f_H$  and  $f_L$  is called band width.

$$B.W = f_H - f_L$$

 


→ There are 2 types of Band Pass filters based on figure of merit (or) quality factor ( $Q$ ).

1. wide Band pass filter ( $\omega < 10$ )

2. Narrow Band Pass filter. ( $\omega > 10$ )
 
### 1. wide band pass filter:-


for  $\omega < 10$ , the band pass filter is called wide band pass filter. In this type, the band width is more. The response is shown in fig.



### 2. narrow Band pass filter:-

For  $\omega > 10$ , the band pass filter is called narrow band pass filter. In this type, band width is very small. The response is shown

in fig.

 

The gain roll off for  $f < f_L$  is +20dB/decade and

$f > f_H$  is -20dB/decade.

and center frequency

$$f_C = \sqrt{f_L f_H}$$


The relationship between Q and bandwidth is

$$Q = \frac{f_c}{Bw} = \frac{f_c}{f_H - f_L}$$
 
### wide band pass filter:-

wide band pass filter is formed by cascading high pass filter and low pass filter.

→ If HPF and LPF are 1<sup>st</sup> order, then band pass filter will have a roll-off rate of -20dB/decade.



For wide band pass response,  $f_H$  must be greater than  $f_L$ .

$$\text{For Lowpass} \rightarrow \left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (f/f_H)^2}}$$

$$\text{For Highpass} \rightarrow \left| \frac{V_o}{V_{in}} \right| = \frac{A_F (f/f_L)}{\sqrt{1 + (f/f_L)^2}}$$

Overall gain is product of 2 gains.

$$\left| \frac{V_o}{V_{in}} \right| = \frac{A_{FT} (f/f_c)}{\sqrt{(1+f/f_H)^2 (1+f/f_L)^2}}$$


where  $A_{FT} \rightarrow$  Total pass band Gain  
i.e  $A_{FT} = \text{Gain of HPF} \times \text{Gain of LPF}$ .

### Narrow Band Pass filter :-

The narrow band pass filter uses only one op-amp against two by wide band filter.

It has  
i) 2 feed back paths ii) op-amp in Inverting configuration

 Due to two feed back paths it also called "multiple feedback filter".



→ Input is applied to Inverting terminal, so it is in Inverting configuration.  $R_3$  connected to Non-Inverting input terminal is offset compensating resistance.

→ Important parameters are  $f_L, f_H$ , center frequency  $f_c$ , gain at center frequency  $A_F$ , quality factor  $Q$ .

For simplifying calculations, choose  $C_1 = C_2 = C$

$$R_1 = \frac{Q}{2\pi f_c C A_F} \quad \text{--- (1)}$$

$$R_2 = \frac{Q}{2\pi f_c C (2Q^2 - A_F)} \quad \text{--- (2)}$$

$$R_3 = \frac{Q}{\pi f_c C} \quad \text{--- (3)}$$

$$\text{and } A_F = \frac{R_3}{2R_1} = \text{Gain at } f_c \quad \dots \quad (4)$$

Gain  $A_F$  must satisfy the equation,  $A_F < 2\omega^2$  — (5)

changing the centre frequency  $f_c$ :

Let  $f_c \rightarrow$  original frequency

$f_c' \rightarrow$  New centre frequency

The new centre frequency can be achieved by changing resistance  $R_2$ .

The new value of resistance is

$$R_2' = R_2 \left( \frac{f_c'}{f_c} \right)^2 \quad \dots \quad (6)$$

 


Fig:— Frequency response

\* Advantage :-  $f_c$  can be changed without changing gain  $A_F$  (or)  
Band width.

Band Elimination filter:-

It also called "band stop filter" (or) "band reject filter"

→ This operation is exactly opposite to Band Pass filter.

→ It contains 2 pass bands and 1 stop band.

→ A band of frequencies is attenuated by this filter hence name

called as "Band Elimination filter".


→ This filter again divided into 2 types

i. wide band reject filter

ii. narrow band reject filter

 i. wide band reject filter :-

similar to wide band pass filter, it also consists of high pass and low pass filters, additionally it contains summing Amplifier.



It has 2 conditions

- The low cut-off frequency,  $f_L$  of high pass filter must be greater than high cut-off frequency,  $f_H$  of low pass filter.
- pass band gain of both high pass and low pass sections must be equal.

The gain of summing Amplifier can be set to 1 for simplicity

$$R_2 = R_3 = R_4 = R \quad \text{--- ①}$$


$$\text{Here, } R_{\text{comp}} = R_2 || R_3 || R_4 = \frac{R}{3} \quad \text{--- ②}$$

Both high pass and low pass sections provide attenuation in stopband between  $f_H$  and  $f_L$ .

for  $f < f_H$ , transmission is due to low pass section, while for  $f > f_L$ , transmission is due to high pass section.

$$\text{centre frequency, } f_c = \sqrt{f_H f_L}$$

The frequency response is shown in fig.

 

## 2. Narrow band reject filter (Notch filter) :-

The application of Notch filter is the rejection of a single frequency, such as 50Hz power line frequency hum.

→ It is used in Biomedical instrumentation and also blanking of control tones for telephone lines.

→ By using this filter, particular unwanted frequency can be eliminated.

→ It also called as Twin T Network.

 


Fig:- Twin T Network

It consists of 2 T Networks. one consists of 2 resistors and a capacitor while other consists of 2 capacitors and 1 resistor.

The Notch out frequency is the frequency at which maximum attenuation occurs.

$$\text{It is given by } f_N = \frac{1}{2\pi RC}$$

The value of  $\omega$  ie figure of merit for the passive network is very low, hence an active notch filter which uses twin T Network is preferred in practice.


 



Fig:- Active Notch filter

To design a notch filter, to eliminate specific Notch frequency  $f_N$ , choose capacitor 'c' less than (or) equal to 1MF. Then, calculate 'R' using  $f_N = \frac{1}{2\pi RC}$  expression.

The frequency response as shown in fig.

 

a) Ideal

 

b) practical

### All pass filter:-

The filter which is used to control the phase response by adding a phase shift between input and output signals is called

as "All pass filter".

- The name indicates, it passes all frequencies of input signal.
- It does not produce any attenuation but provides the required phase shift for the different frequencies of input signal.
- For Example, when signals are transmitted over the transmission lines, there is change in their phase. To compensate for such phase change, all pass filters are used.
- Hence, all pass filters are also called as "delay equalizers" (or) "phase correctors"

 


Fig:- First order All pass filter

Analysis :-

Assume, Input to the Non-Inverting terminal zero. The circuit act as an Inverting Amplifier.

$$\therefore V_{o1} = -\frac{R_f}{R_1} V_{in}$$

$$V_{o1} = -V_{in} \quad \text{--- ①} \quad [\because R_f = R_1]$$

Assume, Input to the Inverting terminal zero. The circuit act as an Non-Inverting Amplifier.

$$V_{o2} = \left(1 + \frac{R_f}{R_1}\right) V_A$$

$$V_{o2} = 2 V_A \quad \text{--- ②} \quad [\because R_f = R_1]$$

By using Potential divider, at  $V_A$ .

$$V_A = \left( \frac{-jX_C}{R-jX_C} \right) \cdot V_{in}$$

$$= \left( \frac{-j}{\frac{R}{2\pi f C} - j} \right) \cdot V_{in} \quad \left[ \because X_C = \frac{1}{2\pi f C} \right]$$

$$= \left[ \frac{\frac{1}{j2\pi f C}}{R + \frac{1}{j2\pi f C}} \right] \cdot V_{in} \quad \left[ \because -j = \frac{1}{j} \right]$$

$$V_o = \left( \frac{1}{1+j2\pi f RC} \right) \cdot V_{in} \quad \text{--- (3)}$$

Substitute eq (3) in (2),

$$V_{o2} = 2 \left( \frac{1}{1+j2\pi f RC} \right) \cdot V_{in} \quad \text{--- (4)}$$

Total output voltage is

$$V_o = V_{o1} + V_{o2}$$

$$= -V_{in} + 2V_{in} \left[ \frac{1}{1+j2\pi f RC} \right]$$

$$= V_{in} \left[ -1 + \frac{2}{1+j2\pi f RC} \right]$$

$$\Rightarrow \frac{V_o}{V_{in}} = \frac{-1 + j2\pi f RC + 2}{1+j2\pi f RC}$$

$$= \frac{-1 - j2\pi f RC + 2}{1+j2\pi f RC}$$

$$\boxed{\frac{V_o}{V_{in}} = \frac{-1 - j2\pi f RC}{1+j2\pi f RC}} \quad \text{--- (5)}$$

The magnitude of the transfer function is

$$\left| \frac{V_o}{V_{in}} \right| = \frac{\sqrt{1+(2\pi f RC)^2}}{\sqrt{1+(2\pi f RC)^2}} = 1 \quad \text{--- (6)}$$

The magnitude is always 1 for all pass filter and it can pass the entire range of frequency.

Phase angle is given by,  $\phi = -\tan^{-1}\left(\frac{2\pi f RC}{1}\right) - \tan^{-1}\left(\frac{2\pi f RC}{1}\right)$

$$\boxed{\phi = -2\tan^{-1}\left(\frac{2\pi f RC}{1}\right)} \quad \text{--- (7)}$$

If  $f=0, \Rightarrow \phi=0^\circ$

$f=\infty, \Rightarrow \phi=-90^\circ$

$f=\infty, \phi=-180^\circ$

This is the phase angle in degrees which indicates that there is a phase shift of  $\phi$  between input and output signal.

If the positions of R and C are interchanged, we get +ve phase shift.

The -ve phase shift indicates that output  $V_o$  lags Input  $V_{in}$  by angle  $\phi$ , +ve phase shift indicates that  $V_o$  leads Input  $V_{in}$  by angle  $\phi$ .

Q.

 



Fig:- phase shift between  $V_o$  and  $V_{in}$ .

#### Four quadrant multiplier :-

A circuit which can function in all the 4 quadrants of operation and generates the product of two input voltages irrespective of the polarity of its input signals is referred as "four quadrant multiplier".

→ It is designed in monolithic form.

 The schematic arrangement of 4-quadrant multiplier as shown in fig.



→ when voltage  $V_A$  is applied to the input of circuit the  $V_A$  is processed and result an intermediate voltage 'v' generated across  $\omega_x$  and

Q<sub>4</sub>.  
 → Any non-linearity signal involved with in V<sub>A</sub> generating V is the inverse of non-linearity related with base emitter junctions of Q<sub>5</sub>-Q<sub>6</sub> and Q<sub>7</sub>-Q<sub>8</sub> transistors.

Therefore, output voltage of circuit is proportional to the linear multiplication of 2 inputs.

The resistors  $R_A, R_B$  called as Emitter degeneration resistors. These resistors is to convert input voltages into linear differential currents  $I_A, I_B$ .

$$I_A = \frac{V_A}{R_A}, \quad I_B = \frac{V_B}{R_B} \quad \text{--- (1)}$$

convert voltage to current,  $R_A$  and  $R_B$  selected as

$$\text{i) } R_A \gg \frac{V_T}{I_1}$$

$$\text{ii) } R_B \gg \frac{V_T}{I_2}$$

The output voltage is

$$V_{\text{out}} = R_L [ (I_6 + I_7) - (I_5 + I_8) ] \quad \text{--- (2)}$$

and

$$\frac{I_6}{I_3 + I_B} = \frac{I_5}{I_3 - I_B} = \frac{I_1 + I_A}{2I_1}$$

$$\Rightarrow I_6 = \frac{(I_3 + I_B)(I_1 + I_A)}{2I_1} \quad \text{--- (3)}$$

$$\Rightarrow I_5 = \frac{(I_3 - I_B)(I_1 + I_A)}{2I_1} \quad \text{--- (4)}$$

and also,

$$\frac{I_8}{I_3 + I_B} = \frac{I_7}{I_3 - I_B} = \frac{I_1 - I_A}{2I_1}$$

$$\Rightarrow I_8 = \frac{(I_1 - I_A)(I_3 + I_B)}{2I_1} \quad \text{--- (5)}$$

$$\Rightarrow R_L = \frac{(Q_A + T_B)(T_1 - T_0)}{2T_1} \quad \text{.....(6)}$$

Substitute members (6) in eqn (2)

$$\begin{aligned}
 V_{AB} &= R_L \left[ \left( \frac{(Q_A + T_B)(T_1 - T_0)}{2T_1} + \frac{(Q_B - T_A)(T_1 - T_0)}{2T_1} \right) \right. \\
 &\quad \left. + \left( \frac{(Q_A - T_A)(T_1 + T_0)}{2T_1} + \frac{(Q_B + T_B)(T_1 - T_0)}{2T_1} \right) \right] \\
 &= R_L \left\{ \left( \frac{T_1 T_0 + Q_A T_0 + Q_B T_0 + T_0 T_0 + T_1 T_0 - Q_A T_0 - Q_B T_0}{2T_1} = T_0 T_0 + T_0 T_B \right) \right. \\
 &\quad \left. - \left( \frac{T_1 T_0 + Q_A T_B - Q_B T_B - T_0 T_B + T_1 T_B - Q_A T_B + Q_B T_B - T_0 T_B}{2T_1} \right) \right\} \\
 &= R_L \left( \frac{Q_A T_0 + Q_B T_0 - Q_A T_B + Q_B T_B}{2T_1} \right) \\
 &= R_L \left( \frac{Q(T_0 - T_B)}{2T_1} \right) = \frac{Q R_L}{2} \left( \frac{T_0 - T_B}{T_1} \right)
 \end{aligned}$$

as  $T_A, T_B$  linearly proportional to  $V_A, V_B$  using eqn (1),  $V_A$  can be considered

$$V_{AB} = k V_A V_B \quad (\because k = \frac{QR_L}{T_1(R_A R_B)})$$

usually,  $k$  value is chosen as 0.1

## Balanced modulator (IC1496) :

 



Fig :- IC1496

- Transistors  $Q_7, Q_8$  are constant current sources.
- Transistors  $Q_1, Q_2, Q_5$  form one differential Amplifier
- Transistors  $Q_3, Q_4, Q_6$  forms another differential Amplifier
- The constant current sources supply equal amount of current to the two differential amplifiers.

- The carrier signal is applied in phase as biasing signal for differential Amplifiers.
- The modulating signal is applied to the bases of  $Q_5, Q_6$ .
- These transistors are connected in the current paths to the differential transistors, therefore will vary the Amplitude of the current in accordance with the modulating signal.
- The currents in  $Q_5, Q_6$  will be  $180^\circ$  out of Phase with each other. As current in  $Q_5$  increases, current through  $Q_6$  decreases and vice versa.
- From the figure, output of a differential Amplifiers connected in parallel, and output is taken across the two collector terminal of the differential Amplifier.
- As a result, common signals are get cancelled and only difference signal appears at the output. This suppresses the carrier signal and output we get is the upper and lower side bands.
 
### sample and Hold circuits :-

In these circuits a JFET is used as switch. During the sampling time the JFET is turned on, and the holding capacitor charges up to the level of Analog Input voltage.



→ open loop architecture of sample and hold circuit

- Here 2 op-amps  $A_1, A_2$  are used. In between these there is E-MOSFET is used as a switch.
- If E-MOSFET is act as closed switch then the capacitor will charge. If the E-MOSFET is act as open-switch then the capacitor starts discharging.
- The acquisition time of S/H circuit is the time required for the holding capacitor  $C_H$  to charge up to the level close to the input voltage during sampling.
- The acquisition time for S/H circuit is low as possible.
- In the circuit, 3 principle factors will control the acquisition time. These factors are
  - i) RC time constant where R is the  $r_{ds(on)}$ , ie on resistance of JFET and 'c' is the holding capacitance  $C_H$ .
  - ii) maximum output current, which can be source (or) sink by operational amplifier

iii) slew rate of the op-amp.

→ If the control voltage  $V_c$  is at +ve, n-MOSFET is closed switch.

If  $V_c$  is at -ve, then n-MOSFET is open switch.

→ Practically, discharging is not possible for this case because,


$$\tau = RC$$

$$\text{Here } R = \infty, \tau = \infty$$


Therefore, discharging time is infinity.

→ Sampling occurs at the time interval is  $0 < t < T_s$

 
→ Holding occurs at the time interval is  $T_h < t < T_H$ .



 → To get maximum output, slew rate of the op-amp rather than  $RC$  time constant we use the circuit as,



 
→ To provide voltage gain, i.e.  $A = 1 + R_F/R_1$ . we use the circuit as



The sampled output voltage is equal to sampled input voltage multiplied by voltage gain factor of  $1 + R_F/R_1$ .

→ The following S/H circuit offers 2 advantages

 - i) The faster capacitor charging rate provides shorter acquisition time because, voltage at Inverting Input terminal A<sub>2</sub> equal to capacitor voltage divided by open loop gain of A<sub>2</sub>.
- ii) In the circuit, summing input of A<sub>2</sub> remains at virtual ground. due to this charge removed from summing junction.



Performance Parameters of S/H circuits :- (extra syllabus)

1) Acquisition time ( $t_{ac}$ ):- It is the time required for the holding capacitor  $C_H$  to charge up to a level close to input voltage during sampling.

It depends on

- i) RC time constant
- ii) maximum output current
- iii) slew rate of OP-AMP.

2) Aperture time ( $t_{ap}$ ):-

Because of propagation delays through driver and switch,  $V_o$  will keep tracking  $V_i$  some time after the inception of the hold command. This is the aperture time.

3) Aperture uncertainty ( $\Delta t_{ap}$ ):- It is the variation in aperture time from sample to sample. Due to aperture uncertainty, it is difficult to compensate aperture time by advancing hold command.

4) Hold mode settling time ( $t_s$ ):- After the application of hold command, it takes a certain amount of time for  $V_o$  to settle within a specified error band, such as 1%, 0.1%, 0.01%. This is the hold mode settling time.

Problems

- 1) design a first order high pass filter at a cut-off frequency of 400 Hz and a passband gain of 1.

sol:-

Step 1 :-  $f_L = 400 \text{ Hz}$

Step 2 :- choose 'c' less than 1MF

$$C = 0.02 \mu\text{F}$$

Step 3 :-  $f_L = \frac{1}{2\pi RC}$


$$\Rightarrow R = \frac{1}{2\pi \times 400 \times 0.02 \times 10^{-6}} = 19.8 \text{ k}\Omega \approx 20 \text{ k}\Omega$$

Step 4 :-  $A_F = 1 + \frac{R_f}{R_1} = 1$

$$\Rightarrow \frac{R_f}{R_1} = 1 - 1 = 0$$

choose  $R_f = 0$  i.e unity gain feedback

choose  $R_f = 10 \text{ k}\Omega$

 

- 2) Design a first order Lowpass filter so that it has cut-off frequency of 2kHz and a pass band gain of 1.

Step 1 :-  $f_H = 2 \text{ kHz}$

Step 2 :- 'c' value chosen as  $0.01 \mu\text{F}$


Step 3 :-  $f_H = \frac{1}{2\pi RC}$

$$\Rightarrow R = \frac{1}{2\pi \times f_H \times C} = \frac{1}{2\pi \times 2 \times 10^3 \times 0.01 \times 10^{-6}} = 7.95 \text{ k}\Omega$$

Step 4:-  $A_f = 1 + \frac{R_f}{R_1}$

$$1 = 1 + \frac{R_f}{R_1} \Rightarrow \frac{R_f}{R_1} = 0 \\ \Rightarrow R_f = 0 \text{ k}\Omega$$

consider  $R_1 = 10 \text{ k}\Omega$

 

- 5) design a second order low pass Butterworth filter having high cut-off frequency of 1 kHz. draw its frequency response.

Step 1:-  $f_H = 1 \text{ kHz}$

Step 2:- choose  $C_2 = C_3 = C = 0.01 \mu \text{F}$

Step 3:- choose  $R_2 = R_3 = R$

$$\Rightarrow f_H = \frac{1}{2\pi RC}$$


$$\Rightarrow R = \frac{1}{2\pi \times 1 \times 10^3 \times 0.01 \times 10^{-6}} = 15.91 \text{ k}\Omega$$

Step 4:-  $R_f = 0.586 R_1$

$$\left[ \because R_f = 0.586 R_1 \right]$$

choose  $R_1 = 10 \text{ k}\Omega$
 
$$\Rightarrow R_f = 0.586 \times 10 \times 10^3 = 5.86 \text{ k}\Omega$$




The gain of 2<sup>nd</sup> order filter is given by

$$\frac{V_o}{V_{in}} = \frac{A_F}{\sqrt{1 + (\frac{f}{f_H})^4}}$$

w.k.t  $A_F = 1.586$ ,  $f_H = 1\text{kHz}$   $\Rightarrow \frac{V_o}{V_{in}} = \frac{1.586}{\sqrt{1 + \left(\frac{f}{1 \times 10^3}\right)^4}}$

frequency (Hz)	$\frac{V_o}{V_{in}}$	$20 \log \left( \frac{V_o}{V_{in}} \right)$
10	1.586	4dB
100	1.585	4dB
500	1.538	3.74 dB
1000	1.121	1dB
5000	0.0633	-23.97 dB
7000	0.032	-29.89 dB
10,000	0.015	-36.47 dB
50,000	$6.34 \times 10^{-4}$	-63.95 dB
10,0000	$1.586 \times 10^{-4}$	-76 dB

### Frequency response

 

4) Design and obtain the frequency response of a band pass filter with  $f_L = 100\text{Hz}$  and  $f_H = 1\text{kHz}$  with pass band gain 4.

5) Design the low pass filter.

$$f_L = 100\text{Hz}$$

$$\omega_L = 0.01\text{MF}$$

$$\Rightarrow R = \frac{1}{\omega_L C} = \frac{1}{0.01 \times 10^6 \times 0.005 \times 10^6} = 15.91\text{ k}\Omega$$

Design the high pass filter,

$$f_H = 1\text{kHz}, \omega_H = 0.05\text{MF}$$

$$\Rightarrow R = \frac{1}{\omega_H C} = \frac{1}{0.05 \times 10^6 \times 0.005 \times 10^6} = 7.95\text{ k}\Omega$$

$$\text{Now } \alpha_{LP} = \alpha_1 \alpha_2 = 1$$


$$\text{Let } \alpha_1 = \alpha_2 = 1 = 1 + \frac{\beta_f}{\beta_1}$$

$$\Rightarrow \frac{\beta_f}{\beta_1} = 1 - 1 = 0 \Rightarrow R_f = 0\text{ }\Omega$$

use  $R_f = 0\text{ }\Omega$

$\therefore$  consider  $R_f = 10\text{ k}\Omega$


The designed circuit is

 

frequency response

$$\left| \frac{V_o}{V_{in}} \right| = \frac{n_{FT} (f/f_L)}{\sqrt{[(1+f/f_L)^v][(1+f/f_H)^v]}} = \frac{f/400}{\sqrt{[1+\left(\frac{f}{400}\right)^v][1+\left(\frac{f}{1000}\right)^v]}}$$

frequency	$\left  \frac{V_o}{V_{in}} \right $	$20 \log \left  \frac{V_o}{V_{in}} \right $
10	0.025	-32.04
100	0.241	-12.34
400	0.656	-3.66
600	0.713	-2.93
1000	0.656	-3.66
5000	0.195	-14.17
10,000	0.099	-20.05

 

$$\text{Now } f_C = \sqrt{f_L f_H} = \sqrt{400 \times 1000} = 632.45 \text{ Hz}$$

$$\text{B.W} = f_H - f_L = 1000 - 400 = 600 \text{ Hz}$$

$$\therefore Q = \frac{f_C}{\text{B.W}} = \frac{632.45}{600} = 1.054$$

- 5) A certain narrow band pass filter has been designed to meet the following specifications:  $f_c = 3\text{kHz}$ ,  $\omega = 25$ ,  $A_F = 10$ . what modifications are necessary in the filter circuit to change the center frequency to 1kHz, keeping the gain and bandwidth constant?

gj:

choose  $C_1 = C_2 = C = 0.02\text{MF}$

$$R_1 = \frac{\omega}{2\pi f_c C A_F} = \frac{25}{2\pi \times 3 \times 10^3 \times 0.02 \times 10^6 \times 10} = 6.631\text{ k}\Omega$$

$$R_2 = \frac{\omega}{2\pi f_c C (2\omega^2 - A_F)} = \frac{25}{2\pi \times 3 \times 10^3 \times 0.02 \times 10^6 (2 \times 25^2 - 10)} = 53.48\text{ }\Omega$$


$$R_3 = \frac{\omega}{\pi f_c C} = \frac{25}{\pi \times 3 \times 10^3 \times 0.02 \times 10^6} = 132.63\text{ k}\Omega$$

change  $R_2$  to  $R_2'$ , To get  $f_c'$  as 1kHz,

$$R_2' = R_2 \left( \frac{f_c}{f_c'} \right)^2$$

$$= 53.48 \times \left( \frac{3 \times 10^3}{1 \times 10^3} \right)^2 = 481.32\text{ }\Omega$$

Designed circuit as,

 

- 6) FOR all pass filter, determine the phase shift between Input and output at  $f=2\text{kHz}$ . To obtain positive phase shift what modifications are necessary in the circuit.

Ej:- The phase shift  $\phi$  for all pass filter is,

$$\phi = -2\tan^{-1}[2\pi f RC]$$

G.T  $f=2\text{kHz}$ , Assume  $R=16\text{k}\Omega$ ,  $C=0.01\mu\text{F}$

$$\begin{aligned}\therefore \phi &= -2\tan^{-1}[2\pi \times 2 \times 10^3 \times 16 \times 10^3 \times 0.01 \times 10^{-6}] \\ &= -126.82^\circ\end{aligned}$$

Thus output lags input by  $126.82^\circ$  but Amplitude & frequency is same as input.

\* To get +ve Phase shift, Positions of R and C must be interchanged in All Pass filter.

- 7) Design all Pass filter with a phase shift of  $-135^\circ$  at a frequency of  $2\text{kHz}$  at the output. draw the circuit diagram.

Ej:- G.T  $f=2\text{kHz}$ ,  $\phi=-135^\circ$

$$\text{W.K.T } \phi = -2\tan^{-1}[2\pi f RC]$$

$$-135 = -2\tan^{-1}[2\pi f RC]$$

$$\Rightarrow 2\pi f RC = \tan(67.5)$$


$$\Rightarrow RC = \frac{2.4142}{2\pi \times 2 \times 10^3} = 1.921 \times 10^{-4}$$

$$\text{choose } C = 0.1\mu\text{F}$$

$$\Rightarrow R = 1.92 \text{k}\Omega$$

$$\text{Let } R_f = R_i = 10\text{k}\Omega$$

The designed circuit as,

 

Q) Design an active high pass filter to meet the following specifications.

i) Butterworth response      ii) cut-off frequency = 4MHz

iii) Decay rate in the stop band = 40dB/decade.

S. i.e., decay rate in stop band is 40dB/decade, it is 2<sup>nd</sup> order high pass filter.

choose,  $C_2 = C_3 = C = 0.02\mu F$

$$\text{if } f_L = 4\text{Hz}$$

$$f_L = \frac{1}{2\pi RC} \Rightarrow 4 \times 10^3 = \frac{1}{2\pi \times R \times 0.02 \times 10^{-6}}$$

$$\Rightarrow R = 1.98 \approx 2\text{k}\Omega$$

$$R = R_2 = R_3 = 2\text{k}\Omega$$

for Butterworth response,

$$A_F = 1.586$$


$$\therefore = 1 + \frac{R_f}{R_1} \Rightarrow \frac{R_f}{R_1} = 0.586$$

$$\Rightarrow R_f = 0.586 R_1$$

$$\text{choose } R_f = 10\text{k}\Omega$$

$$\Rightarrow R_1 = 17\text{k}\Omega$$

Hence designed circuit is,

 

Q) design a notch filter for  $f_N = 8\text{kHz}$ ,  $Q = 10$ . choose  $C = 500\text{pF}$ .

Sol:- use 2nd order Notch filter,  $f_N = \frac{1}{2\pi R C}$

$$8 \times 10^3 = \frac{1}{2\pi R \times 500 \times 10^{-12}}$$

$$\Rightarrow R = 39.7\text{k}\Omega$$

$$\text{Now } Q = \frac{1}{2(\omega - \omega_F)} \Rightarrow 10 = \frac{1}{2(2 - \omega_F)}$$

$$\omega_F = 1 + \frac{R_f}{R_1} = 1.95$$


$$\Rightarrow \frac{R_f}{R_1} = 0.95$$

$$\Rightarrow R_f = 0.95 R_1$$

$$\text{choose } R_1 = 10\text{k}\Omega$$

$$\Rightarrow R_f = 9.5\text{k}\Omega$$

designed circuit as,

 

10) Design a first order wide band-reject filter with a higher cut-off frequency of 100 Hz and lower cut-off frequency of 1 kHz. Calculate  $\omega_0$  of the filter.

$$G.T \quad f_H = 100 \text{ Hz}, \quad f_L = 1 \text{ kHz}$$

For high pass section,  $f_L = 1 \text{ kHz}$

Assume passband gain  $A_F = 2$ .

choose,  $C = 0.01 \mu\text{F}$

$$f_L = \frac{1}{2\pi R C} \Rightarrow R = \frac{1}{2\pi f_L C} = \frac{1}{2\pi \times 10^3 \times 0.01 \times 10^{-6}} = 15.91 \text{ k}\Omega$$

For low pass section,  $f_H = 100 \text{ Hz}$

Assume passband gain  $A_F = 2$ .

choose,  $C' = 0.05 \mu\text{F}$

$$f_H = \frac{1}{2\pi R' C'} = \frac{1}{2\pi R' \times 0.05 \times 10^{-6}}$$

$$\Rightarrow R' = \frac{1}{2\pi f_H C'} = \frac{1}{2\pi \times 100 \times 0.05 \times 10^{-6}} = 31.83 \text{ k}\Omega$$

$$A_F = 1 + \frac{R_f}{R_1} = 2$$

$$\Rightarrow \frac{R_f}{R_1} = 2 - 1 = 1$$

$$\Rightarrow R_f = R_1$$


$$\text{choose } R_f = 10 \text{ k}\Omega \Rightarrow R_f = R_1 = 10 \text{ k}\Omega$$

For summing Amplifier, gain be 1.

$$R_2 = R_3 = R_4 = 10 \text{ k}\Omega$$

$$R_{\text{comp}} = \frac{R_2}{3} = \frac{10}{3} = 3.33 \text{ k}\Omega$$

The designed circuit is,

 

$$f_c = \sqrt{f_H f_L} = \sqrt{100 \times 1 \times 10^3} = 316.22 \text{ Hz}$$

$$B.W = f_L - f_H = 1 \times 10^3 - 100 = 900$$

$$\therefore Q = \frac{f_c}{B.W} = \frac{316.22}{900} = 0.3513$$

## (25)

### narrow band pass filter

KCL A'

$$\begin{aligned} & Y_1(V_a - V_i) + Y_2(V_a - V_b) + Y_3(V_a - V_o) \\ & + Y_4(V_o) = 0 \end{aligned}$$

Virtual short circuit,

$$V_b = 0$$

$$\Rightarrow Y_1(V_a - V_i) + Y_2(V_a) + Y_3(V_a - V_o) + Y_4 V_o = 0$$

$$\Rightarrow V_a [Y_1 + Y_2 + Y_3 + Y_4] - Y_1 V_i - Y_3 V_o = 0$$

$$\Rightarrow V_a [Y_1 + Y_2 + Y_3 + Y_4] = Y_1 V_i + Y_3 V_o \quad \textcircled{1}$$

KCL B'

$$Y_2(V_b - V_o) + Y_5(V_b - V_o) = 0$$

$$\Rightarrow Y_2(0 - V_o) + Y_5(0 - V_o) = 0 \quad [\because V_b = 0]$$

$$\Rightarrow -V_o Y_2 - Y_5 V_o = 0$$

$$\Rightarrow -V_o Y_2 = Y_5 V_o$$

$$\Rightarrow V_o = -\frac{Y_5 V_o}{Y_2} \quad \textcircled{2}$$

sub eq \textcircled{2} in \textcircled{1}


$$\Rightarrow -\frac{Y_5 V_o}{Y_2} [Y_1 + Y_2 + Y_3 + Y_4] = Y_1 V_i + Y_3 V_o$$

$$\Rightarrow -Y_5 V_o [Y_1 + Y_2 + Y_3 + Y_4] = V_o [Y_1 V_i + Y_3 V_o]$$

$$\Rightarrow -V_o [Y_5 [Y_1 + Y_2 + Y_3 + Y_4]] = Y_2 V_i V_o + Y_3 V_o V_o$$

$$\Rightarrow -V_o [Y_5 (Y_1 + Y_2 + Y_3 + Y_4)] = V_o Y_2 V_o = Y_1 V_o V_o$$
 
$$\Rightarrow -V_o [Y_5 (Y_1 + Y_2 + Y_3 + Y_4) + Y_3 V_o] = Y_2 V_i V_o$$



ve. value

$$\Rightarrow \boxed{\frac{V_o}{V_i} = \frac{-Y_1 Y_2}{Y_5 [Y_1 + Y_2 + Y_3 + Y_4] + Y_2 Y_3}}$$

For SPF,  $Y_1 = G_1 = \frac{1}{R_1}$

$$Y_2 = SC_2$$

$$Y_3 = SC_3$$

$$Y_4 = G_4 = \frac{1}{R_4}$$

$$Y_5 = G_5 = \frac{1}{R_5}$$

$$\Rightarrow \boxed{\frac{V_o(s)}{V_i(s)} = \frac{-SC_2 G_1}{G_5 (G_1 + SC_2 + SC_3 + G_4) + SC_2 C_3}}$$

$$\Rightarrow H(s) = \frac{-SC_2 G_1}{SC_2 C_3 + SG_5 (C_2 + C_3) + G_5 (G_1 + G_4)}$$

$$\Rightarrow H(s) = \frac{-SC_2 G_1}{s + SG_5 (C_2 + C_3) + G_5 (G_1 + G_4)}$$

Compare above equation with  $\frac{1}{s^2 + 2\zeta\omega_n s + \omega_n^2}$

$$\Rightarrow \omega_n^2 = \frac{G_5 (G_1 + G_4)}{C_2 C_3}$$

$$\Rightarrow \boxed{\omega_0 = \sqrt{\frac{G_5 (G_1 + G_4)}{C_2 C_3}}}$$

\* Resonant frequency,  $\left. \frac{V_o}{V_i} \right|_{\omega=\omega_0} = \frac{-G_1 C_2}{G_5 (C_2 + C_3)}$

\* Quality factor,  $Q_0 = \frac{\omega_0 C_2 C_3}{G_5 (C_2 + C_3)}$

\* Band width =  $\frac{G_5 (C_2 + C_3)}{2\pi C_2 C_3}$

\* Class  $\epsilon_0 = \epsilon_2 = C$

$$i) \omega_0 = \sqrt{\frac{G_5(C+C_0)}{C}}$$

$$ii) \left. \frac{\partial \omega}{\partial t} \right|_{\omega=\omega_0} = \frac{-G_5 C}{G_5(C+C_0)} = -\frac{G_5 C}{2C+G_5} = -\frac{G_5}{2G_5}$$

$$= -\frac{P_5}{2R_1} = -f_0$$

$$\boxed{A_0 = \frac{P_5}{2R_1}}$$

$$iii) \theta_0 = \frac{\omega_0 \cdot C \cdot C}{G_5(C+C_0)} = \frac{\omega_0 C^2}{2CG_5}$$

$$= \frac{\omega_0 C}{2G_5} = \frac{\omega_0 C P_5}{2}$$

$$iv) \text{ Bandwidth} = \frac{G_5(C+C_0)}{2\pi \cdot \theta_0} = \frac{G_5(2C)}{2C^2\pi} = \frac{G_5}{\pi \cdot C} = \frac{1}{P_5 \cdot \pi C}$$

### Problems

i) choose  $C < 1MF$

$$a) R_5 = \frac{2\omega_0}{\omega_0 \cdot C} = \frac{2\omega_0}{2\pi f_0 C} = \frac{\omega_0}{\pi f_0 C}$$

$$b) R_1 = \frac{P_5}{2A_0} = \frac{\omega_0}{\pi f_0 C \cdot 2A_0} = \frac{\omega_0}{\pi f_0 C \cdot 2A_0}$$

$$c) R_4 = \frac{\omega_0}{2\pi f_0 C (2\omega_0^2 - \omega_0)}$$

[ $\because$  choose  $2\omega_0^2 > \omega_0$   
otherwise we get -ve value]

5. Timers and Phase Locked Loop

Timers:- IC 555 is Linear IC which is mostly used to calculate accurately time delays. Internally it has series combination of three  $5\text{ k}\Omega$  resistors so it called as "555-timer".


\* Packages of 555 timer are

1. 8-Pin min. DIP
2. 14-Pin DIP

\* By using Single 555 timer, we can generate time delays of range 1usec to hours.

\* In XR-2240 timer, we have one 555 timer and one programmable binary counter.

\* In 556 timer it has consists of two 555 timers.

 Features :-

\* It has range of 1usec to hours

\* It has wide range of supply voltages,  $V_{cc} = +5\text{V}$  to  $+18\text{V}$  so that it is versatile and easy to use, reliable and less cost.

\* It can produce a load current of 200mA (or) It can deliver a output load current of 200mA.

\* By using 555 timer, it is possible to adjust the duty cycle i.e by using 555 timers we can generate squarewave and triangular waves.

- \* It can operate in wide range of temperatures
- \* It is designed for operating temperatures ranging from  
 $-55^{\circ}\text{C}$  to  $\pm 125^{\circ}\text{C}$  for NE 555 timer  
 $0^{\circ}\text{C}$  to  $70^{\circ}\text{C}$  for SE 555 timer
- \* It has a temperature stability of  $50 \text{ PPM}/\text{C}$  change in temperature  
 $50 \text{ PPM}/\text{C} \approx 0.005\%/\text{C}$
- \* It is compatible with both TTL and CMOS logic families
  - i) In TTL,  $\rightarrow$  power dissipation is high  
 $\rightarrow$  speed of operation is high
  - ii) In CMOS,  $\rightarrow$  less power dissipation  
 $\rightarrow$  speed of operation is low

### Applications of IC 555 timer :-

1. mono stable multivibrator
2. Astable multivibrator
3. DC-DC converters
4. Digital Logic Probes
5. oscillators
6. waveforms generators such as Ramp, pulse, square wave forms.

7. Analog frequency meters & Tachometers

8. Temperature measurements and control


9. Infrared (IR) transmitters

10. Burglar alarm's and toxic gas alarms

11. Voltage regulator and voltage monitors

 12. Traffic light control

Pin diagram of IC 555 timer :- (IC NE 555 timer)



functions of Pins :- (Pin descriptions)

Pin 1 : Ground :-

All the voltages are measured with respect to this terminal.

Pin 2 :- Trigger :-

The IC 555 uses 2 comparators. The voltage divider

consists of three equal resistances. Due to voltage divider,

the voltage of Non Inverting terminal of comparator 1 is fixed

at  $\frac{V_{cc}}{3}$ . The Inverting input of comparator 2 which is

compared with  $V_{cc}/3$ .

The output of timer changes from one state to another i.e if the voltage at this pin becomes greater than  $\frac{2}{3}V_{cc}$  then output will be low.

If the voltage at this pin becomes lower than  $\frac{1}{3}V_{cc}$  then output will be High.

Pin 3 (outPut):- It is the output pin. A load is connected to this pin.

→ Load can be connected in 2 ways

- i) Between Pin 3 (outPut) and Pin 1 (Ground)
- ii) Between Pin 3 (outPut) and Pin 8 (Supply Voltage).

Pin 4 (Reset):-

This is an interrupt to the timing device. When Pin 4 is grounded, it stops the working of device and makes it off. Thus, Pin 4 provides on/off feature to the IC 555. Input overrides all other functions within the timer when it is momentarily grounded.

Pin 5 (Control voltage Input):-

In most of the applications, external control voltage input is not used. This pin is nothing but inverting input terminal of comparator 1. The voltage divider holds the voltage of this input at  $\frac{2}{3}V_{cc}$ . This is reference level of comparator 1 with

which threshold is compared. If reference level required is other than  $\frac{2}{3}V_{cc}$  for comparator 1 then External Input is to be given to Pin 5.

### Pin 6 (Threshold) :-

This pin is connected to Non-Inverting Input terminal of comparator 1. The external voltage is applied to Pin 6. When this voltage is more than  $\frac{2}{3}V_{cc}$ , comparator 1 output goes high. Due to this output of timer becomes low.

Remember that output at Pin 3 is  $\bar{Q}$  which is complementary output of flipflop.

For threshold  $> \frac{2}{3}V_{cc}$ , flipflop  $\rightarrow$  set,  $Q \rightarrow$  High, output at Pin 3  $\rightarrow$  Low

For trigger  $< \frac{1}{3}V_{cc}$ , flipflop  $\rightarrow$  Reset,  $Q \rightarrow$  Low, output at Pin 3  $\rightarrow$  High

### Pin 7 (Discharge) :-

This pin is connected to collector of discharge transistor  $Q_1$ .

If the output of timer is Low,  $Q_1$  is ON which in turn connects the external capacitor to ground. If the output timer is High,  $Q_1$  OFF which in turn disconnects the external capacitor from ground.

### Pin 8 (Supply Voltage +V<sub>cc</sub>) :-

The IC 555 timer can work with any supply voltage between 4.5V and 16V.

## functional diagram of 555 timer (or) significance of each comparator

 


Fig: functional diagram of 555 IC timer

IC 555 timer contains,

- i) 2-comparators, Non inverting comparator (upper comparator) and Inverting comparator (lower comparator)
- ii) A potential divider network formed by three 5kΩ resistors
- iii) A Power amplifier (or) Inverter
- iv) control flip-flop
- v) Buffer transistor & discharging transistor

→ The voltage divider provides a voltage of  $\frac{2}{3}V_{cc}$  to the Inverting Input of upper comparator and  $\frac{1}{3}V_{cc}$  to the Non Inverting Input of lower comparator. These voltages forms threshold voltage levels of upper and lower comparators. Therefore, they helps to find timing interval.

Hence, the time can be varied by applying modulation voltage to control pin.

→ Initially, Assume that timer is in stable state (or) stand by mode. In this state, output  $\bar{Q}$  of control flip flop is High and it is applied to Power Amplifier.

Power Amplifier is nothing but an Inverter, ie High level signal applied to its input to Low level signal. hence output of timer becomes Low.

→ A negative going external trigger is applied to trigger pin (i.e Inverting input of lower comparator). Here D.c level of -ve trigger pulse should be greater than lower threshold voltage i.e  $\frac{V_{cc}}{3}$ .

when ever -ve trigger passes through lower threshold voltage, the lower comparator provides High output.

Due to this the output of  $\bar{Q}$  of control flip flop changes to Low & Q to High (i.e  $Q=1, \bar{Q}=0$ ). Therefore, output of timer at pin 3 becomes

High.

→ when threshold voltage at Non-Inverting Input of upper comparator exceeds  $\frac{2}{3}V_{cc}$ , the output of upper comparator becomes High. due to this output  $\bar{Q}$  of control flip flop changes back to High ( $Q=0, \bar{Q}=1$ )

Therefore, the output of timer at pin 3 becomes Low. Thus IC 555 timer works.

→ The Pin 1 (Reset pin) is used to reset the timer so as to override the operation of lower comparator.

When the reset is not used it is connected to  $V_{cc}$ . The transistor  $Q_2$  energized by internally available reference voltage  $V_{ref}$ , act as buffer and it is used to isolate the reset input from control flip-flop and discharge transistor  $Q_1$ .

→ When  $\bar{Q}$  of flip flop is Low, the discharge transistor  $Q_1$  will be in OFF condition & Pin 7 is open.


→ When  $\bar{Q}$  of flip flop is High,  $Q_1$  becomes forward biased and conducts due to which Pin 7 will be connected to ground.


### monostable multivibrator:-

The circuit has one stable state and one quasi stable state.

It also called as one-shot (or) mono shot multivibrator.

The functional schematic arrangement as,

 

 

Initially, Assume that the timer is in stable state ( $\bar{Q} = 1$ ) stand by mode.

In this state output  $\bar{Q}$  of control flip flop is High & it is given to transistor  $Q_1$ . Therefore,  $Q_1$  is ON, due to which the external timing capacitor gets clamped to ground (i.e short circuit to ground). Thus the output of timer will be ground potential i.e Low.

Now, when an externally applied -ve going trigger pulse passes through lower threshold voltage ( $\frac{1}{3}V_{cc}$ ), the output of lower comparator is High. Therefore, output  $\bar{Q}$  of flip flop changes to Low i.e  $\bar{Q} = 0$ . Due to this transistor  $Q_1$  will be turned OFF.


Therefore, timing capacitor gets unclamped (disconnected from ground)

and output at times becomes High.

Now, the timing cycle starts. As the timing capacitor is unclamped its voltage starts increase exponentially towards  $V_{CC}$  through resistor  $R$  with a time constant equal to  $RC$ .

After a period of time, say  $T$ , the voltage across  $C$  becomes equal to  $\frac{2}{3}V_{CC}$ , output of upper comparator becomes High thereby resets the flip flop. Therefore,  $Q_1=1$  and  $Q_2$  becomes ON. Due to this capacitor  $C$  gets discharged rapidly to 0V. This makes the output of timer return back to stable state (0V) stand by mode.

waveforms :-

 

## Derivation of pulse width :-

Voltage across capacitor Increases exponentially and is given by

$$V_C = V_{CC} (1 - e^{-t/RC})$$

$$\text{If } V_C = \frac{2}{3} V_{CC}$$

$$\Rightarrow \frac{2}{3} V_{CC} = V_{CC} (1 - e^{-t/RC})$$

$$\Rightarrow \frac{2}{3} = 1 - e^{-t/RC}$$

$$\Rightarrow \frac{2}{3} - 1 = -e^{-t/RC} \quad \Rightarrow \frac{1}{3} = e^{-t/RC}$$

$$\Rightarrow -t/RC = \ln(\frac{1}{3})$$

$$\text{At } t=T$$


$$\Rightarrow -\frac{T}{RC} = \ln(\frac{1}{3})$$

$$\Rightarrow T = 1.1RC$$

## Applications of monostable multivibrator:-
 
### 1. missing Pulse detector:-

when signal Input is at ground level ( $0V$ ), Emitter of transistor  $\alpha_1$ , forward biased and clamps capacitor voltage  $V_C$  to  $0.7V$  i.e. output in high state.



when signal input goes high, the transistor cut-off and capacitor begins to charge.

If input signal again goes low before the 555 completes its timing cycle, voltage across 'C' resets to 0.7V.

 


Fig:- waveforms for missing Pulse detector

## a) pulse position modulation (PPM) :-


In pulse position modulation, the amplitude & width of the pulses are kept constant, while the position of each pulse with reference to the position of reference pulse, is changed according to instantaneous sampled value of modulating signal.

It consists of differentiator and a monostable multivibrator.

The input to the differentiator is a PWM waveform. The differentiator generates +ve and -ve spikes corresponding to leading and trailing edges of the PWM waveform.

Diode D<sub>1</sub> is used to bypass the +ve spikes. The -ve spikes are used to trigger monostable multivibrator.

 
The monostable multivibrator generates the pulses of same width and Amplitude with reference to trigger to give Pulse Position modulated waveform.



### 3) Pulse width modulation (PWM) :-


It is basically Pulse monostable multivibrator with a modulating Input signal applied at control voltage input (pin 5).

Internally, control voltage is

 


is adjusted to  $2/3 V_{cc}$ .

 → externally applied modulating signal changes the control voltage, and hence threshold voltage level of upper comparator. As a result, time period required to charge the capacitor upto threshold voltage level changes, giving pulse width modulated signal at the output.



#### H) Linear ramp generator :-

 

(8)

when a capacitor is charged with a constant current source then linear ramp is obtained.

→ The circuit is used to obtain constant current  $I_c$  is a current mirror circuit, using transistor Q and diode D.

→ The current  $I_c$ , charges capacitor C at a constant rate towards  $+V_{cc}$ .

→ Voltage at Pin 6 i.e. capacitor voltage  $V_c$  becomes  $\frac{2}{3}V_{cc}$ , the comparator makes internal transistor Q<sub>1</sub> ON with in no time.

But while discharging when  $V_c$  becomes  $\frac{1}{3}V_{cc}$ , the 2<sup>nd</sup> comparator makes Q<sub>1</sub> OFF & 'C' starts charging again.

 


Fig:- waveforms of ramp generator


$$\text{Time period, } T = \frac{V_{cc} \cdot C}{3 I_c} \text{ sec}$$

$$I_c = \text{charging current} = \frac{V_{cc} - V_D}{R} = \frac{V_{cc} - V_{BE}}{R}$$

Therefore, frequency is

$$f = \frac{1}{T} = \frac{3I_C}{V_{CC} \cdot C} \text{ Hz}$$

Astable multivibrator using IC 555 :-

 

This circuit has no stable state. The circuit changes its state alternately. Hence the operation is also called free running nonsinusoidal oscillator.

In case of Astable multivibrator, external timing resistor ( $R$ ) is divided into 2 parts i.e.  $R_1, R_2$ . The control pin (i.e. Inverting terminal of upper comparator) is connected to ground through capacitor of  $0.01\text{MF}$ . The Threshold pin (i.e. Non Inverting terminal of upper comparator) and trigger pin (i.e. Inverting terminal of lower comparator) are connected to  $V_C$  terminal.

When power supply  $V_{CC}$  is ON, external timing capacitor starts charging towards  $V_{CC}$  at a rate of  $(R_1+R_2)C$ .


During charging period, output of upper comparator is Low, whereas the output of lower comparator is High. Therefore,  $\bar{Q}_1$  output is Low, hence output of timer is High.

The voltage across capacitor becomes greater than upper threshold voltage i.e.  $\frac{2}{3}V_{CC}$ , output of upper comparator is High, due to which output  $\bar{Q}_1$  is High and output of timer becomes Low. Therefore, transistor  $Q_1$  is switched ON, which in turn makes the capacitor to discharge at a rate of  $R_2C$  to 0V through  $R_2$  and  $Q_1$ .

As soon as the voltage across capacitor becomes lower than lower threshold voltage i.e.  $\frac{1}{3}V_{CC}$ , output of lower comparator becomes Low, due to which output of  $\bar{Q}_1$  is Low and output of timer becomes High.

this makes the Q off and capacitor C gets unclamped. Thus the capacitor charges to  $\frac{2}{3}V_{cc}$  and discharged to  $\frac{1}{3}V_{cc}$  periodically.

 In this state of operation the output will be maintained at high for a period of time that is required for capacitor to charge from  $\frac{1}{3}V_{cc}$  to  $\frac{2}{3}V_{cc}$ .



The voltage across the capacitor is given by

$$V_c = V_{cc} (1 - e^{-t/RC}) \quad \text{--- (1)}$$

At  $t=t_1$ , capacitor charges from 0 to  $\frac{2}{3}V_{cc}$

$$\text{i.e. } V_c = \frac{2}{3}V_{cc}, t = t_1$$

$$\text{or (1)} \Rightarrow \frac{2}{3}V_{cc} = V_{cc} (1 - e^{-t_1/RC})$$

$$\Rightarrow \frac{2}{3} = 1 - e^{-t_1/RC}$$

$$\Rightarrow e^{-t_1/RC} = 1 - \frac{2}{3} \\ = \frac{1}{3}$$

$$\Rightarrow -\frac{t_1}{RC} = \ln(\frac{1}{3})$$

$$\Rightarrow t_1 = -RC \ln\left(\frac{1}{3}\right)$$

$$\therefore t_1 = 1.09 RC \quad \text{--- (2)}$$

At time  $t_2$ , capacitor charge from 0 to  $\frac{1}{3}V_{cc}$

i.e.,  $t=t_2$ ,  $V_c = \frac{1}{3}V_{cc}$  eq (1) becomes

$$\frac{1}{3}V_{cc} = V_{cc} \left(1 - e^{-t_2/RC}\right)$$

$$\Rightarrow e^{-t_2/RC} = 1 - \frac{1}{3}$$

$$= \frac{2}{3}$$

$$\Rightarrow t_2 = -RC \ln(0.6)$$

$$\therefore t_2 = 0.405 RC \quad \text{--- (3)}$$

Therefore, time required by the capacitor to charge from  $\frac{1}{3}V_{cc}$  to  $\frac{2}{3}V_{cc}$

is,

$$\begin{aligned} t_{\text{High}} &= t_1 - t_2 \\ &= 1.09RC - 0.405RC \\ &= 0.69RC \end{aligned}$$

From circuit,  $R = R_A + R_B$

$$\Rightarrow t_{\text{High}} = 0.69(R_A + R_B)C \quad \text{--- (4)}$$

The output is low, capacitor discharges from  $\frac{2}{3}V_{cc}$  to  $\frac{1}{3}V_{cc}$ , voltage across capacitor is given by,

$$\frac{1}{3}V_{cc} = \frac{2}{3}V_{cc} e^{-t/RC}$$

$$\Rightarrow \frac{1}{2} = e^{-t/RC}$$

$$\Rightarrow \ln\left(\frac{1}{2}\right) = -\frac{t}{RC}$$

$$\Rightarrow -RC \ln(2) = b$$

$$\Rightarrow \boxed{t = 0.69RC} \quad \text{--- (5)}$$

From the circuit,  $R_A = R_B$

$$\Rightarrow t = 0.69 R_{BC}$$

$\therefore$  total time ( $T$ ) =  $t_{high} + t_{low}$

$$= 0.69 (R_A + R_B)C + 0.69 R_{BC}$$

$$T = 0.69 (R_A + 2R_B)C \quad \text{--- (6)}$$

$$\therefore f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C} \quad \text{--- (7)}$$

The duty cycle of the circuit is defined as the ratio of ON time to the total Period <sup>of</sup> time.

i.e.  $D = \frac{t_{low}}{T} \times 100$

$$\% D = \frac{R_B}{R_A + 2R_B} \times 100$$

If  $R_A = R_B$ ,  $\Rightarrow \% D = 33.33\%$

If the output voltage high time is considered

$$\% D = \frac{t_{high}}{T} \times 100$$


$$= \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

If  $R_A = R_B$ ,  $\Rightarrow \% D = 66.67\%$

$\rightarrow$  If we need  $\% \text{duty cycle} = 50\%$  i.e.  $t_{high} = t_{low}$ . For that if we make  $R_A = 0$  then we will get 50%.
 
### Schematic diagram:-


It shows the schematic diagram of Astable timer circuit. It contains  $R_A$ ,  $R_B$  & C. Pin 4 is tied to pin 8 & Pin 5 is grounded through a small capacitor.



### Applications of Astable multivibrator :-
 
#### 1. square wave generator:-

To observe expression of duty cycle, it is not possible to achieve 50% duty cycle.




To get exactly 50% duty cycle

i.e square wave output is necessary to modify the Astable timer circuit

In modified circuit, capacitor C charges through  $R_A$  and

diode D and discharges through  $R_B$ . To obtain square wave (50% duty cycle) resistance  $R_B$  is adjusted such that it is equal to summation of  $R_A$  and forward resistance of diode D. Usually potentiometers used for exact adjustments of resistors.

### waveforms:-

 


## 2) Voltage controlled oscillator (VCO):-

It is basically an Astable multivibrator circuit with variable control voltage.

→ we know that, internally control voltage is at  $\frac{2}{3}V_{cc}$ .


→ In this circuit control voltage is externally set by the potentiometer.

 → To change control voltage, upper threshold voltage changes and time required to charge capacitor upto upper threshold voltage changes. similarly discharge time also changes. As a result, frequency of output voltage changes.



- If control voltage is increased, capacitor will take more time to charge and discharge and frequency will decrease.
- If control voltage is decreased, capacitor will take less time to charge and discharge, it increases frequency of output signal. so, varying control voltage, we can change the frequency.

### 3. FSK Generator:-

 

→ Binary inputs 1 and 0, it can be transmitted by shifting a carrier frequency. This type of transmission is called frequency shift keying (FSK) technique.

→ When digital input is High (logic 1), transistor  $T_1$  OFF & 555 timer works in normal astable mode.

The frequency of output waveform is

$$f_o = \frac{1.45}{(R_A + 2R_B)c} \quad (\text{or}) \quad \frac{1.45}{(R_1 + 2R_2)c}$$

→ When input is Low (logic 0), Transistor  $T_1$  ON, and it connects resistance  $R_p$  in parallel with  $R_1$ .

The frequency of output is,

$$f_o = \frac{1.45}{[(R_1 || R_p) + 2R_2]c}$$

#### 4. Adjustable duty cycle :-

This circuit is similar to square wave generator, but instead of connecting diode across  $R_B$  it is connected across a combination of variable  $R_2$  &  $R_3$ .

The resistance  $R_2$  is variable and it added to  $R_1, R_3$  to change the charging and discharging resistance.

The charging time of capacitor is,

$$T_C = (R_1 + \text{part of } R_2) 0.693 C$$

The discharging time of capacitor is,

$$T_D = (R_3 + \text{remaining part of } R_2) 0.693 C$$

$$\therefore T = T_D + T_C = 0.693 C [R_1 + R_2 + R_3]$$

$$f = \frac{1}{T} = \frac{1.44}{(R_1 + R_2 + R_3) C}$$


Ques, Position of  $R_2$  potentiometer is A. i.e. part of  $R_2$  in series with  $R_1$  is zero &  $R_2$  added to  $R_3$

$$\therefore T_C = R_1 0.693 C$$

$$\& T_D = (R_2 + R_3) 0.693 C$$

$$\therefore T = 0.693 C [R_1 + R_2 + R_3]$$

No change in frequency but,

 

$$\therefore D_{\min} = \frac{T_C}{T} \times 100 = \frac{0.693 R_1 C}{0.693 C (R_1 + R_2 + R_3)} \times 100$$

$$\boxed{\therefore D_{\min} = \frac{R_1}{R_1 + R_2 + R_3} \times 100}$$

Thus min. duty cycle, less than 50% is possible.

For, R<sub>2</sub> Potentiometer position at B, max. duty cycle is possible

$$\therefore T_C = 0.693 (R_1 + R_2) C$$

$$\& T_D = 0.693 R_3 C$$

$$\therefore T = 0.693 (R_1 + R_2 + R_3) C$$

$$\therefore \therefore D_{\max} = \frac{T_C}{T} \times 100 = \frac{0.693 (R_1 + R_2) C}{0.693 (R_1 + R_2 + R_3) C} \times 100$$

$$\boxed{\therefore D_{\max} = \frac{R_1 + R_2}{R_1 + R_2 + R_3} \times 100}$$


Schmitt trigger (or) 555 timer as a Schmitt trigger :-

The input is given to pins 2 & 6 which are tied together.

Pins 4, 8 are connected to supply voltage (V<sub>cc</sub>).


The common point of 2 pins 2 & 6 is externally biased at  $\frac{V_{cc}}{2}$  through resistance network R<sub>1</sub>, R<sub>2</sub>.

 Generally, R<sub>1</sub>=R<sub>2</sub>, to get biasing of  $\frac{V_{cc}}{2}$ .




The upper comparator will trip at  $\frac{2}{3}V_{cc}$  while lower comparator at  $\frac{1}{3}V_{cc}$ . The bias provided by  $R_1$  and  $R_2$  is centered with in 2 thresholds.

 when a sinusoidal wave whose amplitude is greater than  $\frac{2}{3}V_{cc} - \frac{1}{3}V_{cc}$  is applied to circuit, the comparators get triggered at reference level thereby causing internal control flip flop to set and reset alternatively. Due to this, square wave is generated at the output.



Sine wave is changed to square wave without changing the frequency. Therefore, this circuit used as wave shaping circuit.

## Phase Locked Loop (PLL) :-

 

### 1. Phase detector (or) phase comparator :-

when an Input voltage ( $v_s$ ) of frequency  $f_s$  is applied to circuit, The phase comparator compares it output voltage  $v_e$ . If the frequency of two incoming signals are different, it will generate difference signal, it also called error voltage. It contains output having both high frequency components ( $f_s + f_{out}$ ) and low frequency components ( $f_s - f_{out}$ ). This error output is applied to low pass filter.

2. Low pass filter :- The output of Phase detector is given to Input of LPF. It contains both high frequency components and low frequency components, LPF allows only low frequency components and reject all high frequency components. So, the output of low pass filter (LPF) contains only ( $f_s - f_{out}$ ) signals and it applied to Input of Amplifier.

3. Amplifier :- The output of low pass filter is given to Input of Amplifier. It is used to amplifies the signal and given to VCO.

→ It amplifies the error voltage, it also called as error Amplifier.

#### 4. Voltage controlled oscillator (VCO);-

Initially PLL is in free running state. When the output of Amplifier is given to VCO as its control voltage, based on control voltage VCO shifts its frequency in order to make it equal to input frequency. During this action PLL is said to be in "capture mode".

→ The output of frequency of VCO becomes equal to frequency of input signal,  $f_{in} - f_{out} = 0$ . In this condition PLL is said to be in "locked mode".

In locked mode PLL tracks the frequency of Input signal.

This cycle repeats and PLL tracks the changes in input frequency.

#### Important definitions related to PLL:-

1. Lock-in range:- once the PLL is locked, it can track frequency changes in the incoming signal. The range of frequencies over which the PLL can maintain lock with the incoming signals is called "lock range" (or) "tracking range".

#### 2. capture range:-

The range of frequencies over which the PLL can acquire lock with an input signal is called "capture range".

3. Pull-in time:- The total time taken by the PLL to establish a lock is called pull-in time.

Individual blocks in PLL :-

1. Phase detector / comparator :-

There are 2 types of Phase detectors





1. Analog phase detector

2. Digital phase detector

1. Analog phase detector :- There are 2 types i.e 1. switch type

2. Balanced modulator type

i) switch type phase detector :-

    

above fig. shows basic circuit and waveforms of Analog Phase detector.

→ switch 's' is opened & closed by signal coming from V<sub>CO</sub>.

The switch is closed when V<sub>CO</sub> output is +ve otherwise it is open.

i) when  $\phi = 0^\circ$ :-

when switch 's' is closed only when V<sub>CO</sub> output is +ve, the output waveform V<sub>E</sub> will be half sinusoids (shaded portion) shown in fig 'c'.

ii) when  $\phi = 90^\circ$ :- The output waveform V<sub>E</sub> contains half portion of negative cycle and half portion of +ve cycle shown in fig 'd'.

iii) when  $\phi = 180^\circ$ :- The output waveform V<sub>E</sub> contains -ve half sinusoids shown in fig 'e'.

This type of phase detector is called half wave detector, since the phase information for only one half of input waveform is detected and averaged.

→ It may be seen that the error voltage is zero when phase shift between 2-inputs (V<sub>S</sub> and V<sub>CO</sub>) is  $90^\circ$ , this is a perfect lock condition.

Analysis :-

phase comparator actually multiplies input signal (V<sub>S</sub> = V<sub>S</sub> sin(2πf<sub>s</sub>t)) by the V<sub>CO</sub> signal (V<sub>CO</sub> = V<sub>CO</sub> sin(2πf<sub>CO</sub>t + φ)).

The output is

$$V_e = KV_s V_o \sin(2\pi f_s t) \sin(2\pi f_o t + \phi) \quad \text{--- (1)}$$

where,

$K \rightarrow$  constant

$\phi \rightarrow$  phase shift between input signal and vco output

$$\Rightarrow V_e = \frac{KV_s V_o}{2} [\cos(2\pi f_s t - 2\pi f_o t - \phi) - \cos(2\pi f_s t + 2\pi f_o t + \phi)] \quad \text{--- (2)}$$

At lock condition,  $f_s = f_o$

$$V_e = \frac{KV_s V_o}{2} [\cos(-\phi) - \cos(2\pi \times 2f_o t + \phi)] \quad \text{--- (3)}$$

eq(3), shows phase detector output contains double frequency term and d.c term.

The d.c term  $\frac{KV_s V_o}{2} \cos \phi$  varies as a function of phase  $\phi$ , ie  $\cos \phi$  between 2 signals.

The double frequency term is filtered by LPF and d.c term is applied to modulating input terminal of vco. The dc term ie dc error voltage is zero at  $\phi = 90^\circ$ . Therefore, perfect lock condition  $f_s = f_o$  and  $\phi = 90^\circ$ .

Problems associated with switch type phase detector :-

1. The output voltage  $V_e$  is proportional to input signal amplitude  $V_s$ . This is undesirable since it makes phase detector gain and loop gain dependent on input signal amplitude.
2. The output is proportional to  $\cos \phi$  and not proportional to  $\phi$  making it non-linear.

## 2. Balanced modulator type Phase detector:-

The problems in switch type phase detector can be eliminated by making amplitude of input signal constant. This can be achieved by converting sinusoidal input signal into square wave input signal.

 


Fig:- Balanced modulator type phase detector

The input signal is applied to differential pair  $Q_1 Q_2$ .

Transistors  $Q_3-Q_4$  and  $Q_5-Q_6$  are 2 sets of SPDT (single pole double throw) switches activated by  $V_{c0}$  output.

 


Fig:- wave forms of Balanced modulator Phase detector

when  $V_s$  is +ve,  $\phi \in Q_1$  ON and  $Q_2$  OFF. when  $V_b$  is +ve  $Q_3, Q_6 \rightarrow$  ON

$Q_4, Q_5 \rightarrow$  OFF.

when  $V_s$  is -ve,  $Q_1$  OFF,  $Q_2$  ON. when  $V_b$  is -ve  $Q_3, Q_6 \rightarrow$  OFF  
 $Q_4, Q_5 \rightarrow$  ON.

The output error Voltage is given by

$$V_e = I_E R_L$$

The average value of phase detector output  $V_e$  can be calculated as,

$$(V_e)_{avg} = \frac{1}{\pi} [ (area A_1) + (area A_2) ]$$

$$\begin{aligned}
 &= \frac{1}{\pi} [(-I_E R_L)(\pi - \phi) + I_E R_L (\phi)] \\
 &= \frac{I_E R_L}{\pi} [-\pi + \phi + \phi] = \frac{2I_E R_L}{\pi} [\phi - \frac{\pi}{2}] \\
 &= \frac{4I_L R_L}{\pi} [\phi - \frac{\pi}{2}] \quad (\because I_E = 2I_L) \\
 &= K_\phi (\phi - \frac{\pi}{2}) \quad \text{where } K_\phi = \frac{4I_L R_L}{\pi}
 \end{aligned}$$

where  $K_\phi \rightarrow$  Phase angle-to-voltage transfer coefficient (or)  
conversion ratio of phase detector.

 


Fig:- Relationship between  $V_e$  and  $\phi$



## 2. Digital Phase detector:-

The XOR gate can be used as a digital phase detector

when both signal  $f_s$  and  $f_o$  are square waves.

The output of XOR gate is high when only

one of the inputs is high.

  

Input/output waveforms

According to waveform,  $f_s$  is leading  $f_o$  by  $\phi$  degrees.

From fig, when  $\phi=0$ ,  $V_{dc}=0$  and when  $\phi=\pi$ ,  $V_{dc}=V_{cc}$ .

 


Fig :- Relationship between  $V_{dc}$  and  $\phi$

The conversion ratio  $K_\phi$  for a supply voltage  $V_{cc}$  is:

$$K_\phi = \frac{V_{cc}}{\pi}$$

If  $V_{cc} = 5V$ ,  $K_\phi = 5/\pi = 1.591 \text{ V/rad.}$


### Low Pass filter :-

The low pass filter not only removes high frequency components and noise, but also controls the dynamic characteristics of PLL. These characteristics include capture range, lock range, Bandwidth, transient response.


If filter band width is reduced, response time increases.

Bandwidth of filter reduces, reducing capture range of PLL.

 The filters may be either passive (or) active type



a) LPF

 

b) Passive filter

 


Fig :- Active filter

### Voltage controlled oscillator (VCO) :-

A common type of VCO available in IC form is NE/SE 566.


 


Fig :- Pin-configuration

- Timing capacitor  $C_T$  is linearly charged (or) discharged by constant current source/sink.
- The amount of current can be controlled by changing  $V_C$  applied at modulating input (Pin 5) or changing timing resistor  $R_T$  external to IC chip.

→ The voltage at Pin 5 is held same voltage as Pin 6.

 → If modulating voltage at Pin 5 is increased, voltage at Pin 6 also increases, resulting less voltage across  $R_T$  thereby decreasing charging current.



- A small capacitor  $0.001\text{MF}$  should be connected between pins 5 and 6 to eliminate possible oscillations.
- The voltage across  $C_T$  is applied to inverting terminal of schmitt trigger  $A_2$  via buffer amplifier  $A_1$ .
- The voltage across schmitt trigger is designed to  $V_{cc}$  and  $0.5V_{cc}$ . If  $R_a = R_b$  in +ve feed back loop, voltage at non-inverting terminal of  $A_2$  swings from  $0.5V_{cc}$  to  $0.25V_{cc}$ .
- The voltage on capacitor  $C_T$  exceeds  $0.5V_{cc}$  during charging, the output of schmitt trigger goes low ( $0.5V_{cc}$ ).
- Now capacitor discharges when it is at  $0.25V_{cc}$ , the output of schmitt trigger goes high ( $V_{cc}$ ).
- we get triangular waveform across  $C_T$  which is available at Pin 4.
- <sup>Inverted</sup>  
square wave output is available at Pin 3.

 
 
 


Fig:- output waveform

The output frequency of VCO can be calculated as

The total voltage on capacitor changes from  $0.25V_{CC}$  to  $0.5V_{CC}$ .

$$\text{so, } \Delta V = 0.25V_{CC}.$$

$$\frac{\Delta V}{\Delta t} = \frac{i}{C_T}$$

$$\frac{0.25V_{CC}}{\Delta t} = \frac{i}{C_T}$$

$$\Rightarrow \Delta t = \frac{0.25V_{CC} C_T}{i} \quad \text{--- ①}$$

Total Time period of triangular waveform  $= 2\Delta t$ .

frequency of oscillator  $f_0 = \frac{1}{T} = \frac{1}{2\Delta t}$

$$= \frac{i}{0.5V_{CC} C_T} \quad \text{--- ②}$$

$$\text{But } i = \frac{V_{CC} - V_C}{R_T}$$

$$\Rightarrow f_0 = \frac{2(V_{CC} - V_C)}{V_{CC} C_T R_T} \quad \text{--- ③}$$

The output frequency of VCO can be changed either by i)  $R_T$  ii)  $C_T$   
 iii) The voltage  $V_C$  at modulating input terminal Pin 5.

→ modulating input voltage

is varied from  $0.75 V_C$  to  $V_C$

which can produce a

frequency variation about 10 to 1.

→ with no modulating input signal,

voltage at Pin 5 is biased at  $(\frac{7}{8})V_{CC}$

 


Fig:- pin configuration for VCO.

$$\Rightarrow f_0 = \frac{\alpha(V_{CC} - (\frac{7}{8})V_{CC})}{V_{CC} R_T C_T} = \frac{1}{4R_T C_T} = \frac{0.25}{R_T C_T} \quad \text{--- (4)}$$

Voltage to frequency conversion factor ( $K_V$ ):-

$$K_V = \frac{\Delta f_o}{\Delta V_C} \quad \text{--- (5)}$$

$\Delta V_C \rightarrow$  modulation voltage required to produce the frequency shift  $\Delta f_o$  for a VCO.

$$\Delta f_o = f_i - f_o = \frac{\alpha(V_{CC} - V_C + \Delta V_C)}{R_T C_T V_C} - \frac{\alpha(V_{CC} - V_C)}{R_T C_T V_C} = \frac{2\Delta V_C}{R_T C_T V_C}$$

$$\Rightarrow \Delta V_C = \frac{\Delta f_o R_T C_T V_C}{2} \quad \text{--- (6)}$$

Put value of  $R_T C_T$  from eq(4),

$$\Delta V_C = \Delta f_o V_{CC} / 8f_o$$

$$(\text{or}) K_V = \frac{\Delta f_o}{\Delta V_C} = \frac{8f_o}{V_C} \quad \text{--- (5)}$$


## Functional diagram of 565 (OT) Internal block diagram of 565 :-

565 is available in 14-DIP Package  
and 10-Pin metal can Package.


The output frequency of VCO  
is given by

$$f_0 = \frac{0.25}{R_T C_T} \text{ Hz}$$

 where  $R_T, C_T$  are external  
resistor and capacitor  
connected to Pin 8, 9.



 The values of  $R_T, C_T$  are adjusted such that free running freq.  
will be at center of input frequency range.  
The value of  $R_T$  is restricted from 2k $\Omega$  to 20k $\Omega$ , capacitor have  
any value.



→ capacitor  $C_2$  connected between pin 7 and +ve supply (pin 10)

forms 1<sup>st</sup> order low pass filter with internal resistance of 3.6 k $\Omega$

→ The value of  $C_2$  should be large enough to eliminate possible oscillations in VCO voltage.

The lock range and capture range for IC565 PLL are given by

$$f_L = \pm \frac{8f_0}{V} \text{ Hz}$$

$$\text{and } f_c = \pm \left[ \frac{f_L}{2\pi(3.6)(10^3)C_2} \right]^{1/2}$$

Derivation of Lock-in range :-

If  $\phi$  radians is the phase detector difference between analog signal and VCO voltage, The output voltage of phase detector is

$$V_e = K_\phi (\phi - \pi/2) \quad \begin{matrix} K_\phi \rightarrow \text{phase angle-to-voltage transfer} \\ \text{coefficient} \end{matrix} \quad \text{--- (1)}$$

The control voltage is,

$$V_c = A K_\phi (\phi - \pi/2) \quad \begin{matrix} A \rightarrow \text{Gain} \end{matrix} \quad \text{--- (2)}$$

$V_c$  shifts VCO frequency from its free running frequency

$f_0$  to frequency  $f$ ,

$$f = f_0 + K_V V_c \quad \text{--- (3)}$$

$K_V \rightarrow$  voltage to frequency transfer coefficient

PLL is locked into signal frequency  $f_s$ ,

$$f = f_s = f_0 + K_V V_c$$

$$V_c = (f_s - f_0) / K_V = A K_\phi (\phi - \pi/2)$$

$$\Rightarrow A K \phi (\phi - \pi/2) = (f_s - f_0)/K_V$$

$$(\phi - \pi/2) = (f_s - f_0)/K_V A K \phi$$

$$\Rightarrow \phi = \frac{\pi}{2} + (f_s - f_0)/K_V A K \phi$$

max. output voltage magnitude available from phase detector

$$\text{occurs for } \phi = \pi, V_C(\text{max}) = \pm K \phi \frac{\pi}{2}$$

$$(f - f_0)_{\text{max}} = K_V V_C(\text{max})$$

$$V_C(\text{max}) = \pm \frac{\pi}{2} K \phi A$$

max. vco frequency swing that can be obtained

$$(f - f_0)_{\text{max}} = K_V V_C(\text{max})$$

$$= K_V K \phi A (\pi/2)$$

max. range of signal frequency over which PLL can remain

locked

$$f_s = f_0 \pm (f - f_0)_{\text{max}}$$

$$= f_0 \pm K_V K \phi (\pi/2) A$$

$$= f_0 \pm \Delta f_L$$

$2 \Delta f_L$  will be lock-in freq. range

$$2 \Delta f_L = K_V K \phi A \pi$$

$$\Delta f_L = \pm K_V K \phi A (\pi/2)$$

free running frequency  $f_0$ ,

$$K_V = \frac{8 f_0}{V}$$

$$V = V_{CC} - (-V_{CC})$$

$$K\phi = \frac{1.4}{\pi}$$

$$A = 1.4$$

Lock-In-range,  $\Delta f_L = \pm 7.8 f_0/V$

$$\boxed{\Delta f_L = \pm \frac{7.8}{V} f_0}$$

Derivation of capture range:-

The phase angle difference between the signal and vco output voltage will be

$$\phi = (\omega_s t + \theta_s) - (\omega_o t + \theta_o) = (\omega_s - \omega_o)t + \Delta\theta \quad \{ \because \Delta\theta = \theta_s - \theta_o \}$$

Phase angle difference does not maintain constant it will be change with time at a rate given by

$$\frac{d\phi}{dt} = \omega_s - \omega_o$$

$$\therefore \Delta f = f_s - f_o$$

Low Pass filter is a simple RC network having

$$T(jf) = \frac{1}{1+j(f/f_i)}$$

where  $f_i = \frac{1}{2\pi RC}$  is the 3-dB point of LPF. Slope position of LPF where  $(f/f_i) \gg 1$

$$T(f) \approx \frac{f_i}{jf} \Rightarrow T(\Delta f) \approx \frac{f_i}{\Delta f}$$

The fundamental frequency term supplied to LPF by the phase detector will be difference frequency  $\Delta f = f_s - f_o$

The Voltage  $V_C$  to drive the VCO is,

$$V_C = V_b \times T(f) \times A$$

$$V_{C(\max)} = V_{C(\max)} \times T(f) \times A$$

$$= \pm K_\phi (\pi/2) A (f_1/\Delta f)$$

The corresponding value of max. VCO frequency shift is,

$$(f-f_0)_{\max} = K_V V_{C(\max)}$$

$$= \pm K_\phi K_V (\pi/2) A (f_1/\Delta f)$$

nb  $f = f_S$ , max. signal frequency range,

$$(f_S - f_0)_{\max} = \pm K_V K_\phi (\pi/2) A (f_1/\Delta f_c)$$

$$\text{Now } \Delta f_c = (f_S - f_0)_{\max}$$

$$(\Delta f_c)^2 = K_V K_\phi (\pi/2) A f_1$$

$$\Delta f_L = \pm K_V K_\phi (\pi/2) A$$

$$\text{we get, } (\Delta f_c) \approx \pm \sqrt{f_1 \Delta f_L}$$

Total capture range is,  $2\Delta f_c \approx 2\sqrt{f_1 \Delta f_L}$

$$\text{lock-in-range} = 2\Delta f_L$$
$$= K_V K_\phi A \pi$$

$$(\Delta f_c)^2 = \Delta f_L \times f_1$$

$$\Delta f_c = \sqrt{\Delta f_L \times f_1}$$

$$f_1 = \frac{1}{2\pi R_1 C_1}$$


$$\Delta f_c = \sqrt{\frac{\Delta f_L}{2\pi R_1 C_1}} \Rightarrow \Delta f_c = \left( \frac{\Delta f_L}{2\pi R_1 C_1} \right)^{1/2}$$

In 565 PLL,  $R_1 = 3.6 \text{ k}\Omega$

$$\Rightarrow \Delta f_c = \left[ \frac{\Delta f_L}{2\pi \times 3.6 \times 10^3 \times C_1} \right]^{1/2}$$

### Applications of PLL:-

#### 1. Frequency multiplier/division :-

 

In this arrangement uses a divided by  $N$  network between VCO output and Phase comparator.

i) when PLL is in locked mode, In this condition output of frequency divider is same as the input frequency  $f_s$ . Therefore, VCO output is multiple of  $f_s$ .


$$f_{out} = N f_s \quad N \rightarrow \text{Integer} \quad (\text{or}) \quad f_{out} = N f_s$$

ii) when PLL is in harmonic locking mode, If the input signals are rich in harmonics e.g. square wave, pulse train etc.. then VCO can be locked directly to  $n$ th harmonic of input. As the amplitude of higher harmonics decreases with increase of order, The order (or) value of  $n$  is maintained below 10.

frequency division obtained by locking  $m^{\text{th}}$  order harmonic of VCO output, since it is rich in harmonics.

$$\text{the output } f_o = \frac{f_{in}}{m} \quad (\text{or}) \quad f_o = \frac{f_0}{m}$$

## a) Frequency Translation:-

 

Input signal  $f_S$  and VCO output frequency  $f_{out}$  applied to multiplier. It has 2 inputs and output is  $f_{out} \pm f_S$ . This output of multiplier is applied to LPF. It allows only low frequencies and rejects high frequency so output of LPF will be  $f - f_{in}$ .


In locked state of PLL,

$$f_{out} = f_{in} = f \quad (\text{or})$$

$$f = f_{out} - f_S$$

$$\Rightarrow f_{out} = f + f_S$$
 
### 3. AM detection (or) AM demodulator :-




when an AM signal is applied to circuit, PLL gets locked to the carrier frequency of AM signal, and VCO present inside the PLL produces a signal whose frequency is same as the carrier of AM Signal. Thus the VCO output of PLL is applied to multiplier.

when AM signal passes through phase shift circuit, the Phase shift of signal changes by  $90^\circ$ , since under locked state of PLL, output of VCO will be  $90^\circ$  out of phase with Input. The phase shifted signal applied to multiplier. The 2 signals applied to multiplier are in same phase. The output of multiplier given to LPF, which rejects high frequency components and passes only low frequency components. The signal obtained at output of filter is demodulated output.

→ AM demodulator using PLL has

- i) High degree of selectivity
- ii) High degree of noise immunity.

## 4. FM demodulation:-

 

when PLL is Locked in FM signal, VCO frequency follows the instantaneous frequency of the FM signal, and error voltage (or) VCO control voltage is proportional to deviation of input frequency from the center frequency. Therefore, ac component of error voltage (or) control voltage of VCO will represent true replica of modulating voltage that is applied to FM carrier at transmitter. The faithful reproduction of modulating voltage depends on linearity between instantaneous frequency deviation and control voltage of VCO.


Note that FM frequency deviation and modulating frequency should remain in locking range of PLL to get faithful replica of modulating signal.

If the product of modulation freq.  $f_m$  and freq. deviation exceeds  $(\Delta f)^2$ , VCO will not be able to follow the instantaneous frequencies of FM signal.
 
## 5 Frequency shift keying (FSK) demodulator :-

Binary data transmitted by means of carrier frequency.  
It uses 2 carrier frequencies logic 0 (or) logic 1. This type of data transmission is called frequency shift keying.

In this data transmission, on receiving end, 2 carrier frequencies are converted into 1 and 0 to get original data. This process is called FSK demodulation.



Let us consider 2 frequencies, 1-freq. represents as '0' another freq. as '1'. If PLL remain in locked into FSK signal at both  $f_1, f_2$  VCO control voltage which is also supplied to the comparator will given as

$$V_{C1} = (f_1 - f_0) / K_V$$

$$\& V_{C2} = (f_2 - f_0) / K_V$$

where  $K_V \rightarrow$  voltage to frequency transfer coefficient.

The difference between 2 control voltage levels will be

$$\Delta V_C = (f_2 - f_1) / k_V$$


The reference voltage for comparator is derived from additional lowpass filter and it is adjusted midway between  $V_{C1}, V_{C2}$ .

Therefore,  $V_{C1}, V_{C2}$  comparator gives output as '0' and '1'.

## 6. A/D and D/A converters

### Introduction:-
 
#### Basic blocks Preceding an A/D and D/A converters :-



→ sensor/transducer measures different physical Parameters such as temperature, pressure, voltage, current etc. and provides output in Analog form.

→ The output of sensor is applied to Antialiasing filter. In this section, high frequency noise signals are eliminated only low frequency output is passed to sample and Hold circuit.


→ The function of sample and Hold circuit is to sample the output of filter at frequency which is greater than twice the maximum frequency of its input. and maintain constant value during process of Analog to digital conversion.

- The ADC converts sample and signal to its digital equivalent signal which is displayed on monitor of controlling system in which a control algorithm is loaded.
- control algorithm measures (or) compares the measured value with set value.
- D/A converter converts digital binary signal to staircase signal which is given to smoothing filter.
- smoothing filter eliminates quantization noise and produces analog signal.
- To maintain the parameter within the set point limits and to get output from plant.

#### Applications :-

1. Digital and audio recording and playback
2. music and video synthesis
3. Direct digital control
4. Data Acquisition
5. Digital signal Processing
6. Pulse code modulation
7. Digital multimeter
8. microprocessor based instrumentation

## D/A converters:-

 

$b_1 \rightarrow$  most significant bit (MSB) &  $b_n \rightarrow$  least significant bit (LSB)

mathematically,

$$V_o = K V_{FS} (b_1 \bar{a}^1 + b_2 \bar{a}^2 + \dots + b_n \bar{a}^n)$$

where,  $V_o \rightarrow$  output voltage

$K \rightarrow$  scaling factor usually it is unity


$V_{FS} \rightarrow$  full scale output voltage.

## D/A conversion techniques:-

1. weighted resistor method (or) Binary weighted resistor D/A converter
2. R-2R Ladder network method
3. Inverted R-2R Ladder network method
4. multiplying DAC (IC 1408)
 
### 1. Binary weighted Resistor D/A converter:-

A binary weighted resistor DAC consists of binary weighted resistor network ( $\bar{a}R, \bar{a}^2R, \bar{a}^3R, \dots, \bar{a}^nR$ ), summing amplifier (either connected in inverting mode (or) non inverting mode) and  $n$ -electronic switches ( $d_1, d_2, d_3, \dots, d_n$ ).



From the figure, switch positions are controlled by digital inputs.

- \* When digital input is '1', corresponding switch is connected to reference voltage.
- \* When digital input is '0', switch is connected to Ground.

$$\text{Switch ON} \rightarrow I = \frac{V_{\text{ref}}}{R}$$

$$\text{Switch OFF} \rightarrow I = 0$$

Here, OP-Amp is used for Summing Amplifier,

The output current of OP-Amp is given by

$$I_{\text{out}} = I_1 + I_2 + I_3 + \dots + I_n$$

The output voltage across  $R_F$  is given by

$$V_o = -I_0 R_F$$

$$= -[I_1 + I_2 + I_3 + \dots + I_n] R_F$$

$$= -\left[\frac{V_{\text{ref}}}{2^R} d_1 + \frac{V_{\text{ref}}}{2^{2R}} d_2 + \frac{V_{\text{ref}}}{2^{3R}} d_3 + \dots + \frac{V_{\text{ref}}}{2^{nR}} d_n\right] R_F$$

$$= -V_{\text{ref}} \left[ \frac{d_1}{2R} + \frac{d_2}{2^2 R} + \frac{d_3}{2^3 R} + \dots + \frac{d_n}{2^n R} \right] R_f$$

$$= -V_{\text{ref}} \cdot \frac{R_f}{R} \left[ \frac{d_1}{2} + \frac{d_2}{2^2} + \frac{d_3}{2^3} + \dots + \frac{d_n}{2^n} \right]$$

If  $R_f = R$ ,

$$V_o = -V_{\text{ref}} \left[ \frac{d_1}{2} + \frac{d_2}{2^2} + \frac{d_3}{2^3} + \dots + \frac{d_n}{2^n} \right]$$


$$V_o = -V_{\text{ref}} \left[ d_1 \bar{2}^1 + d_2 \bar{2}^2 + d_3 \bar{2}^3 + \dots + d_n \bar{2}^n \right]$$

From above equation, it is clear that Analog output voltage is directly proportional to Input binary (digital) word.

Draw backs:-

It requires wide range of binary weighted resistors.  
As no. of bits increases, required range of resistors also increases.  
i.e it does not used for more than 8-bits.
 
## 2. R-2R ladder DAC (voltage switched) :-




\* It uses the resistors as R and 2R.

\* In this circuit R → Resistors are connected in series & 2R resistors are connected in parallel.


Ex:- consider 3-bit DAC as 100

$$d_1=1, d_2=0, d_3=0$$



The above circuit can be drawn as

 


The equivalent circuit as

 

  
$$\frac{2R \times 2R}{2R + 2R} = \frac{4R^2}{4R} = R$$



(4)

 
 
$$\left[ \because \frac{2R \times 2R}{2R + 2R} = \frac{4R^2}{4R} = R \right]$$





Apply Thevenin's voltage & Thevenin's resistance,

$$V_{TH} = \frac{(-V_R)(2R)}{2R+2R} = -\frac{V_R \cdot 2R}{4R} = -\frac{V_R}{2}$$

$\left[ \because \text{one resistance is connected to Ground & other one as -ve Voltage so apply Thevenin theorem.} \right]$

$$R_{TH} = 2R \parallel 2R = R$$

  

$$\text{The output voltage } V_O = -\frac{2R}{2R} \cdot \left( -\frac{V_R}{2} \right)$$

$\left[ \because \text{w.k.t Inverting op-Amp Gain} = -\frac{R_f}{R_i} \right]$


$$V_O = \frac{V_R}{2}$$

→ which is equivalent to binary input 100

In general, output voltage is given by

$$V_O = -V_R (d_1 \bar{2}^1 + d_2 \bar{2}^2 + d_3 \bar{2}^3 + \dots + d_n \bar{2}^n)$$

## R-2R Ladder DAC (current switched) :-

 

The main difference between circuit diagram in voltage switched & current switched is in place of OP-AMP we are connecting ground & in place of ground we are connecting OP-AMP.

$$I = \frac{V}{R}$$

$$\text{output voltage } V_o = -I' R_f$$

$$I' = \left[ \frac{I}{2} + \frac{I}{4} + \frac{I}{8} \right] \quad \text{— for 3-bit}$$

for N-bits

$$I' = \left[ \frac{I}{2} + \frac{I}{4} + \frac{I}{8} + \dots + \frac{I}{2^N} \right]$$


$$\begin{aligned} \Rightarrow V_o &= -R_f \left[ \frac{I}{2} + \frac{I}{4} + \frac{I}{8} + \dots + \frac{I}{2^N} \right] \\ &= -R_f \left[ \frac{V_R}{2R} d_1 + \frac{V_R}{4R} d_2 + \frac{V_R}{8R} d_3 + \dots + \frac{V_R}{2^N R} d_N \right] \\ &= -\frac{V_R R_f}{R} \left[ d_1 \bar{2}^1 + d_2 \bar{2}^2 + \dots + d_N \bar{2}^N \right] \end{aligned}$$

If  $R_f = R$ ,

$$V_o = -V_R \left[ d_1 \bar{2}^1 + d_2 \bar{2}^2 + d_3 \bar{2}^3 + \dots + d_N \bar{2}^N \right]$$
 
### 3. Inverted R-2R Ladder DAC :-

An inverted R-2R ladder type DAC employs voltage scaling, Identical resistors and Inverting summing OP-Amp.



$$I_1 = \frac{V_{ref}}{2R}$$

$$I_2 = \frac{\frac{V_{ref}}{2}}{2R} = \frac{V_{ref}}{4R}$$

$$I_3 = \frac{\frac{V_{ref}}{4}}{2R} = \frac{V_{ref}}{8R}$$

$\therefore$  The output Voltage  $V_o = -I_o R_f$

$$= -[I_1 + I_2 + I_3] R_f$$

$$= -R_f \left[ \frac{V_{ref}}{2R} d_1 + \frac{V_{ref}}{4R} d_2 + \frac{V_{ref}}{8R} d_3 \right]$$

For N-bit,

$$V_o = -R_f \left[ \frac{V_{ref}}{2R} d_1 + \frac{V_{ref}}{4R} d_2 + \frac{V_{ref}}{8R} d_3 + \dots + \frac{V_{ref}}{2^n R} d_n \right]$$


If  $R_f = R$ ,

$$V_o = -V_{ref} \left[ \frac{d_1}{2} + \frac{d_2}{2} + \frac{d_3}{3} + \dots + \frac{d_n}{2^n} \right]$$

For 3-bit DAC,

$$V_o = -V_{ref} \left[ d_1 \frac{1}{2^1} + d_2 \frac{1}{2^2} + d_3 \frac{1}{2^3} \right]$$

000	$\rightarrow$	$\frac{V_o}{0}$
001	$\rightarrow$	$\frac{V_R}{8}$
010	$\rightarrow$	$\frac{2V_R}{8}$
111	$\rightarrow$	$\frac{7V_R}{8}$

 


\* The minimum height of each staircase case is called Resolution (or) 1 LSB

IC 1408 DAC :- (or) monolithic DAC :-


The IC 1408 is an 8-bit R-2R ladder type D/A converter.

 The pin configuration of IC 1408 D/A converter is shown in fig.



- \* The ICMOS consists of an reference current amplifier, R-2R ladder and 8-high speed current switches. It has 8-input data lines d<sub>1</sub> (MSB) through d<sub>8</sub> (LSB).

 - \* It consists of 2-power supplies  $V_{CC} = 5V$ ,  $V_{EE} = -15V$



The output current is given by

$$I_{out} = \frac{V_{ref}}{R_{ref}} \left( \frac{d_1}{2} + \frac{d_2}{4} + \frac{d_3}{8} + \frac{d_4}{16} + \frac{d_5}{32} + \frac{d_6}{64} + \frac{d_7}{128} + \frac{d_8}{256} \right)$$

when all the data lines are at logic high,

$$\begin{aligned} I_{out} &= \frac{5}{2.5 \times 10^3} \left( \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16} + \frac{1}{32} + \frac{1}{64} + \frac{1}{128} + \frac{1}{256} \right) \\ &= 1.992 \text{ mA} \end{aligned}$$

The output current is converted into voltage by  $I$  to  $V$  converter.

The output voltage for full scale input can be given as

$$V_o = 1.992 \times 10^{-3} \times 2.5 \times 10^3 = 4.98 \text{ V}$$

Characteristics of IC 1408 :-

- power supply range  $\rightarrow V_{CC} = 5\text{V}$   
 $V_{EE} = -5\text{V} \text{ to } -15\text{V}$
- reference current for max. input scale  $\rightarrow 2\text{mA}$
- max. output current  $\rightarrow 1.992\text{mA}$
- settling time  $\rightarrow 300\text{ns}$
- Accuracy  $\rightarrow 0.1\%$

The typical circuit arrangement of IC 1408 as shown in fig.

 



Fig:- Typical circuit of IC 1408

\* From the figure, output in unipolar range.

\* When digital input is 00H, output voltage is 0V

\* When digital input is FFH, output voltage is 5V.

## A/D converters:

 

\* The A/D conversion is a quantizing process whereby an Analog signal is converted into equivalent binary word.

\* There are 2 types based on the conversion techniques

i) comparing analog signal with internally generated reference voltage  
it contains

- successive APPROXIMATION
- flash (or) parallel comparator type
- delta modulated
- Adaptive delta modulated


ii) In this technique, changing an Analog signal into time (or) frequency and comparing these new parameters against known values.

It contains i) Integrator converters  
ii) Voltage-to-frequency converters.
 
## b. Parallel comparator type (or) Flash ADC :-

In this technique used to improve speed of operation.  
All the comparators are connected in parallel.

→ For  $n$ -bit conversion, it requires  $2^{n-1}$  comparators &  $2^n$  resistors  
consider 3-bit flash A/D converter, it contains  ~~$2^3 - 1$~~   $2^3 - 1 = 7$   
comparators (or) op-Amps and  $2^3$  resistors.



- \* From the figure, one input of each comparator is connected to input signal and other input to reference voltage.
- \* The comparator give output 1 (or) 0 it depending on Input signal and reference signal.

If  $V_{in} > V_{ref}$  → The output of comparator is High (1)


$V_{in} < V_{ref}$  → The output of comparator is Low (0)

Advantage → It is a fastest A/D converter

Truth table of Flash type ADC :-

Input voltage	comparator outputs									Digital output		
	D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>		Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
$0 < V_{in} < \frac{V_{ref}}{8}$	0	0	0	0	0	0	0	1		0	0	0
$\frac{V_{ref}}{8} < V_{in} < \frac{2V_{ref}}{8}$	0	0	0	0	0	0	1	x		0	0	1
$\frac{2V_{ref}}{8} < V_{in} < \frac{3V_{ref}}{8}$	0	0	0	0	0	1	1	x		0	1	0
$\frac{3V_{ref}}{8} < V_{in} < \frac{4V_{ref}}{8}$	0	0	0	0	1	1	1	x		0	1	1
$\frac{4V_{ref}}{8} < V_{in} < \frac{5V_{ref}}{8}$	0	0	0	1	1	1	1	x		1	0	0
$\frac{5V_{ref}}{8} < V_{in} < \frac{6V_{ref}}{8}$	0	0	1	1	1	1	1	x		1	0	1
$\frac{6V_{ref}}{8} < V_{in} < \frac{7V_{ref}}{8}$	0	1	1	1	1	1	1	x		1	1	0
$V_{in} > \frac{7V_{ref}}{8}$	1	1	1	1	1	1	1	x		1	1	1
 
## 2. Counter type (or) Ramp type A/D converter :-



\* In this type, the output of DAC is continuously compared with Analog Input to ADC which is to be converted into digital output.

### Operation:-


- i) Initially, the counter is Reset, i.e. output is zero by applying a reset pulse. The output of counter is given to Input of DAC it produces as zero i.e.  $V_d = 0$ .
- ii) when  $V_{in} > V_d$ , the output of comparator becomes high.
- iii) It is given to 1 Input of AND gate, and 2<sup>nd</sup> Input is clock pulses.  
i.e. For an AND gate, one input is clock pulses and other input is output of comparator. Because of high output of comparator, the clock pulses are allowed to pass through AND gate.

iv) The counter starts counting these clock pulses. According to no. of clock pulses, the output of counter increasing. It increases output of DAC.

v) If  $V_{in} < V_d$ , the output of comparator becomes low. This disables AND gate, so the clock pulses are not allowed to pass through AND gate. The counting process of N-bit counter is stopped.

→ In this type, we are using  $2^N - 1$  clock pulses.

waveforms:-

 


## Disadvantages:

- There is a limitation in clock frequency, As clock frequency is low, speed of conversion is less.
- conversion time is not constant. It increases with increase in Input voltage. (or) conversion time is high at high input voltage.
 
## 3. successive APPROXIMATION type A/D converter :-

It consists of DAC, comparator, successive approximation register (SAR).



- \* Soc (start of conversion) used for Initiates an A/D conversion process.
- \* Eoc (End of conversion) used for activating when conversion is completed.

The SAR consists of 2 conditions

i) whenever switch is ON, MSB of SAR set to '1'.


ii) when  $V_{in} > V_d \rightarrow$  set your next bit (from MSB to LSB)

when  $V_{in} < V_d \rightarrow$  already set bit is going to reset and it will set next bit.

for example, consider  $V_{in}=3$  (3-bit successive Approximation)

The Input is 3-bits,

 i) switch is ON, MSB set to '1' i.e 100 (3-bits)



\* In this case we are using 3-bits so, 3-clock cycles are used

\* For N-bit, we can use N-clock cycles.

\* The time for one Analog to digital conversion must depend on both the clock's period  $T$  and No. of bits ' $n$ '.

It is given as,

$$T_c = T(n+1)$$

where  $T_c \rightarrow$  conversion time

$T \rightarrow$  clock period

$n \rightarrow$  No. of bits

#### 4. Dual-slope ADC :-

Dual slope conversion is an Indirect method for A/D conversion where an Analog voltage & reference voltage are converted into Time Periods by an Integrator & measured by counter.

 


Fig :- Dual slope A/D converter

\* It consists of Integrator (Ramp generator), comparator, Binary counter, output latch and reference Voltage.

→ Integrator Input is switched between Analog Input voltage  $V_i$  and negative reference voltage,  $-V_{REF}$ .

→ Analog switch is controlled by msb of counter.

when msb = logic 0 → analog input is connected to integrator

when msb = logic 1 →  $\frac{-V_R}{R_1 C_1}$  Reference Voltage is connected to ramp generator (integrator)

 


Fig :- Integrator output voltage

At time  $t=0$ , Analog switch 'S' is connected to Analog input voltage  $V_i$ , so that Analog input voltage Integration begins.

The output voltage is

$$V_{oi} = \frac{1}{R_1 C_1} \int_0^t V_i dt$$

$$= -\frac{V_i t}{R_1 C_1} \quad \text{--- (1)}$$

$R_1 C_1 \rightarrow \text{Time const.}$   
 $V_i \rightarrow \text{also constant.}$

→ At the end of  $2^N$  clock periods msb of counter goes high.

It gives flip flop also high, which causes analog switch 'S' to be switched from  $V_i$  to  $-V_R$ .

- The -ve input voltage ( $-V_R$ ) connected to input of Integrator caused the Integrator output to ramp positive.
- When Integrator output reaches to zero, comparator output voltage goes low, which disables clock AND gate. This stops clock pulses reaches the counter, so that counter will be stopped at a count corresponding to no. of clock pulses in time  $t_2$ .

→ Integrator o/p <sup>ramp</sup><sub>x</sub> down to voltage  $V$  and get back to 0. So, charge voltage is equal to discharge voltage,

$$\frac{V_i t_1}{R_1 C_1} = \frac{V_R t_2}{R_1 C_1}$$

$$V_i t_1 = V_R t_2 \Rightarrow \boxed{t_2 = \frac{V_i t_1}{V_R}} \quad \text{--- (2)}$$

- The actual conversion of Analog voltage  $V_{in}$  into a digital count occurs during  $t_2$ .

The control circuit connects the clock to counter at begining of  $t_2$ . The clock is disconnected at end of  $t_2$ . Thus counter contains digital output

$$\therefore \text{Digital output} = \left( \frac{\text{counts}}{\text{second}} \right) t_2 \quad \text{--- (3)}$$

From eq(2)

$$\text{Digital output} = \left( \frac{\text{counts}}{\text{second}} \right) t_1 \left( \frac{V_i}{V_R} \right) \quad \text{--- (4)}$$

The counter o/p is connected to digital display.

### Advantages

- High accurate
- Low cost
- Immune to temperature caused variations in  $R_1, C_1$ .

### Disadvantage

- \* Low Speed

## Performance specifications of DAC :-

### 1. Accuracy:-

It is defined as the difference between measured output and actual output.

- Absolute accuracy refers to maximum deviation of measured output from the actual output value.
- It is expressed in percentage of its full scale voltage (or) fractions of  $\pm \frac{1}{2}$  of its LSB.

$$\text{Accuracy} = \frac{V_{\text{OFS}}}{(2^n-1)2}$$

### 2. Resolution:-

→ It is defined as no. of different analog output values provided by a DAC.

$$\text{for } n\text{-bit DAC} \rightarrow \text{Resolution} = 2^n$$

- It is also stated that, the ratio of change in output voltage resulting from a change of 1 LSB at digital inputs.


$$\text{for } n\text{-bit DAC} \rightarrow \text{Resolution} = \frac{V_{\text{OFS}}}{2^n-1}$$

where,  $V_{\text{OFS}}$  → full scale output voltage.
 
### 3. settling time:- (conversion time)

It is defined as the time taken by the output of converter to reach and stay within  $\pm \frac{1}{2}$  LSB of its final value for a given change in input.

- settling time of a converter varies between 10ns to 10μs.



#### 4. Dynamic range:-


It is defined as the ratio of largest output to the smallest output, excluding zero.

→ It is expressed in dB.

$$\text{Dynamic range} = 20 \log 2^n \approx 6n.$$

 
#### 5. offset error:-

It is defined as the nonzero level of output voltage when all inputs are zero.


 
#### 6. Gain error:-

It is defined as the difference between the calculated gain of the current to voltage converter & actual gain achieved.



## 7. stability :-

The performance of converter changes with temperature, age and power supply variations. So all the parameters such as offset, gain, linearity error and monotonicity must be specified over the full temperature and power supply ranges.

These parameters represent the stability of converter.

## 8. monotonicity:-

It is defined as no variations (or) linear increase in Analog output for an increase in digital input.

→ If the output of DAC does not increase linearly (or) sometimes decreases for linear increase in input, then DAC is said to be non-monotonic DAC.

## 9. Linearity :-

The term linearity describes how close the measured output appears to its ideal (actual) transfer characteristics. Thus, linearity of a DAC is defined as a measure of its accuracy.

- In case of Ideal DAC, the output linearly increases for an increase in Input.
- In case of Practical, the output is not linear even though there is an equal increment in output.

## Performance Specifications of ADC :-

### i. Resolution:-

i) same as DAC definition

ii) It also defined as, the ratio of change in Input voltage resulting from a change of 1LSB at digital outputs.

$$\text{for } n\text{-bit ADC, Resolution} = \frac{V_{IFS}}{2^n - 1}$$

where,  $V_{IFS} \rightarrow$  Full scale Input voltage.

## 2. conversion time (or) settling time :-

It is defined as the total time required to convert an Analog signal into digital output.

→ It depends on conversion technique used and the propagation delay of circuit parameters.

## AD574A (12-bit ADC converter) specifications

It requires no external components to provide the complete successive approximation based on Analog to digital conversion. The performance specifications are given as

### 1. Power supply

- i) Positive power supply voltage  $V_{DD}$  : +14V to +16.5
- ii) Negative power supply voltage  $V_{SS}$  : -14V to -16.5
- iii) Logic : +14.5 to +5.6

2. Resolution : 12-bit

3. Linearity error :  $\pm 1LSB$

4. Temperature range : 0 to  $70^{\circ}\text{C}$

5. Analog input range : -5 to +5V

6. Internal reference voltage : 9.98 to 10.02

7. Maximum conversion time : 35μS

### 8. Operating current

$I_{Logic}$  : 30-40mA

$I_{CC}$  : 2-5mA

$I_{EE}$  : 18-30mA

9. Power dissipation : 390mW (typical)

: 725mW (maximum)

### Problems

The 1LSB of a 10-bit DAC is  $20\text{mV}$ .

i) what is v. resolution ii) what is full scale range

iii) what is o/p voltage for an input,  $10110\ 01101$

i)  $\% \text{resolution} = 80 \times 10^3 \times 100 = 2\%$

ii)  $V_{\text{FS}} = 2^{10} - 1 \times \text{Resolution} = 2^{10} - 1 \times 0.2 = 20.46$

iii)  $(1011001101)_2 = (1 \times 2^9 + 0 \times 2^8 + 1 \times 2^7 + 1 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0)$   
 $= 512 + 128 + 64 + 8 + 4 + 1 = 717$

$\therefore \text{output voltage } V_{\text{out}} = 717 \times 20 \times 10^{-3} = 14.34\text{V}$

2. LSB of 9-bit DAC is represented by  $19.6\text{mV}$ . If an input of 9 zero bits is represented by 0V.

i) find the output of DAC for an Input,  $101101101$  and  $011011011$

ii) what is the full scale reading (FSR) of this DAC.

iii)  $(101101101)_2 = 1 \times 2^8 + 0 \times 2^7 + 1 \times 2^6 + 1 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0$   
 $= 365$

Output  $V_{\text{out}} = 365 \times 19.6 \times 10^{-3} = 7.15\text{V}$

iv)  $(011011011)_2 = 0 \times 2^8 + 1 \times 2^7 + 1 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0$   
 $= 219$

$\therefore V_{\text{out}} = 219 \times 19.6 \times 10^{-3} = 4.29\text{V}$

v) Full scale reading (FSR)  $= (2^9 - 1)$  of  $19.6\text{mV}$

$= (2^9 - 1) \times 19.6 \times 10^{-3}$

$= 10\text{VOLTS}$

3. calculate the conversion time for a full scale input in case of 12-bit counter type Analog to digital converter driven by 2MHz clock.

$$T = \frac{1}{2 \times 10^6} = 0.5 \mu s$$

for 12-bit counter type  $= (2^n - 1) \times T$

$$= (2^{12} - 1) \times 0.5 \times 10^{-6} = 2.047 \text{ ms}$$

4. if the max. output voltage of 7-bit DAC is 25.4 V, what is the smallest change in output as the binary count increases.

$$\text{Resolution} = \frac{V_{OFS}}{2^n - 1} = \frac{25.4}{2^7 - 1} = 0.2 \text{ V}$$

5. determine o/p voltage produced by a 7-bit DAC whose o/p voltage range is 0 to 10V when the binary no. is 0110

$$\text{G.T } V_{OFS} = 10 \text{ V}$$

$$\text{Resolution} = \frac{10}{2^7 - 1} = 0.6667 \text{ V}$$

$$\text{o/p voltage at } 0110 = 0.6667 \times 6 = 4 \text{ V}$$

6. Determine the resolution of an 8-bit A/D ADC for an 10V Input.

$$\text{Resolution} = \frac{V_{IFS}}{2^n - 1} = \frac{10}{2^8 - 1} = 39.215 \text{ mV}$$

7. calculate the no. of bits required to represent a full scale voltage of 10V with a resolution of 5mV approximately.

$$\text{resolution} = \frac{V_{OFS}}{2^n - 1} \Rightarrow 2^n - 1 = \frac{V_{OFS}}{\text{Resolution}}$$

$$\Rightarrow 2^n = \frac{V_{OFS}}{\text{Resolution}} + 1 = \frac{10}{5 \times 10^{-3}} + 1 = 2001$$

$$\Rightarrow 2^n = 2001$$

when n=11, we have  $2^n = 2048$ ,  $\therefore$  minimum 11 bits are required to represent a full scale voltage of 10V.

- 8) A 12-bit D to A converter has a full scale range of 15V. Its max. differential linearity error is  $\pm \frac{1}{2}$  LSB.

i) what is the percentage resolution?

ii) what are min. and max. possible values of increment in its output voltage.

Given  $n=12$ ,  $V_{FS} = 15V$

i) percentage resolution :-

$$\% \text{ Resolution} = \frac{V_{FS}}{2^n} \times 100 = \frac{15}{2^{12}} \times 100 = 0.366\% \text{ Volts}$$

ii) min. and max. values of output voltage :-

$$MSB = \frac{V_{FS}}{2} = \frac{15}{2} = 7.5V$$

$$LSB = \frac{V_{FS}}{2^n} = \frac{15}{2^{12}} = 3.66mV$$

- 9) An Inverted R-2R ladder type digital to Analog converter  $R=10k\Omega$ ,  $V_{ref}=+20V$   
find the current in each  $20k\Omega$  resistor and max. current passing into  
feed back resistor OP-AMP.

Given  $R=10k\Omega$ ,  $V_{ref}=20V$ ,  $2R=20k\Omega$

Let Inverted R-2R Ladder type D/A converter is 4-bit converter

i.e  $n=4$

$$I_1 = \frac{V_{ref}}{2R} = \frac{20}{2 \times 10^3} = 1mA$$

$$I_2 = \frac{V_{ref}/2}{2R} = \frac{V_{ref}/2R}{2} = \frac{I_1}{2} = \frac{1mA}{2} = 0.5mA$$

$$I_3 = \frac{V_{ref}/4}{2R} = \frac{V_{ref}/4R}{2} = \frac{I_2}{2} = \frac{0.5mA}{2} = 0.25mA$$

$$I_4 = \frac{V_{ref}/8}{2R} = \frac{V_{ref}/8R}{2} = \frac{I_3}{2} = \frac{0.25mA}{2} = 0.125mA$$

The output voltage of D/A converter is given by

$$\begin{aligned}
 V_{\text{out}} &= -I_{\text{out}} R_f \\
 &= -[I_1 + I_2 + I_3 + I_4] R \quad \{ \because R_f = R \} \\
 &= -\left[\frac{V_{\text{ref}}}{2R} + \frac{V_{\text{ref}}}{4R} + \frac{V_{\text{ref}}}{8R} + \frac{V_{\text{ref}}}{16R}\right] R \\
 &= -V_{\text{ref}} \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}\right) \\
 &= -20 \left[\frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \frac{1}{16}\right] = -18.75 \text{V}
 \end{aligned}$$

- 10) Design a 4-bit weighted resistor DAC whose full-scale output voltage is -10V. Assume  $R_f = 10\text{k}\Omega$ , Logic '1' level as +5V, logic '0' level as '0' volts. what is the output voltage when input is 1011.

Given:  $V_{\text{ref}} = -10\text{V}$ ,  $R_f = 10\text{k}\Omega$ , Logic '1' level as +5V  
Logic '0' level as 0V

The output voltage is,  $V_{\text{out}} = I_{\text{out}} R_f$

$$= \frac{V_R}{R} R_f \left[\frac{d_1}{2} + \frac{d_2}{2^2} + \frac{d_3}{2^3} + \frac{d_4}{2^4}\right]$$

If  $R_f = R$ ,  $V_R = V_{\text{ref}} = -10\text{V}$  then

$$\begin{aligned}
 \therefore V_{\text{out}} &= -10 \left[5 \times \frac{1}{2} + 0 \times \frac{1}{2^2} + 5 \times \frac{1}{2^3} + 5 \times \frac{1}{2^4}\right] \\
 &= -10[34.375]
 \end{aligned}$$

$\{ \because '1' \rightarrow 5$   
 $\& '0' \rightarrow \text{as '0'} \}$   
Input  $\rightarrow \begin{matrix} 1 & 0 & 1 & 1 \\ 5 & 0 & 5 & 5 \end{matrix}$

$$\therefore V_{\text{out}} = -34.375 \text{V}$$